

Chap 6 Structures for Discrete-Time Systems

- Introduction
- Block Diagram Representation of LCCDE
- Signal Flow Graph of LCCDE
- Basic Structures for IIR Systems
- Transposed Forms
- Basic Network Structures for FIR Systems
- Lattice Structures
- Overview of Finite-Precision Numerical Effects
- Effects of Coefficient Quantization
- Effects of Roundoff Noise in Digital Filters
- Zero-Input Limit Cycles in Fixed-Point Realizations of IIR Digital Filters

1. Introduction

- Structures $\leq \Rightarrow$ Implementation
 - ▣ Interconnection of additions, multiplications, delay.
- Approaches
 - ▣ A combination of algebraic manipulations and manipulations of block diagram representations.
 - ▣ Derive equivalent equivalent structures.
- Pondering Questions
 - ▣ Finite Impulse Response
 - ▣ Infinite Impulse Response
 - ▣ Numerical Problems in Implementation

2. Block Diagram Representation of LCCDE

Notations

■ Addition

■ Multiplication




■ Delay

Example

■ $y[n] = a_1 y[n-1] + a_2 y[n-2] + bx[n]$

$$y[n] - \sum_{k=1}^N a_k y[n-k] = \sum_{k=0}^M b_k x[n-k]$$
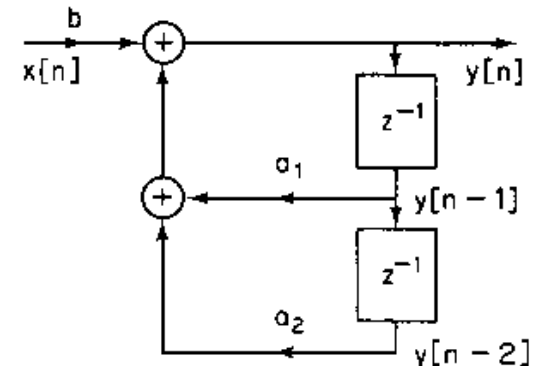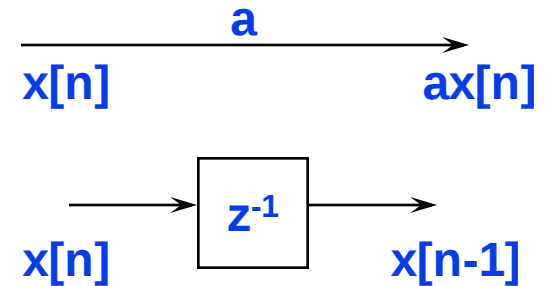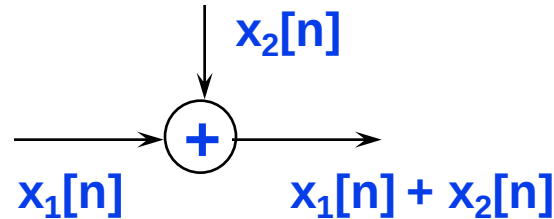
$$H(z) = \frac{\sum_{k=0}^M b_k z^{-k}}{1 - \sum_{k=1}^N a_k z^{-k}}$$



2. Block Diagram Representation of LCCDE (c.1)

Block Diagram 1


Difference Equations

$$v[n] = \sum_{k=0}^M b_k x[n-k]$$

$$y[n] = \sum_{k=0}^M b_k x[n-k] + v[n]$$

Transfer Function
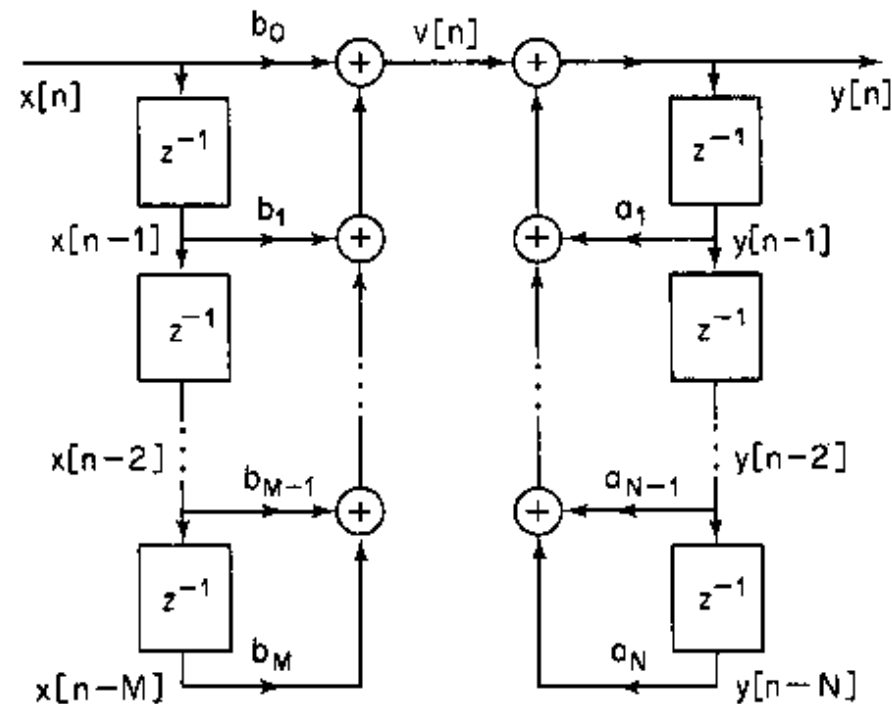
$$H(z) = H_2[z]H_1[z] = \left(\frac{1}{1 - \sum_{k=1}^N a_k z^{-k}} \right) \left(\sum_{k=0}^M b_k z^{-k} \right)$$



Direct Form I

2. Block Diagram Representation of LCCDE (c.2)

Block Diagram 2

Transfer Function



$$H(z) = H_1[z]H_2[z] = \left(\sum_{k=0}^M b_k z^{-k} \right) \left(\frac{1}{1 - \sum_{k=1}^N a_k z^{-k}} \right)$$

$$w[n] = \sum_{k=0}^M b_k w[n-k]$$

Equations

$$y[n] = \sum_{k=0}^M b_k w[n-k]$$



Direct Form II or Canonic Direct Form

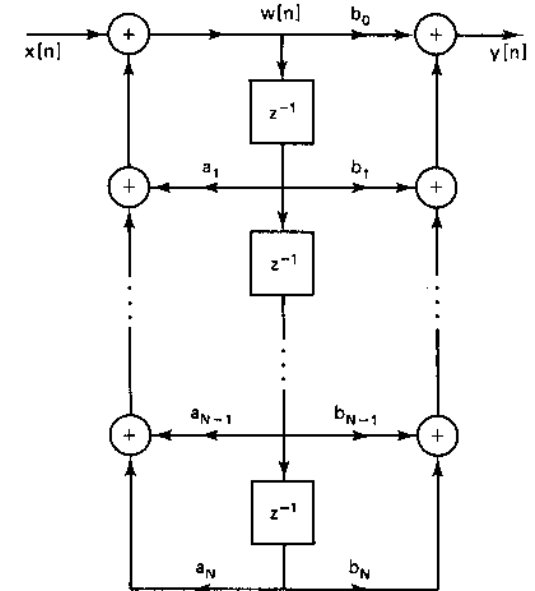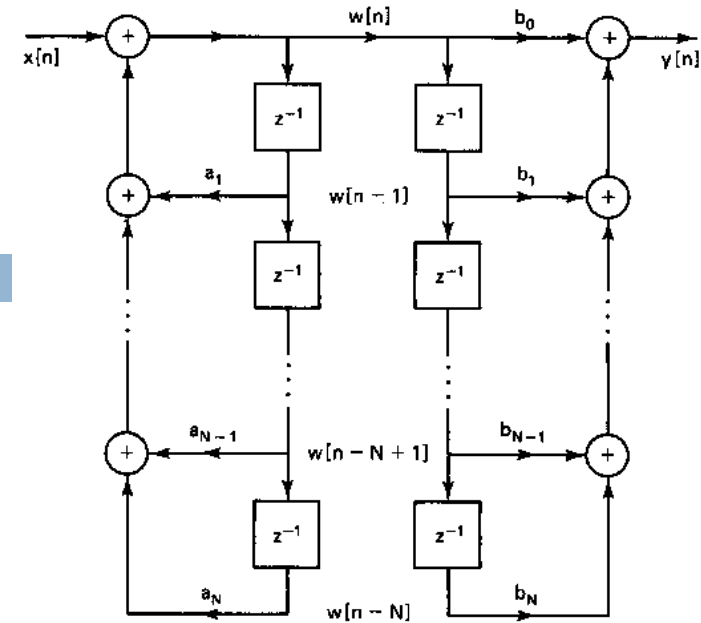

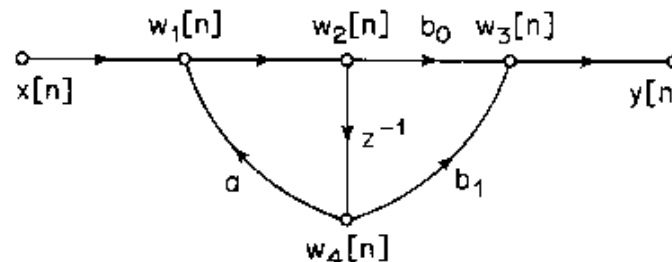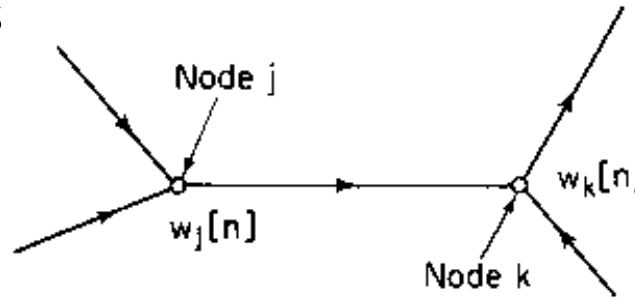3. Signal Flow Graph of LCCDE



□ Signal Flow Graph

- ▣ A network of directed branches that at nodes.
- ▣ Source nodes
- ▣ Sink nodes
- ▣ branch gains



$$w_2[n] = aw_2[n-1] + x[n]$$

$$y[n] = b_0w_2[n] + b_1w_2[n-1]$$

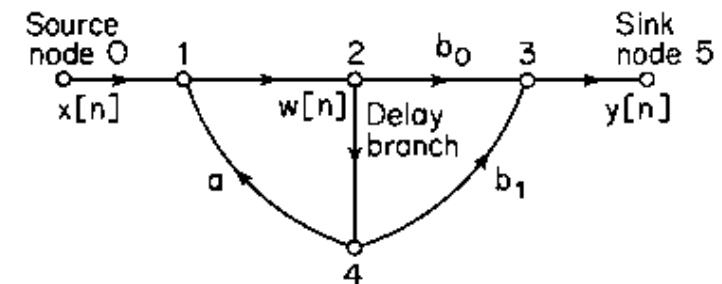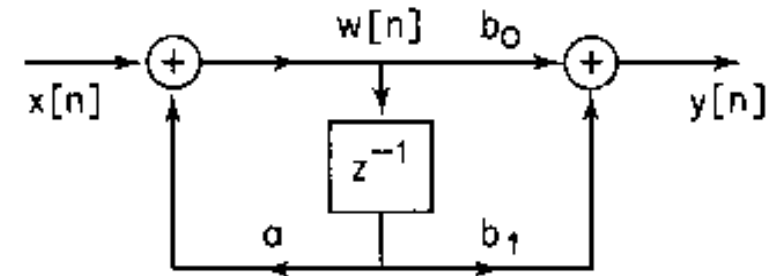


4. Basic Structures for IIR Systems

□ Signal Flow Graphs


- Direct Form I

- Direct Form II

Direct Form I

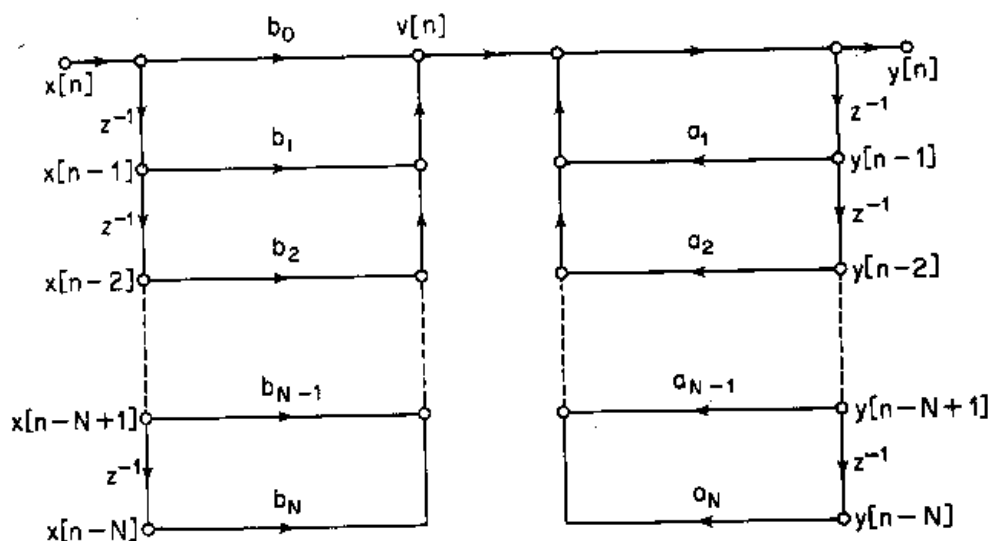


Direct Form II

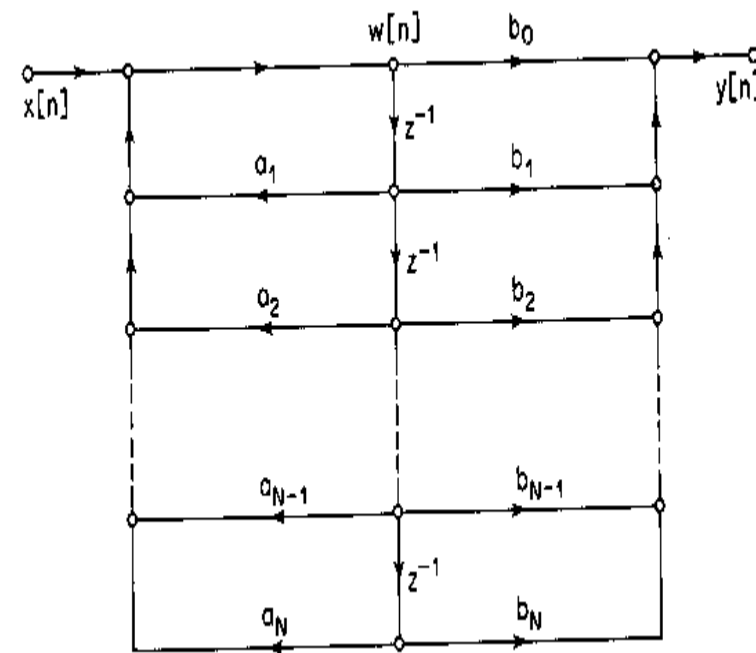

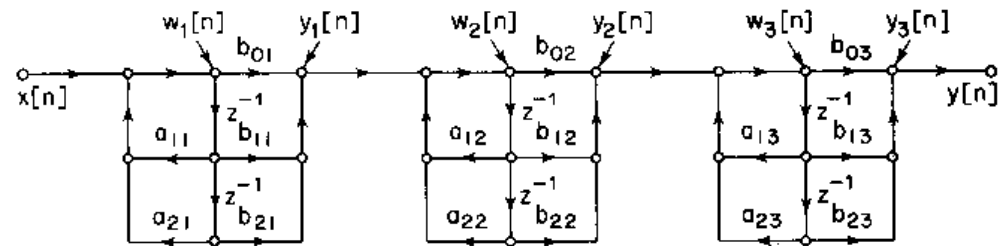4. Basic Structures for IIR Systems (c.1)


□ Cascade Form

$$H(z) = \prod_{k=1}^{N_s} \frac{b_{0k} + b_{1k}z^{-1} + b_{2k}z^{-2}}{1 - a_{1k}z^{-1} + a_{2k}z^{-2}}$$



□ Parallel Form
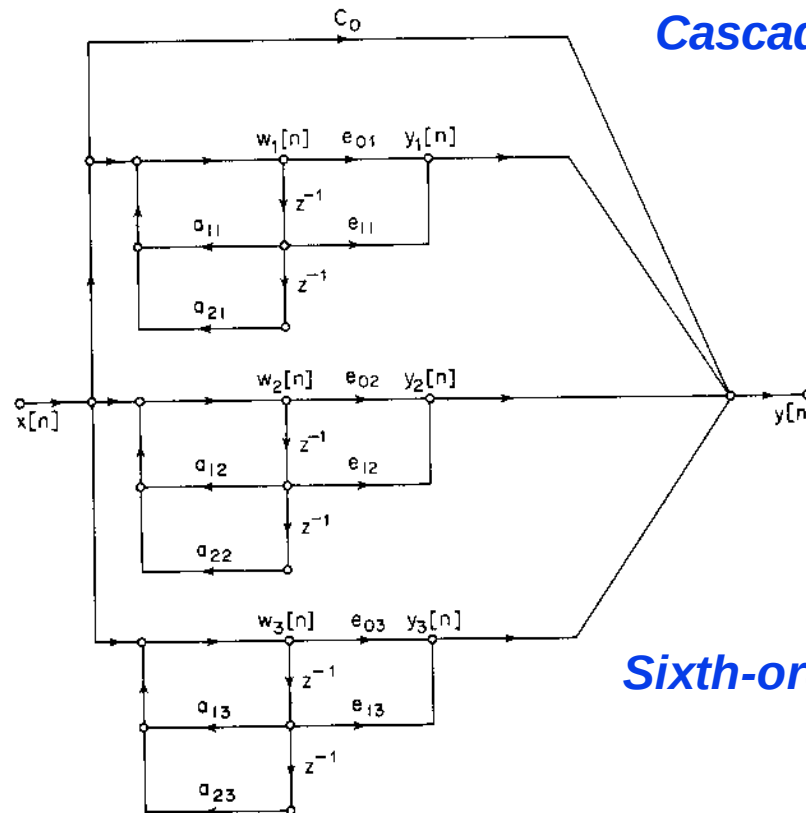
$$H(z) = \sum_{k=0}^{N_p} C_k z^{-k} + \sum_{k=1}^{N_1} \frac{A_k}{1 - c_k z^{-1}} + \sum_{k=1}^{N_1} \frac{B_k (1 - e_k z^{-1})}{(1 - d_k z^{-1})(1 - d_k^* z^{-1})}$$








Cascade Structures

Sixth-order system

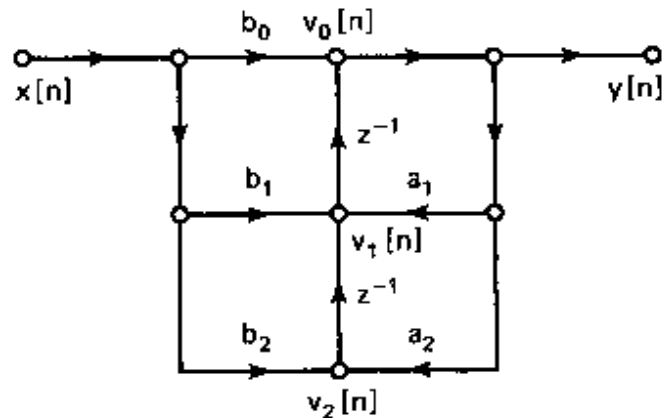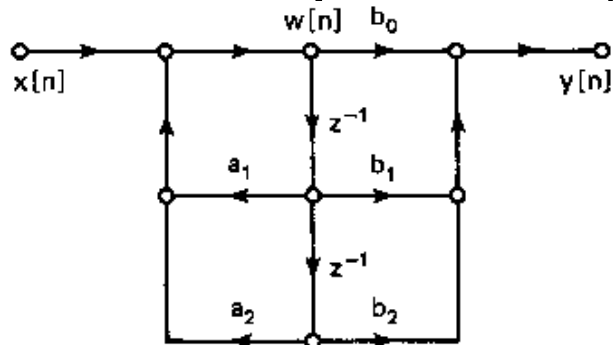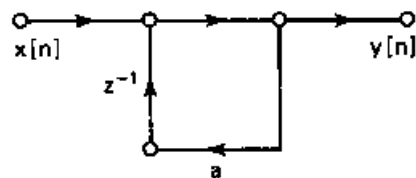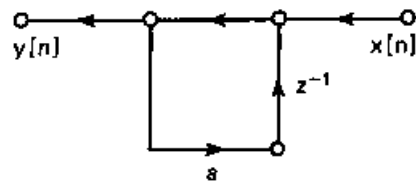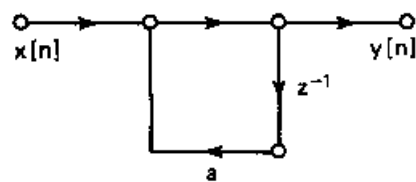5. Transposed Forms

□ Flow Graph Reversal $\Rightarrow$ Equivalent I/O Relation



$$w[n] = a_1 w[n-1] + a_2 w[n-2] + x[n],$$

$$y[n] = b_0 w[n] + b_1 w[n-1] + b_2 w[n-2].$$

$$v_0[n] = b_0 x[n] + v_1[n-1],$$


$$y[n] = v_0[n],$$

$$v_1[n] = a_1 y[n] + b_1 x[n] + v_2[n-1],$$


$$v_2[n] = a_2 y[n] + b_2 x[n].$$

5. Transposed Forms (c.1)

□ Transposed of Direct Form I

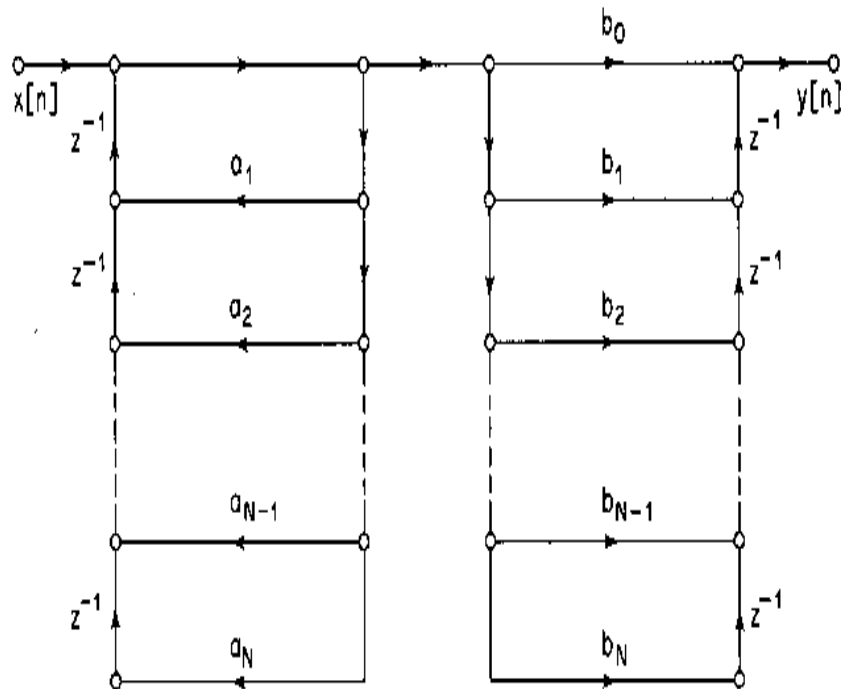

□ ***Transposed of Direct Form II***

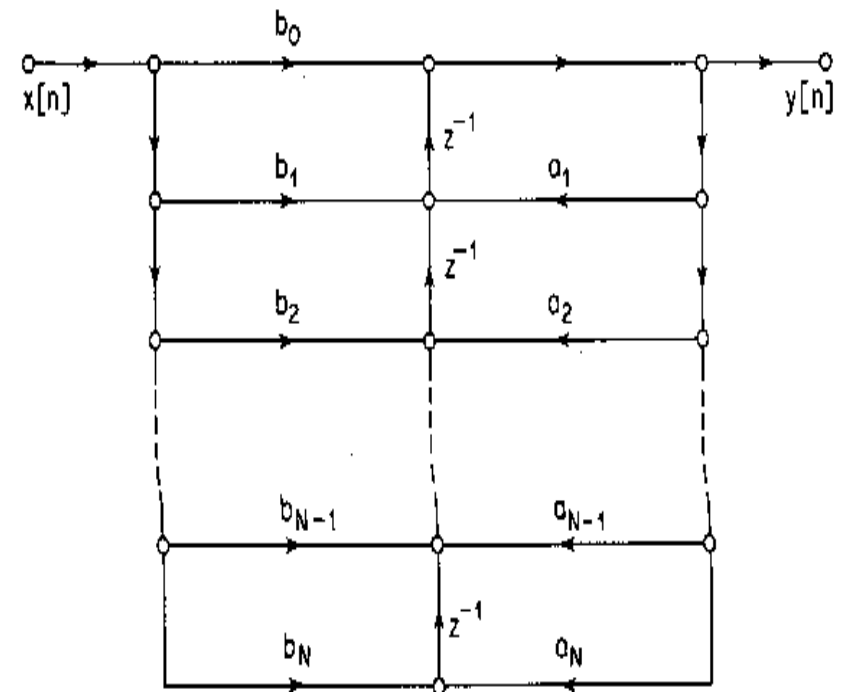

6. Basic Network Structures for FIR Systems

□ Direct Form


$$y[n] = \sum_{k=0}^M b_k x[n-k]$$

▣ Derived from the direct form



□ Cascade Form

$$H(z) = \sum_{k=1}^M h[k] z^{-k}$$
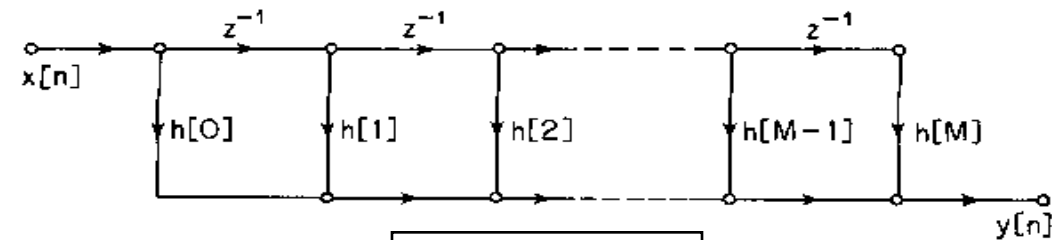
$$= \prod_{k=1}^{M_s} (b_{0k} + b_{1k} z^{-1} + b_{2k} z^{-2}), \quad M_s = \lfloor (M+1)/2 \rfloor$$



Transposed

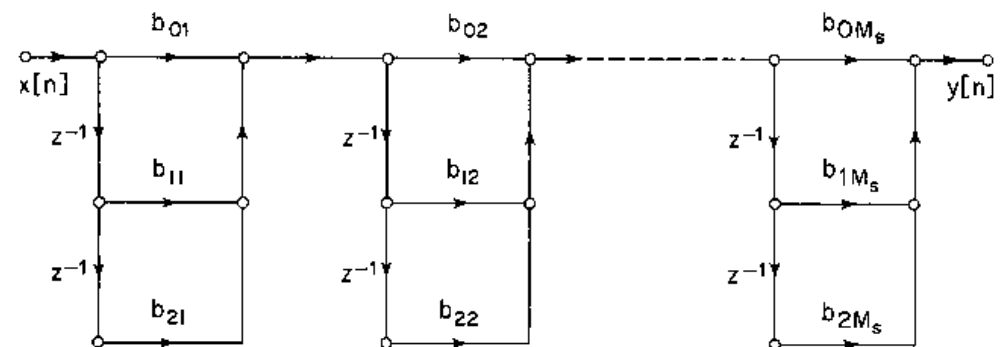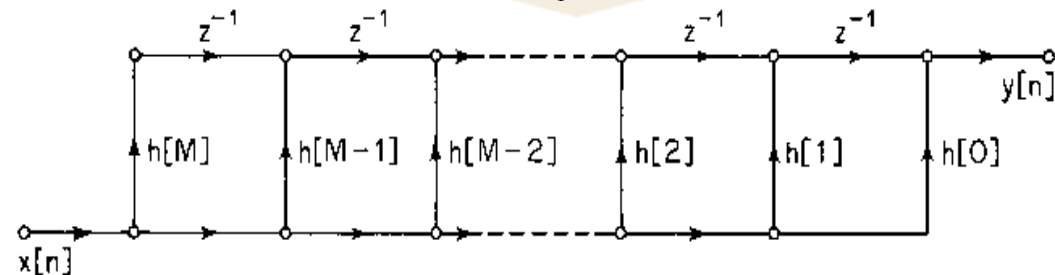

6. Basic Network Structures for FIR Systems

□ Linear Phase FIR Structure

- ▣ M even for Type I and III systems

$$h[M - n] = h[n]$$

or

$$h[M - n] = -h[n]$$


- ▣ Consider the following form

$$y[n] = \sum_{k=0}^M h[k] x[n - k]$$

$$= \sum_{k=0}^{M/2-1} h[k] x[n - k] + h[M/2] x[n - M/2] + \sum_{k=M/2+1}^M h[k] x[n - k]$$

$$= \sum_{k=0}^{M/2-1} h[k] x[n - k] + h[M/2] x[n - M/2] + \sum_{k=0}^{M/2-1} h[M - k] x[n - M + k]$$

6. Basic Network Structures

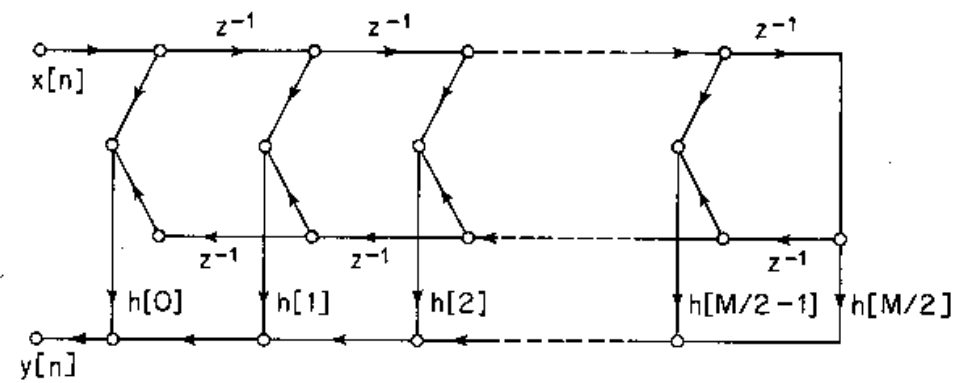

- Type I Systems (M is even)

$$y[n] = \left\{ \sum_{k=0}^{M/2-1} h[k](x[n-k] + x[n-M+k]) \right\} + h[M/2]x[n-M/2]$$

- Type III Systems (M is even)


$$y[n] = \left\{ \sum_{k=0}^{M/2-1} h[k](x[n-k] - x[n-M+k]) \right\} + h[M/2]x[n-M/2]$$

- Type II Systems (M is odd)

$$y[n] = \left\{ \sum_{k=0}^{M/2-1} h[k](x[n-k] + x[n-M+k]) \right\}$$

- Type IV Systems (M is odd)
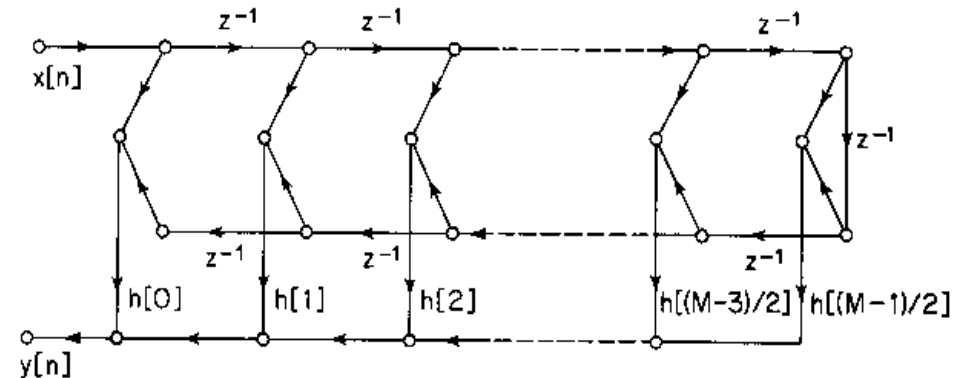
$$y[n] = \left\{ \sum_{k=0}^{M/2-1} h[k](x[n-k] - x[n-M+k]) \right\}$$



6. Basic Network Structures for FIR Systems (c.2)


- The zeros of a linear phase system
 - ▣ Zeros occurs in mirror-image pairs.
 - Ex. z_0 is a zero and $1/z_0^*$ also a zero.
 - ▣ Real zeros not on the unit circle occur in reciprocal pairs.
 - Grouped into a pair of two
 - ▣ Complex zeros occurs in group of four

□ Ex.

$$H(z) = h[0](1 + z^{-1})(1 + az^{-1} + z^{-2}) \\ \times (1 + bz^{-1} + z^{-2})(1 + cz^{-1} + dz^{-2} + cz^{-3} + z^{-4})$$

where $a = (z_2 + 1/z_2)$, $b = 2\text{Re}(z_3)$,

$$c = -2\text{Re}(z_1 + 1/z_1), d = 2 + |z_1 + 1/z_1|^2$$

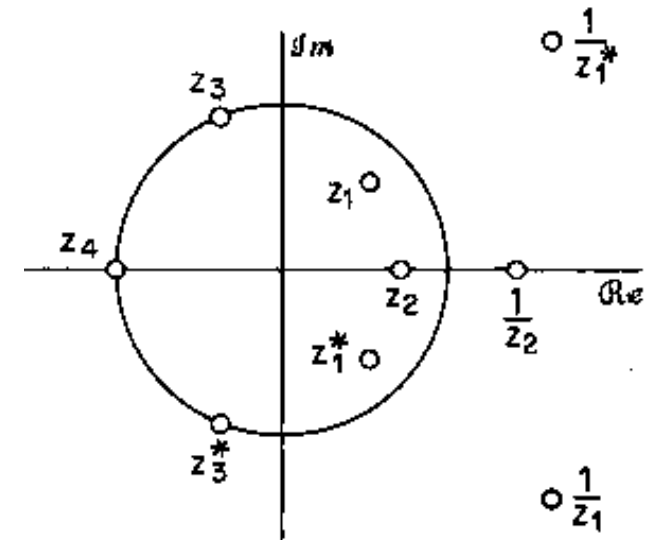

7. Lattice Structures

□ FIR Lattice

▣ An alternative of the filter structures

▣ The difference equations

$$e_0[n] = \tilde{e}_0[n] = x[n]$$


$$e_i[n] = e_{i-1}[n] - k_i \tilde{e}_{i-1}[n-1], \quad i = 1, 2, \dots, N$$

$$\tilde{e}_i[n] = -k_i e_{i-1}[n] + \tilde{e}_{i-1}[n-1], \quad i = 1, 2, \dots, N$$

$$y[n] = e_N[n]$$

$$h[0] = 1$$

$$h[N] = -k_N$$

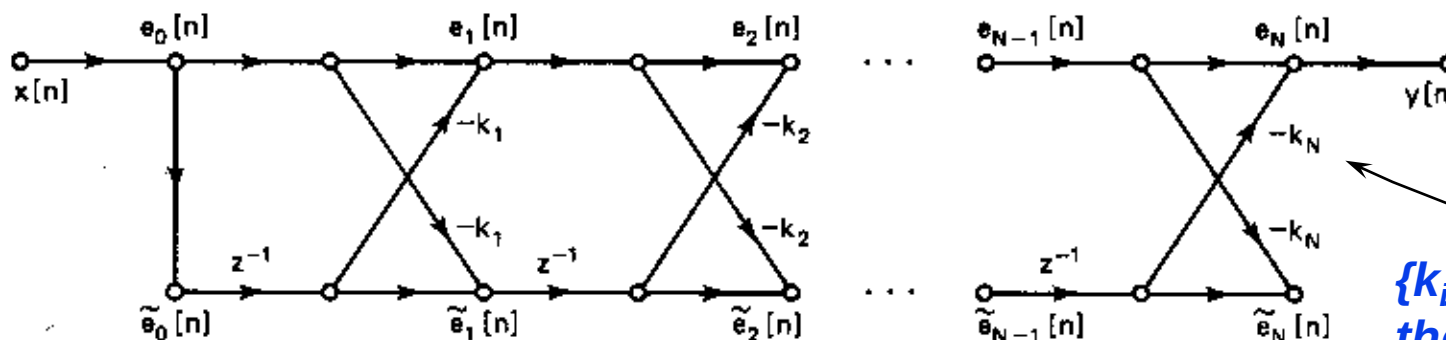

$\{k_i\}$ is
the k -parameters

7. Lattice Structures (c.1)

□ Relation with the impulse response

▣ Define the impulse response

$$h[n] = \begin{cases} 1, & \text{for } n = 0 \\ -a_n, & \text{for } n = 1, 2, \dots, N. \\ 0, & \text{otherwise} \end{cases}$$

$$A_i(z) = \frac{E_i(z)}{E_0(z)} = \left[1 - \sum_{m=1}^i a_m^{(i)} z^{-m} \right] \quad \text{and} \quad \tilde{A}_i(z) = \frac{\tilde{E}_i(z)}{\tilde{E}_0(z)}$$

▣ Define


$$A_0(z) = \tilde{A}_0(z) = 1; \quad X(z) = E_0(z) = \tilde{E}_0(z); \quad A(z) = A_N(z)$$

$$E_0(z) = \tilde{E}_0(z) = X(z)$$

$$E_i(z) = E_{i-1}(z) - k_i z^{-1} \tilde{E}_{i-1}(z), \quad i = 1, 2, \dots, N$$

$$\tilde{E}_i(z) = -k_i E_{i-1}(z) + z^{-1} \tilde{E}_{i-1}(z), \quad i = 1, 2, \dots, N$$

$$Y(z) = E_N(z)$$

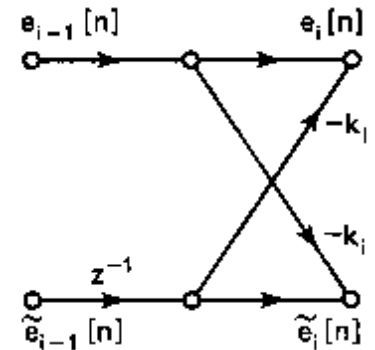

7. Lattice Structures (c.2)

□ Recurrence Formula

- ▣ The coefficient of z^{-m} is

$$a_i^{(i)} = k_i,$$

$$a_m^{(i)} = a_m^{(i-1)} - k_i a_{i-m}^{(i-1)}, \quad m = 1, 2, \dots, (i-1)$$

$$a_m = a_m^{(N)}, \quad m = 1, 2, \dots, N.$$

- The final set of coefficients is

$$a_m^{(N)} = a_m, \quad m = 1, 2, \dots, N.$$

- ▣ The recursion is repeated for $l=1, 2, \dots, N$, and the final set of coefficients for $A(z)=A_N(z)$ is

$$k_i = a_i^{(i)},$$

$$a_m^{(i-1)} = \frac{a_m^{(i)} + k_i a_{i-m}^{(i)}}{1 - k_i^2}, \quad m = 1, 2, \dots, (i-1)$$

Reflection coefficients
or PARCOR coefficients

7. Lattice Structures (c.3)

□ Example

$$A(z) = (1 - 0.8z^{-1})(1 + 0.8z^{-1})(1 - 0.9z^{-1})$$

$$= 1 - 0.9z^{-1} + 0.64z^{-2} - 0.576z^{-3}$$

$$k_3 = a_3^{(3)} = 0.576,$$



$$a_1^{(2)} = \frac{a_1^{(3)} + k_3 a_2^{(3)}}{1 - k_3^2} = 0.79518245,$$

$$a_2^{(2)} = \frac{a_2^{(3)} + k_3 a_1^{(3)}}{1 - k_3^2} = -0.18197491,$$

$$k_2 = a_2^{(2)} = -0.18197491,$$

$$a_1^{(1)} = \frac{a_1^{(2)} + k_2 a_1^{(2)}}{1 - k_2^2} = 0.67275747,$$

$$k_1 = a_1^{(1)} = 0.67275747.$$

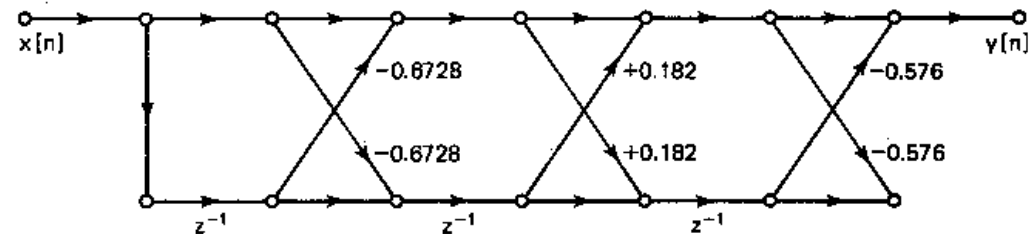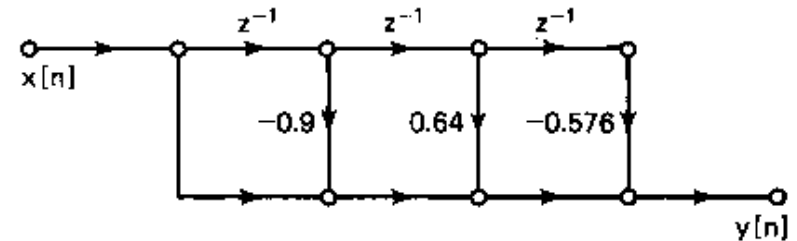

7. Lattice Structures-- All-Pole Lattice

□ A Lattice System

▣ $H(z) = 1/A(z)$

$$e_N[n] = x[n],$$


$$e_{i-1}[n] = e_i[n] + k_i \tilde{e}_{i-1}[n-1], \quad i = N, (N-1), \dots, 1,$$

$$\tilde{e}_i[n] = -k_i e_{i-1}[n] + \tilde{e}_{i-1}[n-1], \quad i = N, (N-1), \dots, 1,$$




$$y[n] = e_0[n] = \tilde{e}_0[n].$$

$$H(z) = \frac{1}{1 - 0.9z^{-1} + 0.64z^{-2} - 0.576z^{-3}}$$

▣ Example

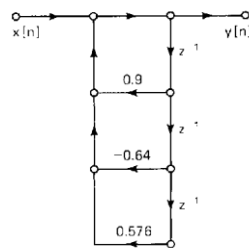

Stability Test from k_i ?

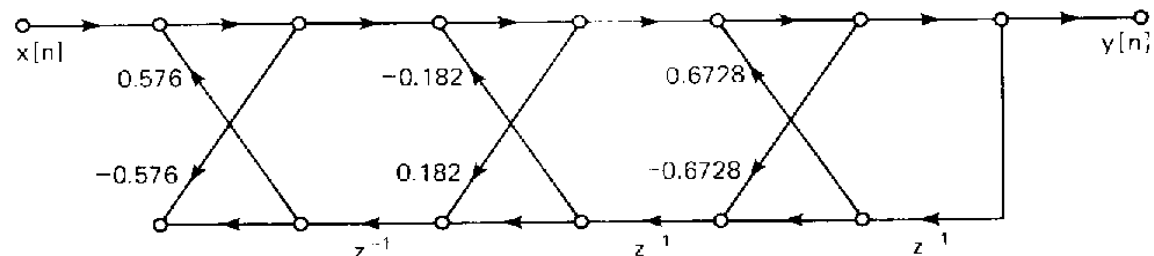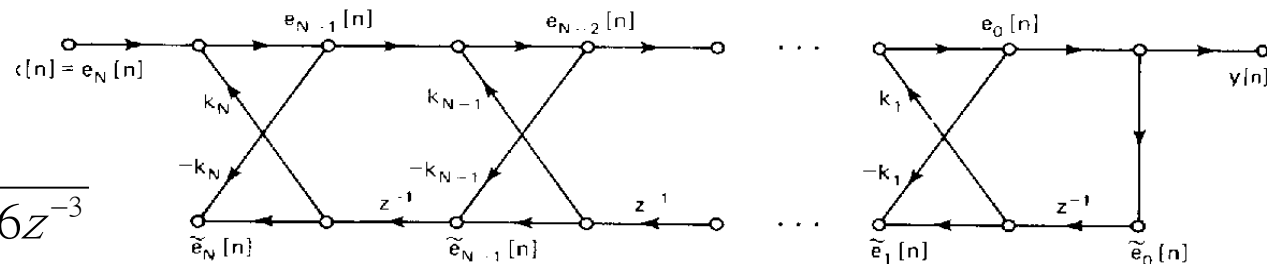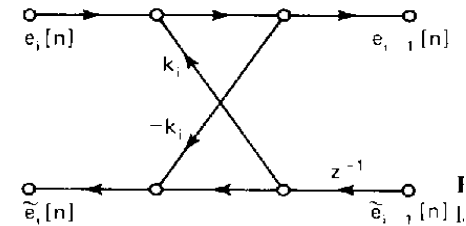

7. Lattice Structures-- Normalized Lattice

□ Equations of a Cell

$$e_N[n] = x[n],$$





$$e_{i-1}[n] = e_i[n] + k_i \tilde{e}_{i-1}[n-1],$$

$$\tilde{e}_i[n] = -k_i e_i[n] + (1 - k_i^2) \tilde{e}_{i-1}[n-1],$$

$$y[n] = e_0[n] = \tilde{e}_0[n].$$

$$\sin \theta_i = k_i$$

$$\cos \theta_i = \sqrt{1 - k_i^2}$$

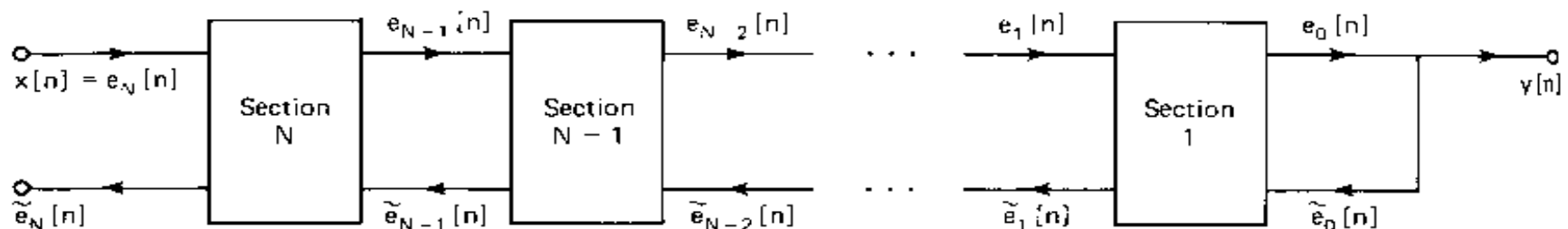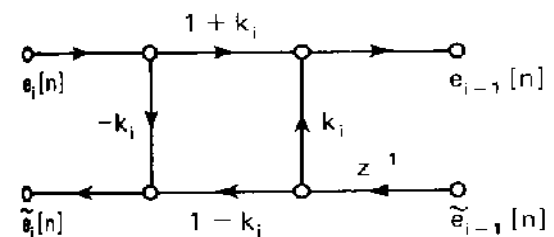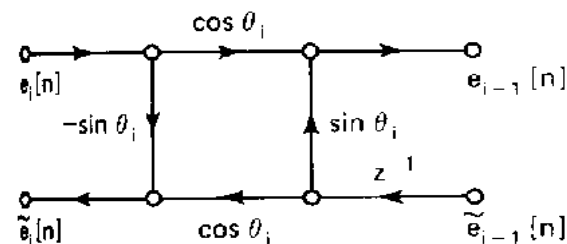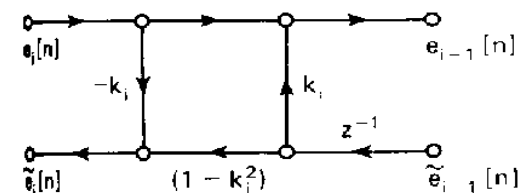

7. Lattice Structures-- Lattice Systems with Poles and Zeros




Equations

$$\tilde{E}_i(z) = z^{-i} A_i(z^{-1}) \tilde{E}_0(z) = z^{-i} A_i(z^{-1}) Y(z)$$

$$\tilde{H}_i(z) = \tilde{E}_i(z) / X(z) = \frac{z^{-i} A_i(z^{-1})}{A(z)}$$

$$H(z) = \frac{Y(z)}{X(z)} = \sum_{i=0}^N \frac{c_i z^{-i} A_i(z^{-1})}{A(z)} = \frac{B(z)}{A(z)}$$
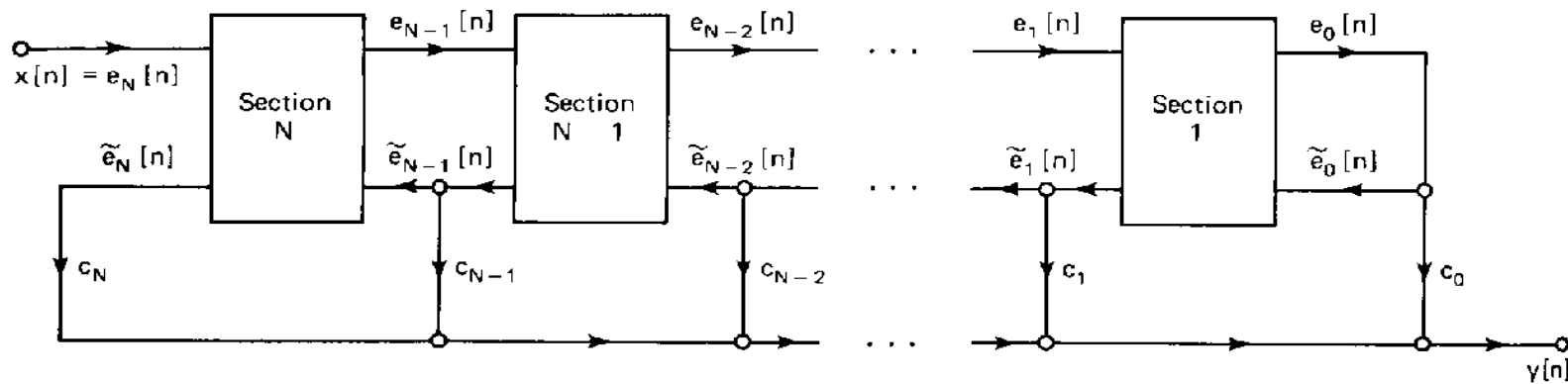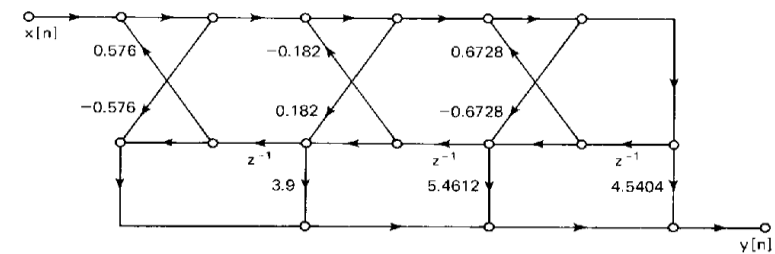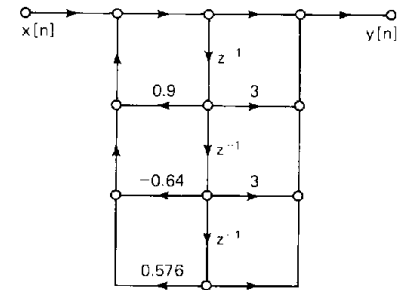
$$B(z) = \sum_{m=0}^N b_m z^{-m} \quad b_m = c_m - \sum_{i=m+1}^N c_i a_{i-m}^{(i)}$$



7. Effects of Coefficient Quantization

Specification

$$0.99 < |H(e^{j\omega})| \leq 1.01,$$


$$|H(e^{j\omega})| \leq 0.01 \text{ (i.e., } -40 \text{ dB),}$$

$$|H(e^{j\omega})| \leq 0.01 \text{ (i.e., } -40 \text{ dB),}$$


$$0.3\pi < \omega \leq 0.4\pi,$$

$$\omega \leq 0.29\pi,$$



$$0.41\pi \leq \omega \leq \pi.$$

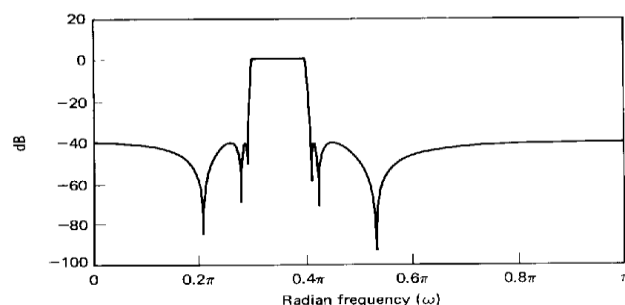


(a)

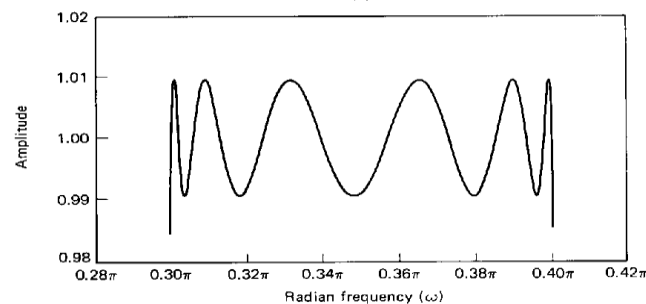


(b)

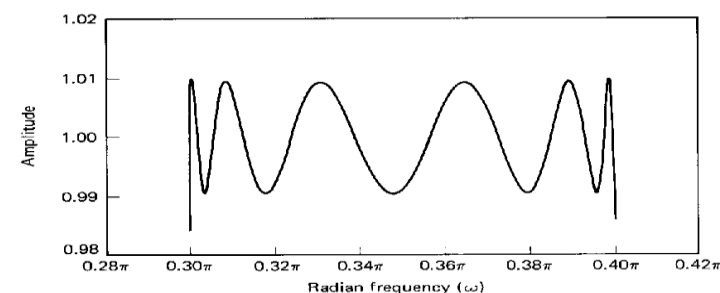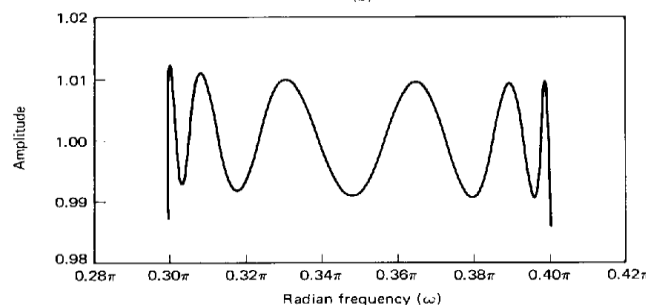

(d)

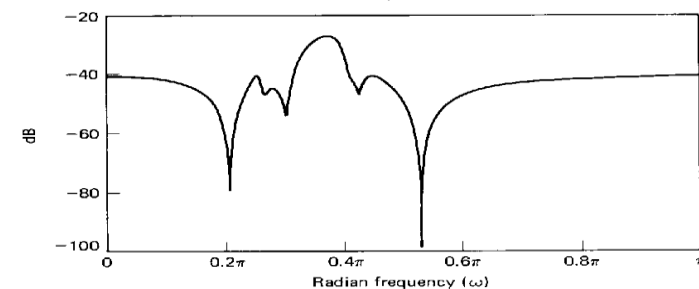

(e)

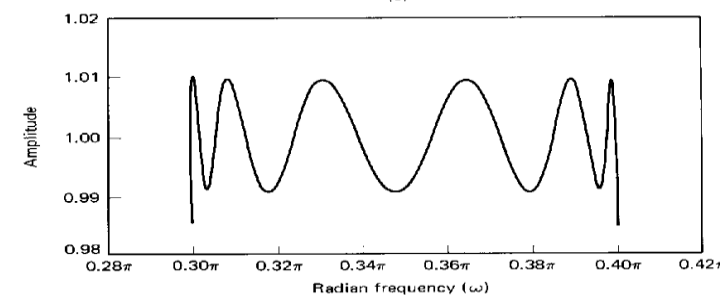

(f)

7. Effects of Coefficient Quantization

□ Analysis from Poles and Zeros

▣ The denominator

$$A(z) = 1 - \sum_{k=1}^N a_k z^{-k} = \prod_{j=1}^N (1 - z_j z^{-1})$$

▣ The error of i th pole

$$\Delta z_i = \sum_{k=1}^N \frac{\partial z_i}{\partial a_k} \Delta a_k, \quad i = 1, 2, \dots, N.$$







▣ Since that
$$\left(\frac{\partial A(z)}{\partial z_i} \right)_{z=z_i} \frac{\partial z_i}{\partial a_k} = \left(\frac{\partial A(z)}{\partial a_k} \right)_{z=z_i}.$$

▣ It follows that

$$\frac{\partial z_i}{\partial a_k} = \frac{z_i^{N-k}}{\prod_{j=1, j \neq i}^N (z_i - z_j)}$$

- **Narrow bandwidth Filters**
- **Implementation through modular structures like cascade or parallel forms**

7. Effects of Coefficient Quantization

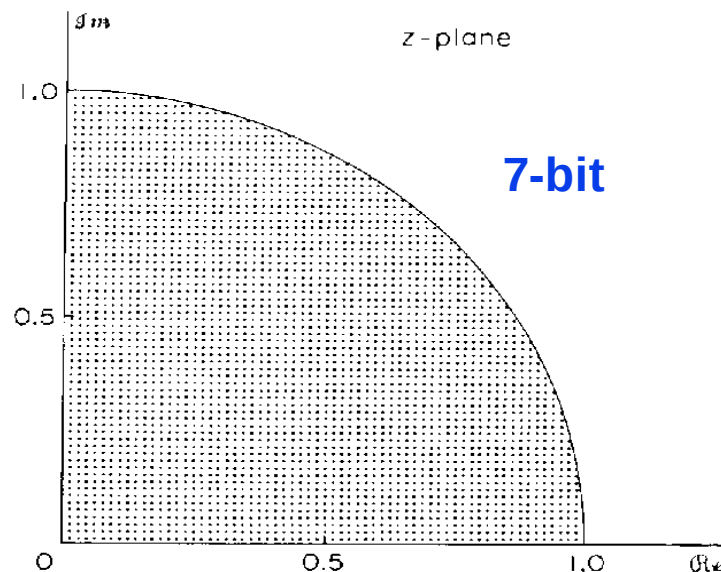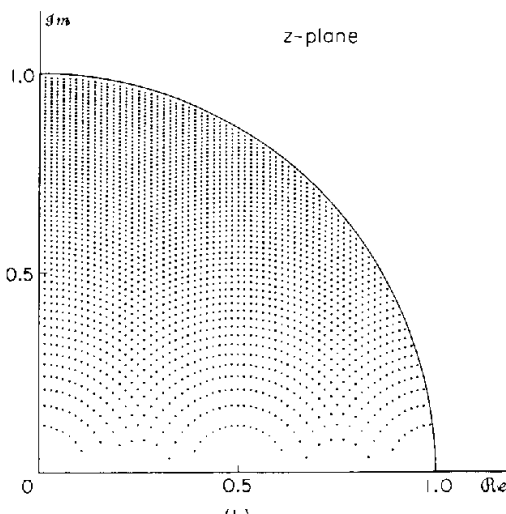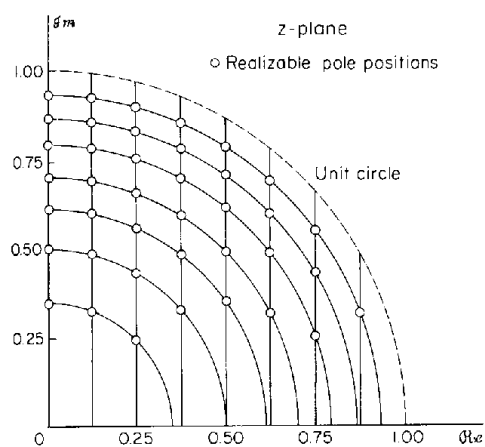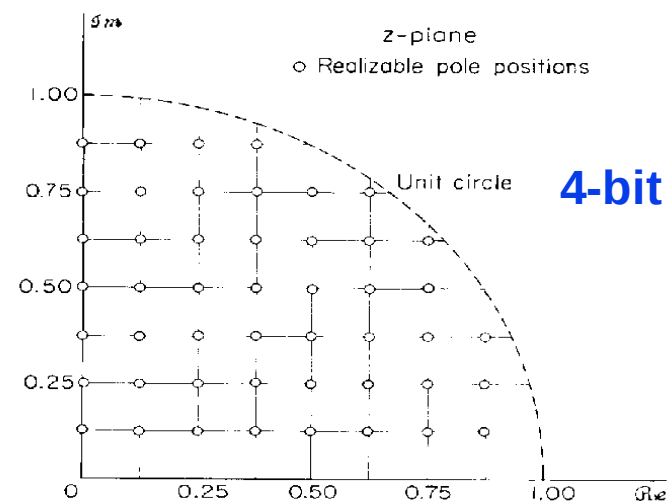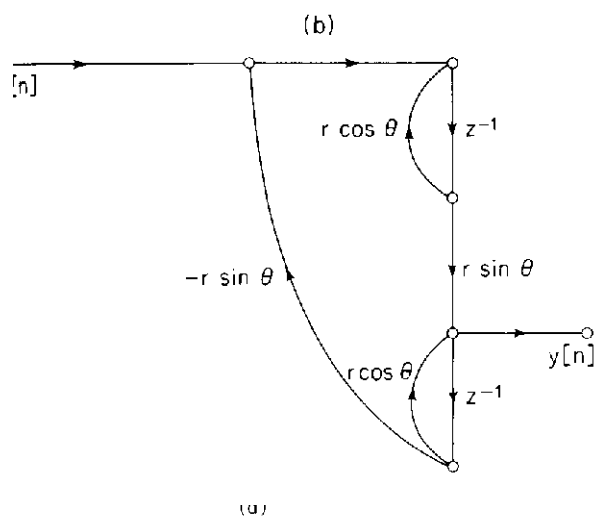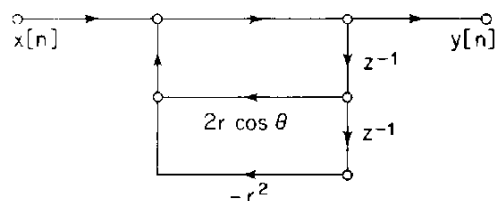

8. Effects of Round-off Noise in Digital Filters

□ IIR Structure




▣ (B+1) bit fixed point

$$y[n] = \sum_{i=1}^N a_i y[n-i] + \sum_{k=0}^M b_k x[n-k]$$

$$\hat{y}[n] = \sum_{i=1}^N Q[a_i \hat{y}[n-i]] + \sum_{k=0}^M Q[b_k x[n-k]]$$

▣ Assumption on Noise

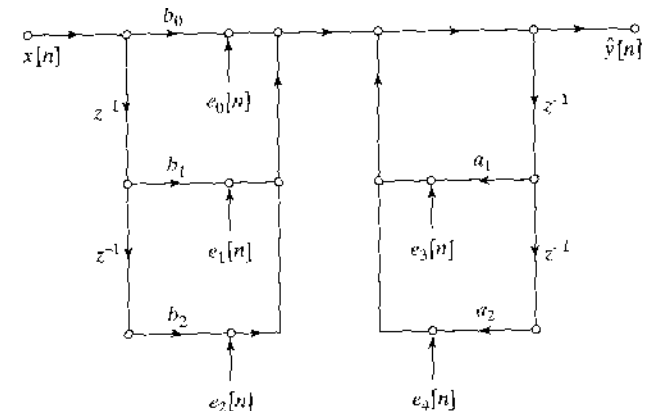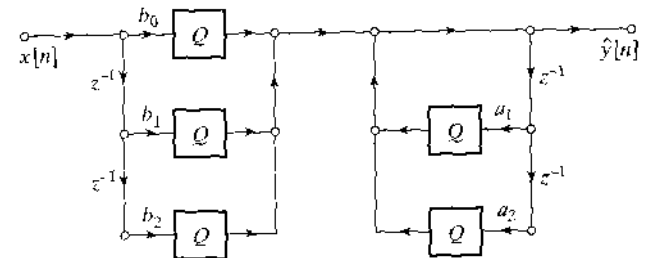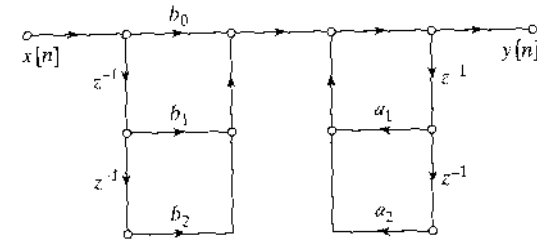- $e[n]$ is wide-sense stationary white-noise.
- A uniform distribution of amplitude.
- Noise is uncorrelated with the input.




Quantization

For $(B + 1)$ -bit quantization, we showed in Section 6.6 that, for rounding,

$$-\frac{1}{2}2^{-B} < e[n] \leq \frac{1}{2}2^{-B},$$

$$m_e = 0,$$

$$\sigma_e^2 = \frac{2^{-2B}}{12}.$$

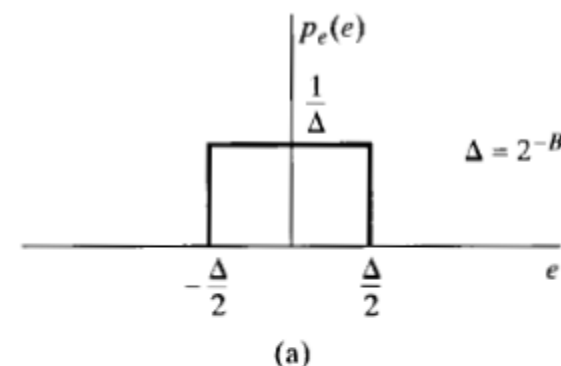


for two's-complement truncation,

$$-2^{-B} < e[n] \leq 0.$$

$$m_e = -\frac{2^{-B}}{2},$$

$$\sigma_e^2 = \frac{2^{-2B}}{12}.$$

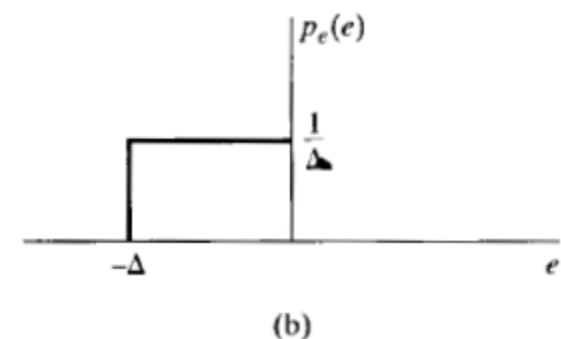

8. Effects of Round-off Noise in Digital Filters (c.1)

Quantization Errors

- For $(B+1)$ -bit quantization

$$-\frac{1}{2}2^{-B} < e[n] \leq \frac{1}{2}2^{-B}$$

- For 2's complement

$$-2^{-B} < e[n] \leq 0$$




Autocorrelation sequence

$$\phi_{ee}[n] = \sigma_e^2 \delta[n] + m_e^2.$$

Total noise

$$e[n] = e_0[n] + e_1[n] + e_2[n] + e_3[n] + e_4[n].$$
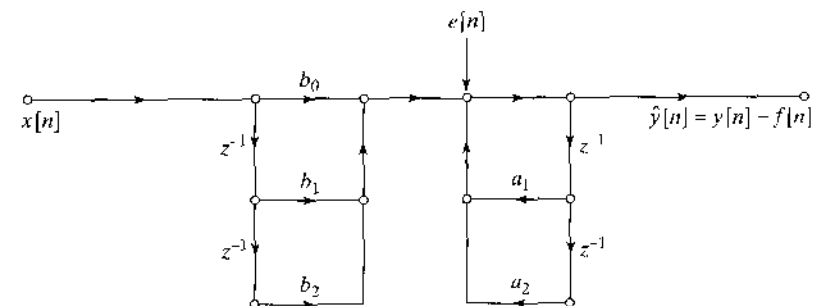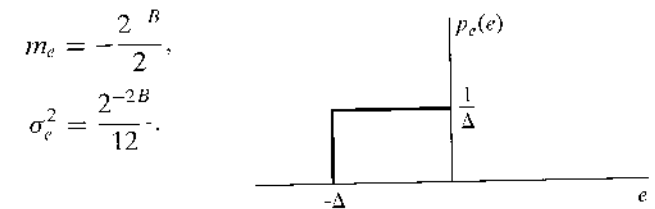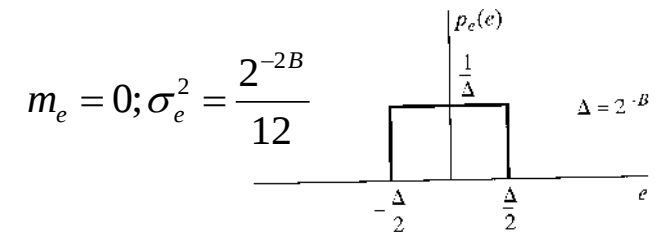
$$\sigma_e^2 = \sigma_{e_0}^2 + \sigma_{e_1}^2 + \sigma_{e_2}^2 + \sigma_{e_3}^2 + \sigma_{e_4}^2 = 5 \cdot \frac{2^{-2B}}{12},$$



8. Effects of Round-off Noise in Digital Filters (c.2)

□ General Form

$$\sigma_e^2 = (M+1+N) \frac{2^{-2B}}{12}, \quad f[n] = \sum_{k=1}^N a_k f[n-k] + e[n];$$

$$m_f = m_e \sum_{n=-\infty}^{\infty} h_{ef}[n] = m_e H_{ef}(e^{j0}).$$

$$P_{ff}(\omega) = \Phi_{ff}(e^{j\omega}) = \sigma_e^2 |H_{ef}(e^{j\omega})|^2.$$

$$\sigma_f^2 = \frac{1}{2\pi} \int_{-\pi}^{\pi} P_{ff}(\omega) d\omega = \sigma_e^2 \frac{1}{2\pi} \int_{-\pi}^{\pi} |H_{ef}(e^{j\omega})|^2 d\omega.$$

$$\sigma_f^2 = \sigma_e^2 \sum_{n=-\infty}^{\infty} |h_{ef}[n]|^2$$

Parserval's relationship.

8. Effects of Round-off Noise in Digital Filters (c.3)

□ Noise Variance



$$P_{ff}(\omega) = N \frac{2^{-2B}}{12} |H(e^{j\omega})|^2 + (M+1) \frac{2^{-2B}}{12}$$

$$\begin{aligned} \sigma_f^2 &= N \frac{2^{-2B}}{12} \frac{1}{2\pi} \int_{-\pi}^{\pi} |H(e^{j\omega})|^2 d\omega + (M+1) \frac{2^{-2B}}{12} \\ &= N \frac{2^{-2B}}{12} \sum_{n=-\infty}^{\infty} |h[n]|^2 + (M+1) \frac{2^{-2B}}{12}. \end{aligned}$$

$$\hat{y}[n] = Q \left[\sum_{k=1}^N a_k \hat{y}[n-k] + \sum_{k=0}^M b_k x[n-k] \right];$$

$$\hat{w}[n] = Q \left[\sum_{k=1}^N a_k \hat{w}[n-k] + x[n] \right]$$
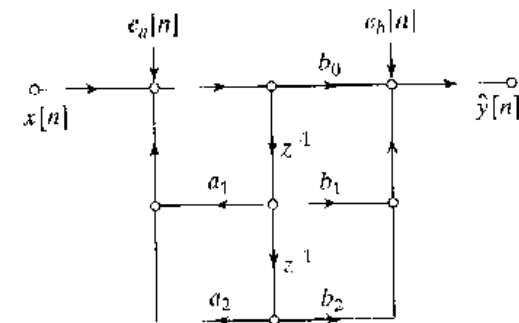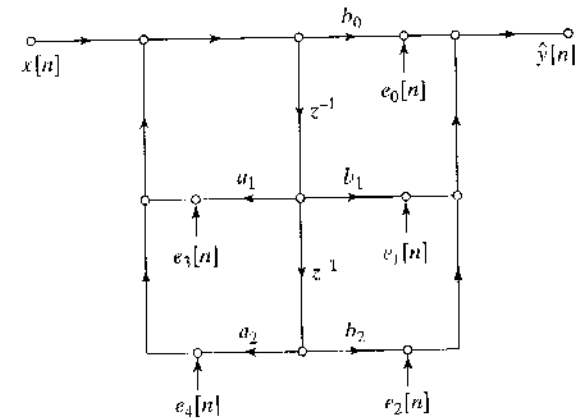
$$\hat{y}[n] = Q \left[\sum_{k=0}^M b_k \hat{w}[n-k] \right].$$



8. Effects of Round-off Noise in Digital Filters – Scaling in Fixed-Point Implementation

- The overflow concerns

$$|w_k[n]| = \left| \sum_{m=-\infty}^{\infty} x[n-m]h_k[m] \right|, \quad |w_k[n]| < 1$$

- Sufficient condition for

$$|w_k[n]| \leq x_{\max} \sum_{m=-\infty}^{\infty} |h_k[m]| \quad x_{\max} < \frac{1}{\sum_{m=-\infty}^{\infty} |h_k[m]|}$$


- Hence

$$Sx_{\max} < \frac{1}{\max_k \left[\sum_{m=-\infty}^{\infty} |h_k[m]| \right]}.$$


9. Zero-Input Limit Cycles in Fixed-Point

□ Due to Round-off and Truncation

$$y[n] = ay[n-1] + x[n], \quad |a| < 1.$$


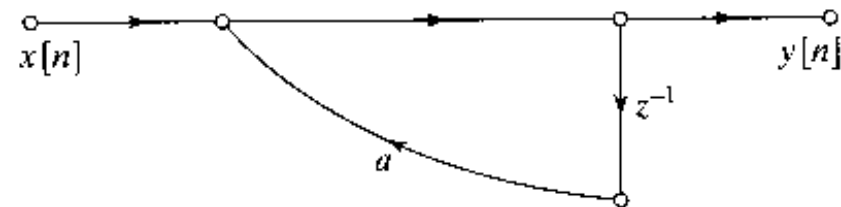


$$\hat{y}[n] = Q[ay[n-1]] + x[n],$$

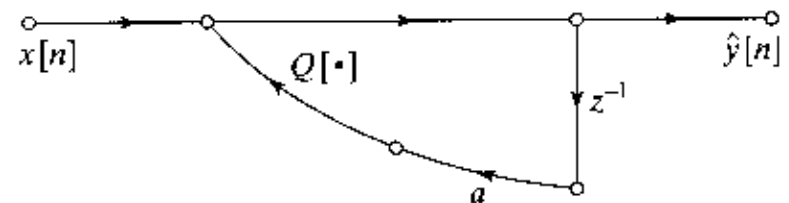

where $Q[\cdot]$ represents the rounding operation. Let us assume that $a = 1/2 = 0_2100$ and that the input is $x[n] = (7/8)\delta[n] = (0_2111)\delta[n]$. Using Eq. (6.120), we see that for $n = 0$, $\hat{y}[0] = 7/8 = 0_2111$. To obtain $\hat{y}[1]$, we multiply $\hat{y}[0]$ by a , obtaining the result $a\hat{y}[0] = 0_2011100$, a 7-bit number that must be rounded to 4 bits. This number, $7/16$, is exactly halfway between the two 4-bit quantization levels $4/8$ and $3/8$. If we choose always to round upward in such cases, then $0_2011100$ rounded to 4 bits is $0_2100 = 1/2$.

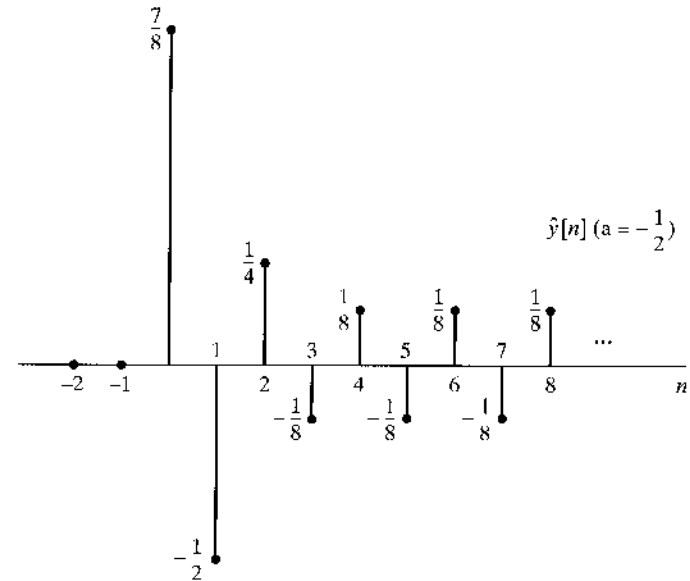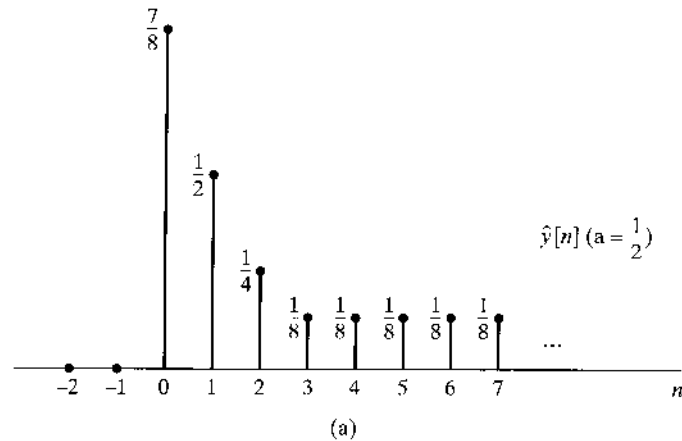9. Zero-Input Limit Cycles in Fixed-Point



Homeworks

- 6.23, 6.24d, 6.25, 6.40,
6.42, 6.45
- 2.82, 2.85, 2.90