



# Lecture 5-1: Digital System

## **CS10014 Computer Organization**

Department of Computer Science

Tsung Tai Yeh

Thursday: 1:20 pm– 3:10 pm

Classroom: EC-022



# Acknowledgements and Disclaimer

- Slides were developed in the reference with
  - CS 61C at UC Berkeley
    - <https://inst.eecs.berkeley.edu/~cs61c/sp23/>
  - CS 252 at UC Berkeley
    - <https://people.eecs.berkeley.edu/~culler/courses/cs252-s05/>
  - CSCE 513 at University of South Carolina
    - <https://passlab.github.io/CSCE513/>




# Outline

- Logic Gate
- Arithmetic Logic Unit (ALU)
- Clock Signal
- Latch
- D Flip-Flop
- Register


 
# Digital Systems


- Digital
  - All values are discrete
  - A value can be on (1) or off (0)
- Analog
  - Have a continuous range of values





# Logic Gate: AND

A	B	out
0	0	0
0	1	0
1	0	0
1	1	1

 


`out = A & B`  
          ↑  
          C syntax



# Logic Gate: OR

A	B	out
0	0	0
0	1	1
1	0	1
1	1	1

 


$$\text{out} = A \mid B$$

↑  
C syntax



# Logic Gate: XOR

A	B	out
0	0	0
0	1	1
1	0	1
1	1	0

 


$$\text{out} = A \hat{\ } B$$

↑  
C syntax



# Logic Gate: NOT

A	out
0	1
1	0

 

$$\text{out} = \sim A$$


↑  
C syntax





# Logic Gate: NAND

A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

 


$$\text{out} = \sim (A \ \& \ B)$$

C syntax



# Logic Gate: NOR

A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

 


$$\text{out} = \sim (A \mid B)$$

C syntax



# Logic Gate: XNOR

A	B	out
0	0	1
0	1	0
1	0	0
1	1	1

 


$$\text{out} = \sim (A \wedge B)$$

C syntax


 
# Connecting Logic Gate

- $\text{Out} = (A \& B) \mid C$ 
  - (A, B, and C are one bit each)





# Types of Circuit

- Combinational Logic (CL) circuits
  - Output is a function of the inputs only
  - Similar to a pure function in mathematics,  $y = f(x)$
- State Elements
  - Circuit that store information




# Outline

- Logic Gate
- **Arithmetic Logic Unit (ALU)**
- Clock Signal
- Latch
- D Flip-Flop
- Register


 
# Arithmetic Logic Unit (ALU) (1/12)

- The ALU is used to compute the result of R-type instructions (ADD, SUB, ADDI, AND, OR)




When  $S = 00$ ,  $R = A + B$   
When  $S = 01$ ,  $R = A - B$   
When  $S = 10$ ,  $R = A \& B$   
When  $S = 11$ ,  $R = A | B$


 
# Arithmetic Logic Unit (ALU) (2/12)

- The ALU is used to compute the result of R-type instructions (ADD, SUB, ADDI, AND, OR)
  - A 32-bit bitwise AND unit
  - A 32-bit bitwise OR unit
  - A 32-bit ADD/SUBTRACT unit with a control line
  - The logic to output carry
  - Overflow
  - Zero
  - Negative







# Arithmetic Logic Unit (3/12)

- Binary addition

Carry out from the  
second column /  
Carry into the third  
column

$$\begin{array}{r} 111 \\ + 101 \\ + 111 \\ \hline 100 \end{array}$$

Carry in to the  
second column





# Arithmetic Logic Unit (ALU) (4/12)

- Half adder
  - Add only two 1-bit binary numbers, sum is from 0 to 2

A	B	C <sub>o</sub>	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_o = AB$$

  



# Arithmetic Logic Unit (ALU) (5/12)

- Full adder (single bit)
  - Add three 1-bit binary numbers
  - Sum is from 0 to 3, which can be expressed with two output bits (“11”)

S is 1 when 1 or 3 of the bits are 1

$$S = A \oplus B \oplus C_i$$

A	B	C <sub>i</sub>	C <sub>o</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1





# Arithmetic Logic Unit (ALU) (6/12)

- Full adder (single bit)

$$S = A \oplus B \oplus C_i$$


$$C_o = AB + C_i (A \oplus B)$$

  



# Arithmetic Logic Unit (ALU) (7/12)


- 4-bit adder

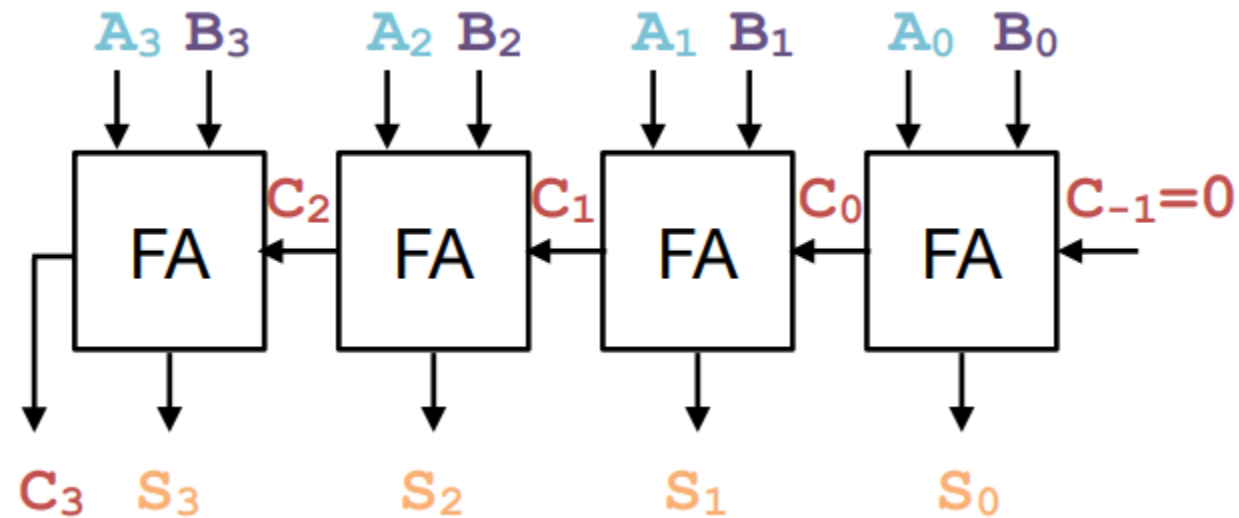


 
# Arithmetic Logic Unit (ALU) (8/12)

- Overflow
  - Indicate when the result cannot fit into n bits
- Highest adder
  - $C_{in} = \text{Carry-in} = C_1$
  - $C_{out} = \text{Carry-out} = C_2$
  - No  $C_{out}$  or  $C_{in}$  -> No overflow!
  - $C_{in}$  and  $C_{out}$  -> No overflow!
  - $C_{in}$ , but no  $C_{out}$  -> **Overflow!**
  - $C_{out}$ , but no  $C_{in}$  -> **Overflow!**




$$\text{Overflow} = c_n \text{ XOR } C_{n-1}$$


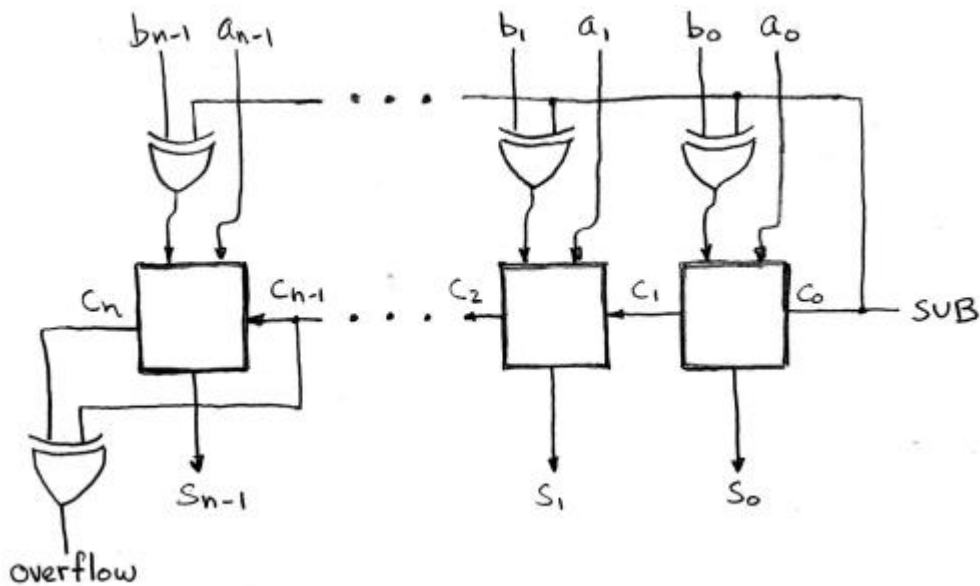
# Arithmetic Logic Unit (ALU) (9/12)

- Subtractor ( $A - B = A + (-B)$ )
  - XOR serves as conditional inverter!



A	B	out
0	0	0
0	1	1
1	0	1
1	1	0

XOR Truth Table



# Arithmetic Logic Unit (ALU) (10/12)



- Logical AND on 32-bit number

$$X = AB$$

$$A = A_{31} A_{30} A_{29} \dots A_0$$

$$B = B_{31} B_{30} B_{29} \dots B_0$$

$$X = X_{31} X_{30} X_{29} \dots X_0$$

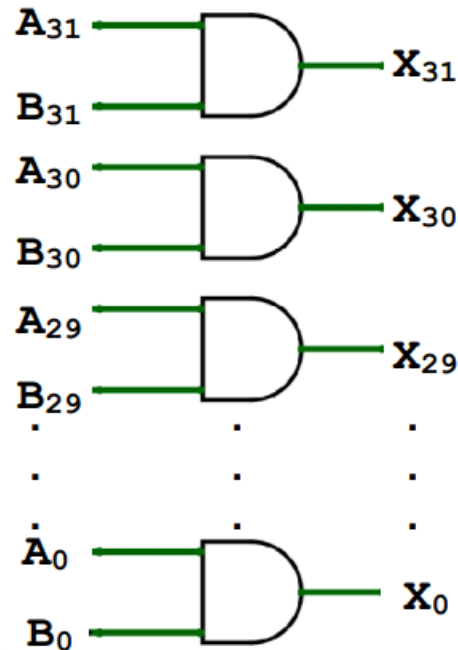 






# Arithmetic Logic Unit (ALU) (11/12)

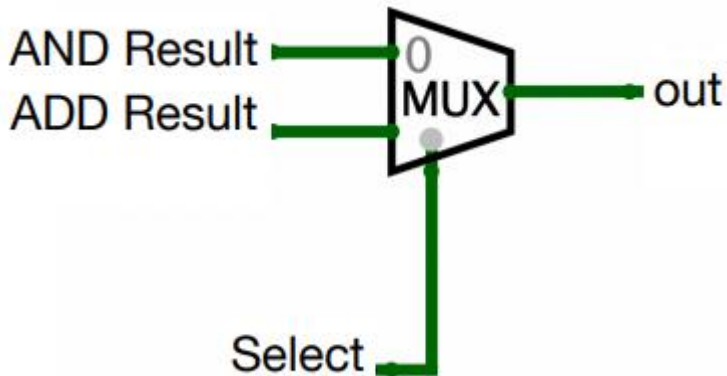- 2:1 Multiplexors
  - Selects an input to propagate to the output




If select = 0, out = AND Result  
If select = 1, out = ADD Result




# Arithmetic Logic Unit (ALU) (12/12)

 - 2:1 Multiplexors
  - Selects an input to propagate to output



$$\text{out} = A\bar{S} + BS$$

 

$$\begin{aligned} c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\ &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\ &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\ &= \bar{s}(a(1) + s((1)b) \\ &= \bar{s}a + sb \end{aligned}$$




# Outline

- Logic Gate
- Arithmetic Logic Unit (ALU)
- **Clock Signal**
- Latch
- D Flip-Flop
- Register


 
# Clock Signal (1/2)


- Clock Signal
  - Oscillates between a high and low state
  - Period = time between one rising edge to the next rising edge
  - Frequency =  $1/\text{period}$




 
# Clock Signal (2/2)

- Clock
  - The unit for frequency is Hertz (Hz)
  - E.g. clock frequency is 4 GHz
    - The clock goes through 4 billion cycles every second
    - $\text{Period} = 1/\text{frequency} = 1/4\text{GHz} = 0.25 \text{ ns}$





# Outline

- Logic Gate
- Arithmetic Logic Unit (ALU)
- Clock Signal
- **Latch**
- D Flip-Flop
- Register




# Latch (1/2)

- **Latch**

- An **asynchronous circuit** (it doesn't require a clock signal to work)
- Has two stable states, HIGH ("1"), and LOW ("0")
- Can be used for storing binary data

- **Set-Reset (S-R) latch**

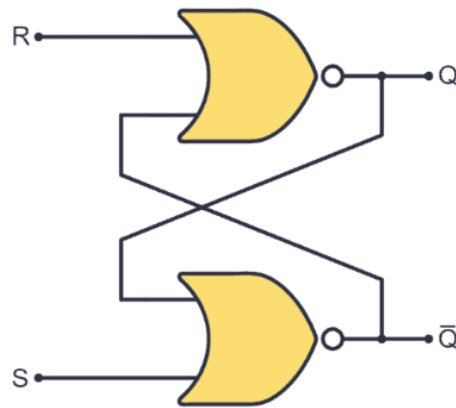- Two NOR gates with a cross-feedback loop
- The feedback path stores one bit of data as long as the circuit is powered
- Two inputs (R and S)
- Two outputs (Q and inverted Q)




S-R Latch with NOR gates


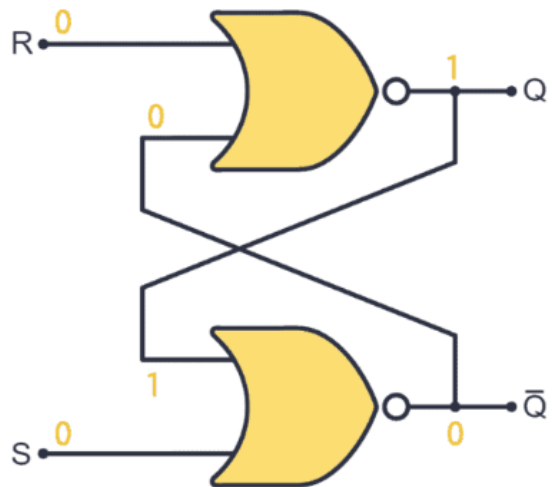
## Latch (2/2)

- Set-Reset (S-R) latch
  - NOR gate gives 1 when both of its inputs are “0”
  - When both inputs S and R are equal to “0”, the output Q remains the same as it was (saves the previous value)
  - If one input is “1”, the output will be “0”



Input S	Input R	Output Q
0	0	Previous State
0	1	0
1	0	1
1	1	0 (Invalid)





# Outline

- Logic Gate
- Arithmetic Logic Unit (ALU)
- Clock Signal
- Latch
- **D Flip-Flop**
- Register




# D Flip Flop (1/3)

- Flip Flops

- A flip-flop is a state element
- State element: A circuit component that can hold a value
- Store one bit (1 or 0) on flip flop output
- **Synchronous circuit** that need a clock signal (Clk)

- D Flip-Flop

 - The D Flip-Flop will only store a new value from the D input when the clock goes from 0 to 1 (rising edge) or 1 to 0 (falling edge)
- Commonly used as a basic building block to create counters or memory blocks such as shift register






# D Flip-Flop (2/3)

- Inputs C (clock) and D
- When C is 1, latch open, output = D
- When C is 0, latch closed, output = store value


C	D	AND
0	0	0
0	1	0
1	0	0
1	1	1

 


 
# D Flip-Flop (3/3)

- The output Q only changes to the value of the D input at the moment the clock goes from 0 to 1






# Outline

- Logic Gate
- Arithmetic Logic Unit (ALU)
- Clock Signal
- Latch
- D Flip-Flop
- **Register**


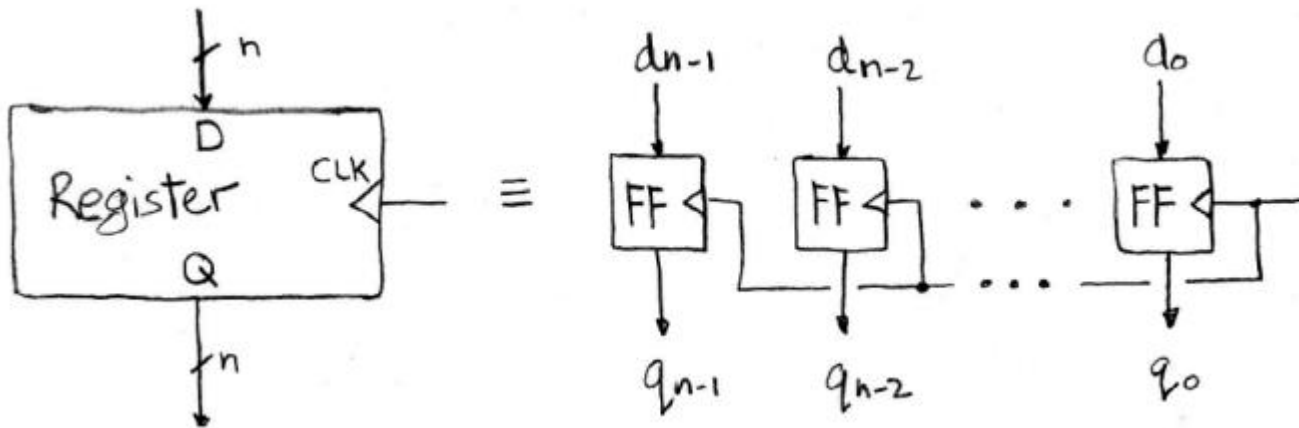
# Register

- How to store a 32-bit number?
  - Put 32 flip flops together
  - A register is a state element





# Summary

- ALU can be implemented using a mux
  - Couple with basic block elements
- N bit adder-subtractor done using N 1-bit adders with XOR gates on input
  - XOR serves as conditional inverter