



Lecture 6: RISC-V Datapath II

CS10014 Computer Organization

Department of Computer Science
Tsung Tai Yeh
Thursday: 1:20 pm– 3:10 pm
Classroom: EC-022



Acknowledgements and Disclaimer

- Slides were developed in the reference with
 - CS 61C at UC Berkeley
 - <https://inst.eecs.berkeley.edu/~cs61c/sp23/>
 - CS 252 at UC Berkeley
 - <https://people.eecs.berkeley.edu/~culler/courses/cs252-s05/>
 - CSCE 513 at University of South Carolina
 - <https://passlab.github.io/CSCE513/>



Outline

- Processor Datapath
- Immediate Generator
- Load Instruction
- Store Instruction
- Conditional Branch
- Unconditional Jump
- U-Format Instruction




Processor Datapath (1/3)

- **Datapath**

- Elements/wires that process data and addresses in the CPU

- Registers,
ALU,
MUX,
Memories

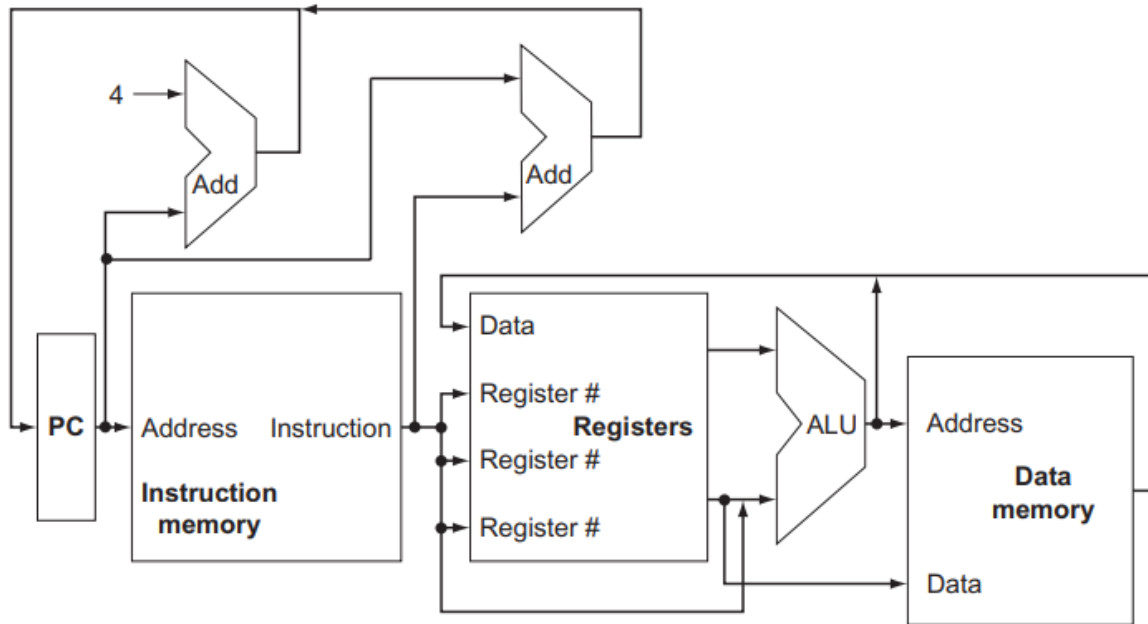




Processor Datapath (2/3)

Edge-triggered write.

If RegWEn=1, RegFile updated with input to dataW on the next rising-clock edge.

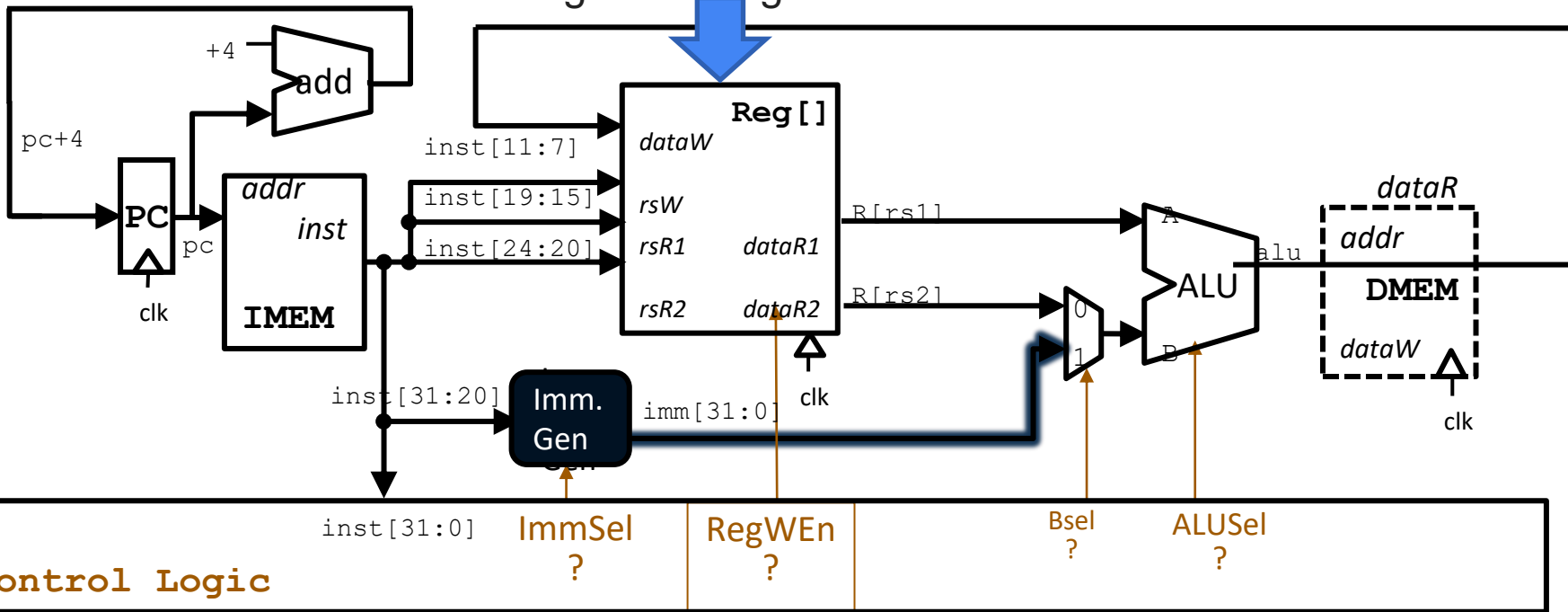Bold black wires carry data.
Thin orange wires are control logic.





Processor Datapath (3/3)


- Instruction Fetch

0x0FFE1230: add x6, x12, x13

0x0FFE1234: lw x6, 24(x12)

0x0FFE1238: sw x13, 24(x12)

0x0FFE123C: beq x12, x13, offset

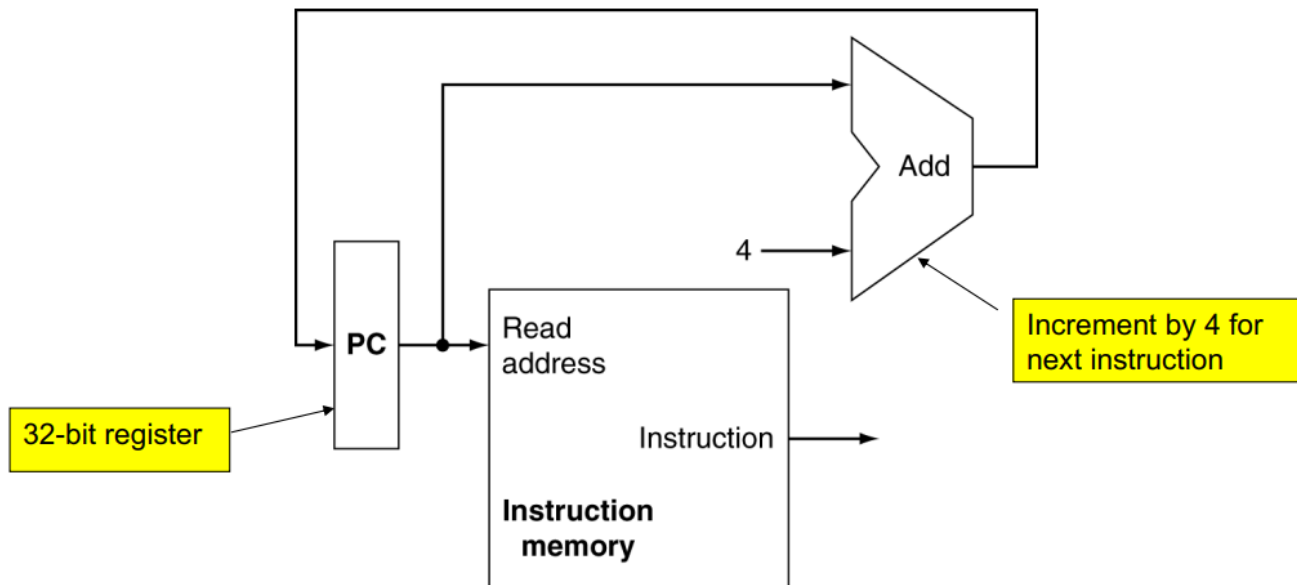



Outline


- Processor Datapath
- **Immediate Generator**
- Load Instruction
- Store Instruction
- Conditional Branch
- Unconditional Jump
- U-Format Instruction



Immediate Gen.(1/4)


- **Immediate Generator**

 - Generate 32 or 64-bit immediate value (depending on whether we design 32-bit or 64-bit machine) from an instruction word
- Select the 12-bit from the instruction word and sign-extended to 32 or 64-bit
- Used for I, S, and SB-format (I-format ALU, load, store, and beq)






Immediate Gen.(2/4)

 


Instruction *inst*[31:0]

	31	30		25	24		20	19		15	14	12	11		7	6		0
I-Type	imm[11 10:5]					imm[4:0]			rs1		funct3		rd		I-OPCODE			
S-Type	imm[11 10:5]					rs2			rs1		funct3		imm[4:0]		S-OPCODE			


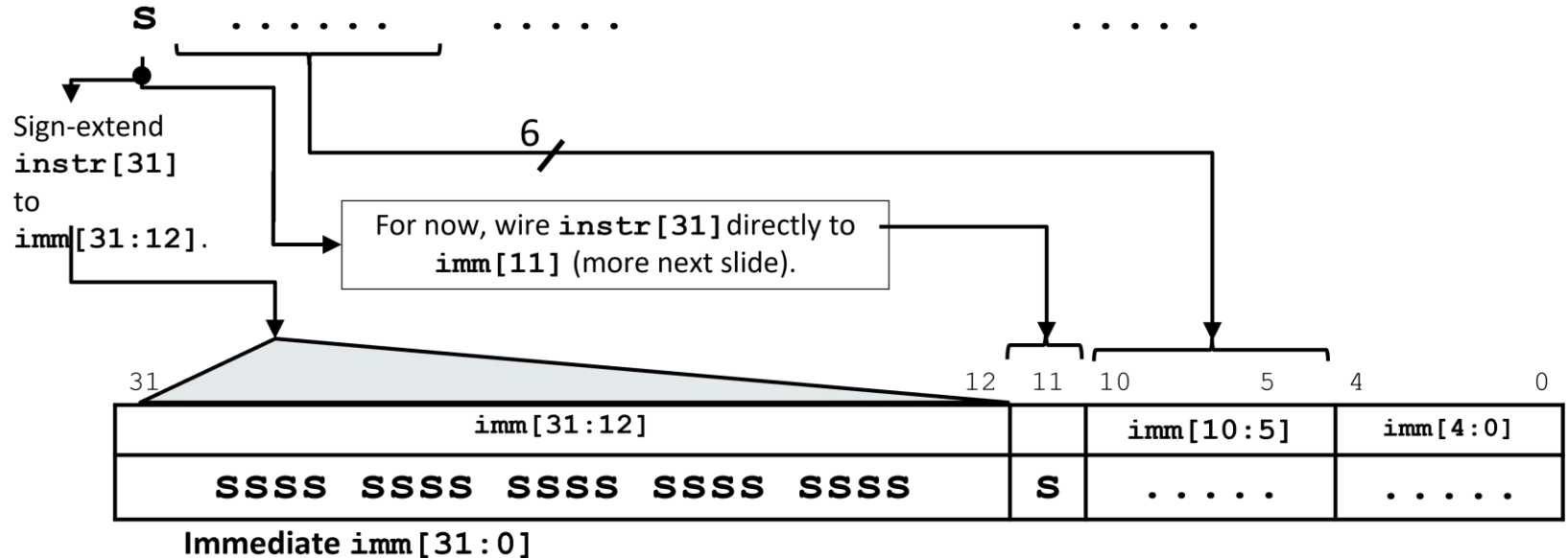




Immediate Gen.(3/4)

 


Instruction $inst[31:0]$

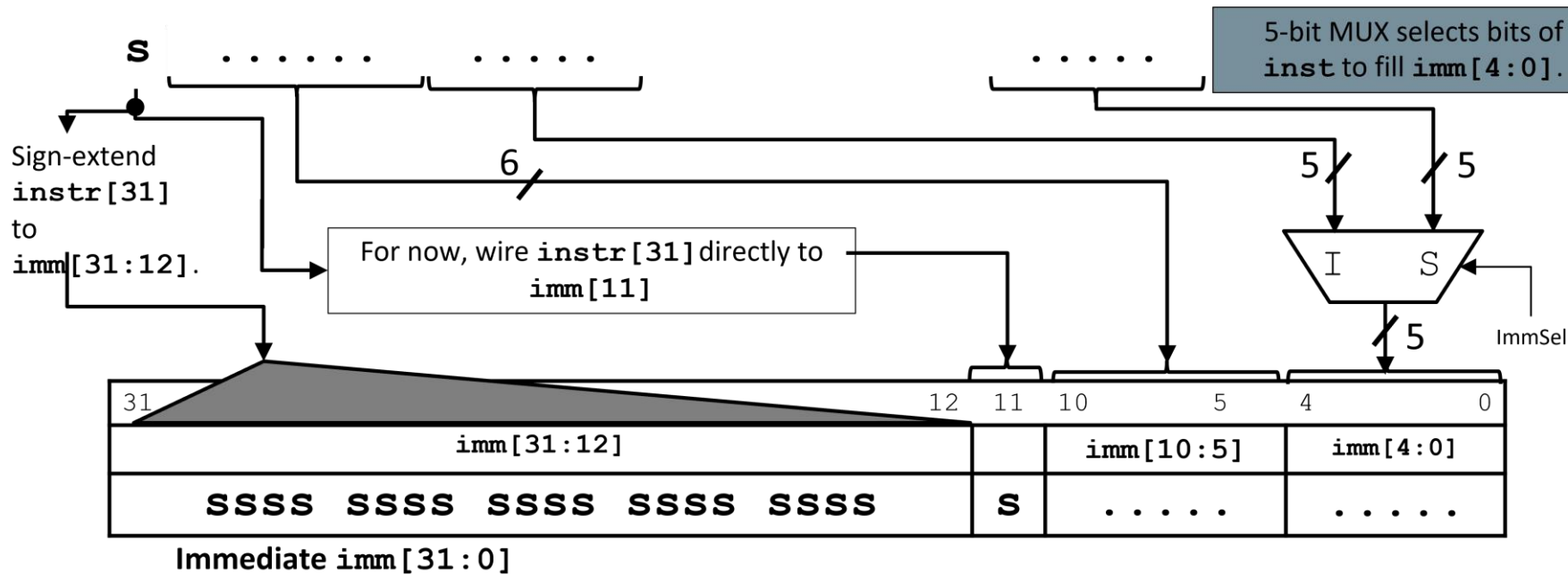 




Immediate Gen.(4/4)

 

Instruction inst[31:0]

 

instr[31] is always the sign bit.

MUX for imm[11]:

- S: instr[31]
- B: instr[7]

MUX for imm[0]:

- S: instr[7]
- B: 0 (implicit 0;



Immediate imm[31:0]



Outline


- Processor Datapath
- Immediate Generator
- **Load Instruction**
- Store Instruction
- Conditional Branch
- Unconditional Jump
- U-Format Instruction



Load Instruction (1/4)

- **I-format: lw x14, 8(x2)**
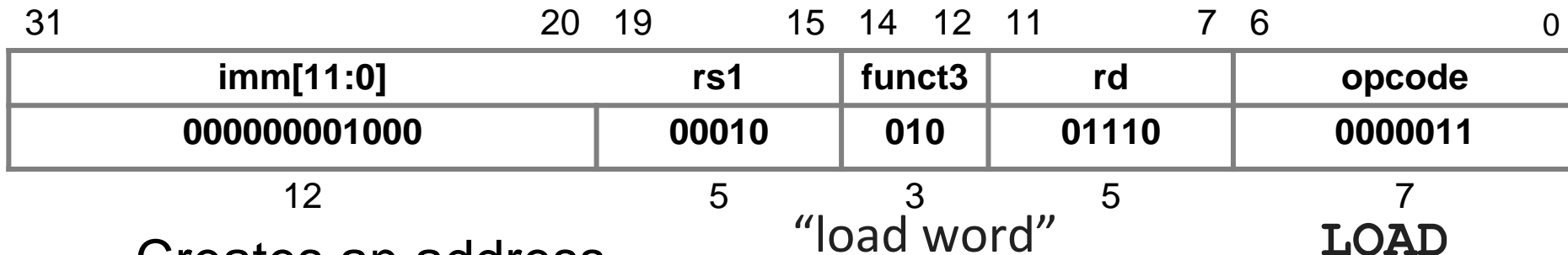
$$\text{addr} = (\text{Base register } rs1) + (\text{sign-extended } imm \text{ offset})$$




- Creates an address
- State element access includes a memory read!
 - DMEM (read word at address addr)
 - RegFile Reg[rs1] # read; Reg[rd] # write
 - PC PC = PC + 4



If load instruction, save **mem.**
Otherwise, save **alu.**

Load Instruction (2/4)

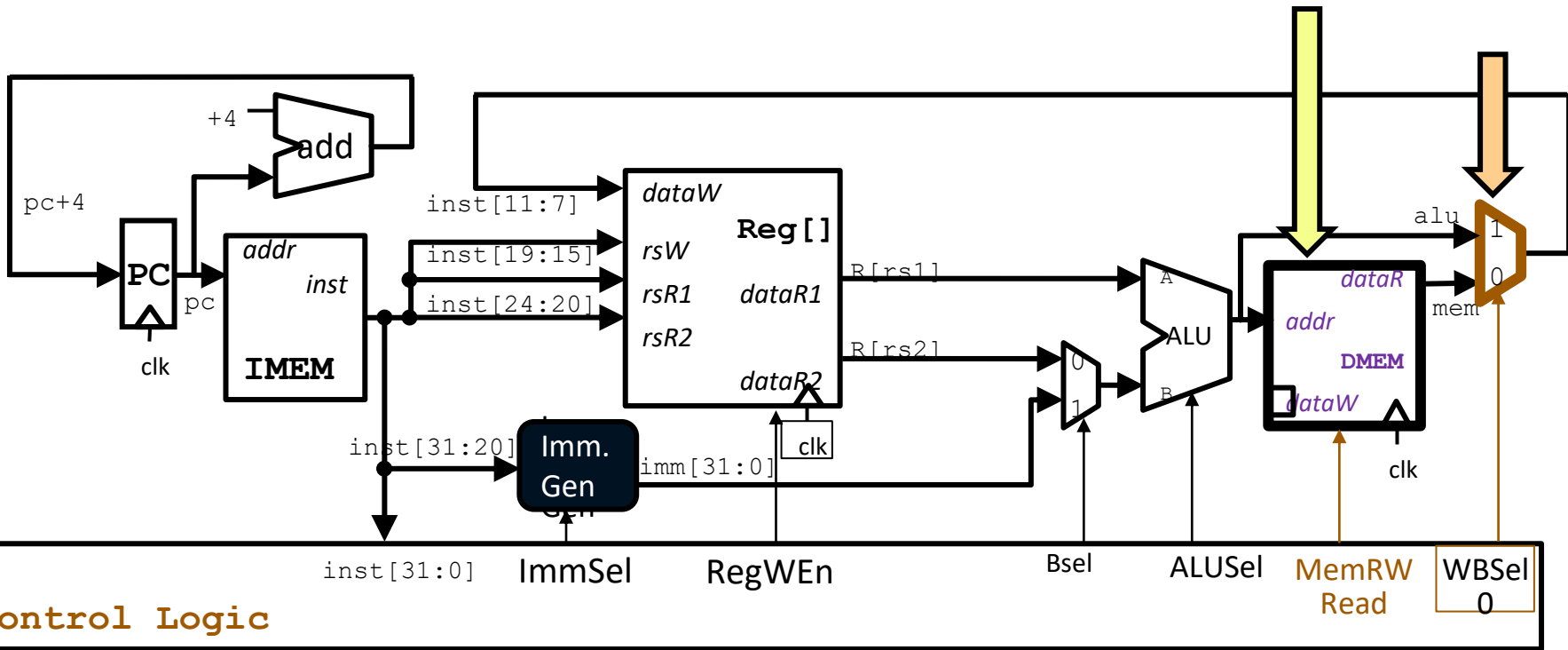Read memory at address
 $alu = R[rs1] + imm.$





Load Instruction (3/4)


Increment PC to next instruction.

Immediate Generation Block builds a 32-bit immediate **imm**.

ALU computes address **alu** = $R[rs1] + imm$.

Read memory at address **alu**.

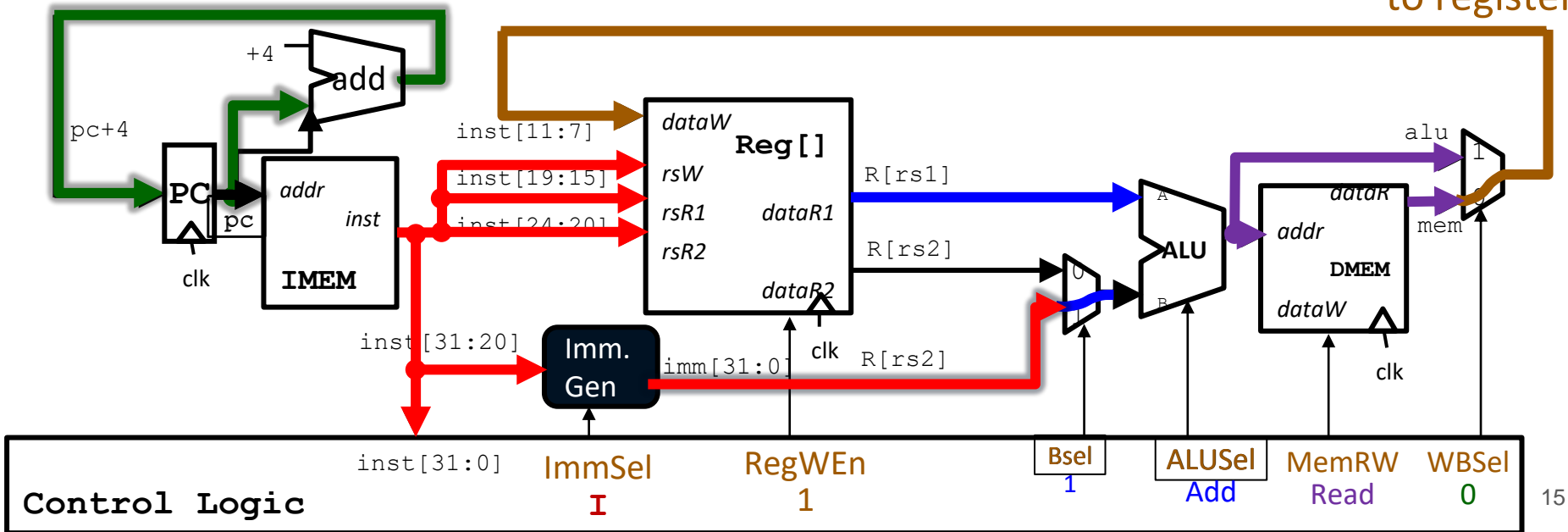Write loaded memory value **mem** to register.





Load Instruction (4/4)

- **RV32I can load different width**

- To support narrow loads (lb, lh, lbu, lhu)
- Load 32-bit word from memory
- Add additional logic to extract correct byte or halfword
- Sign- or zero-extend result to 32 bits to write into RegFile

		funct3		opcode	
imm[11:0]	rs1	000	rd	0000011	lb
imm[11:0]	rs1	001	rd	0000011	lh
imm[11:0]	rs1	010	rd	0000011	lw
imm[11:0]	rs1	100	rd	0000011	lbu
imm[11:0]	rs1	101	rd	0000011	lhu



Outline

- Processor Datapath
- Immediate Generator
- Load Instruction
- **Store Instruction**
- Conditional Branch
- Unconditional Jump
- U-Format Instruction




Store Instruction (1/4)

- **S-format: sw x14, 36(x2)**

31	25	24	20	19	15	14	12	11	7	6	0
imm[11:5]			rs2		rs1		funct3		imm[4:0]		opcode
0000001			01110		00010		010		00100		0100011



- **New Immeidate Format:**

 

- $\text{addr} = (\text{Base register rs1}) + (\text{sign-extended } \text{imm} \text{ offset})$

- **State Elements Accessed**

- DMEM (write R[rs2] to word at address addr)
- RegFile R[rs1] (base address), R[rs2] (value to store)
- PC PC = PC + 4




Store Instruction (2/4)

Update Blocks
for sw

Control ImmSel selects how to
generate immediate type: I, S.

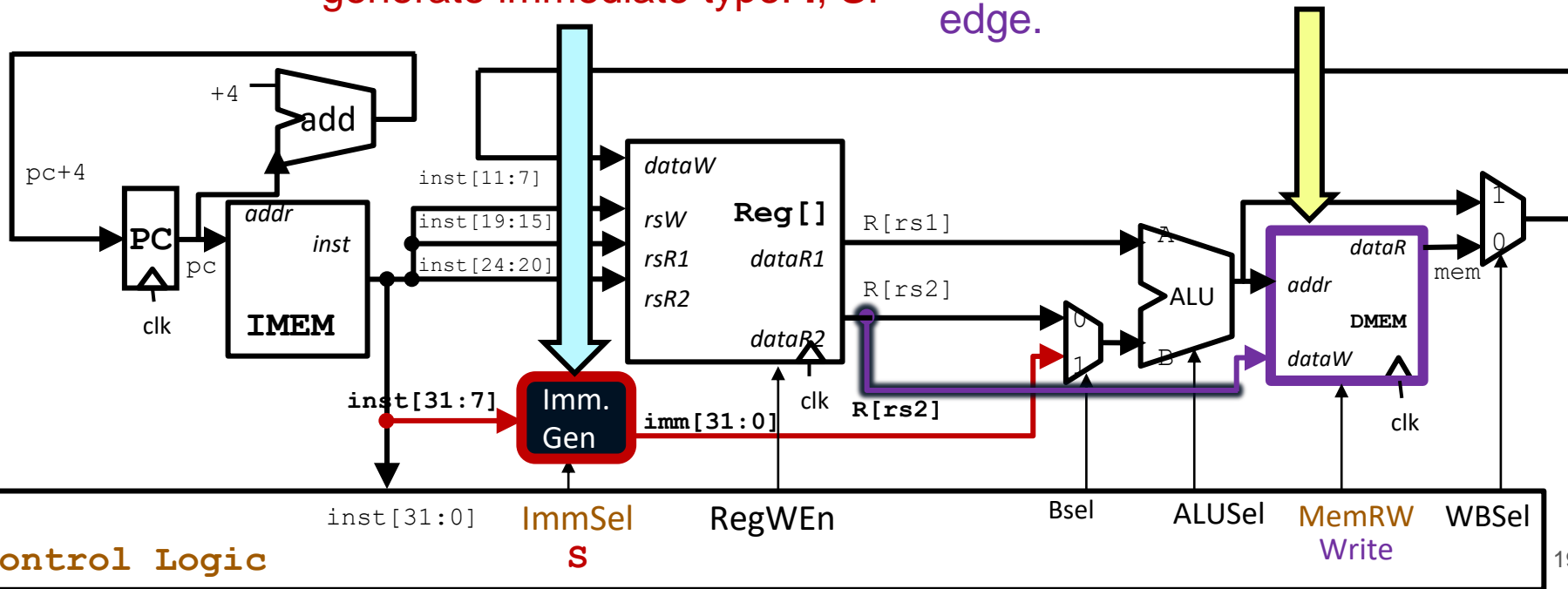Control MemRW=Write saves rs2
to memory on the next rising clock
edge.






Store Instruction (3/4)

How to set sw control lines?

	RegWEn	Bsel	WBSel
A.	Read(0)	0	0
B.	0	0	1
C.	0	1	0
D.	0	1	1
E.	Write(1)	0	0
F.	1	0	1
G.	1	1	0
H.	1	1	1

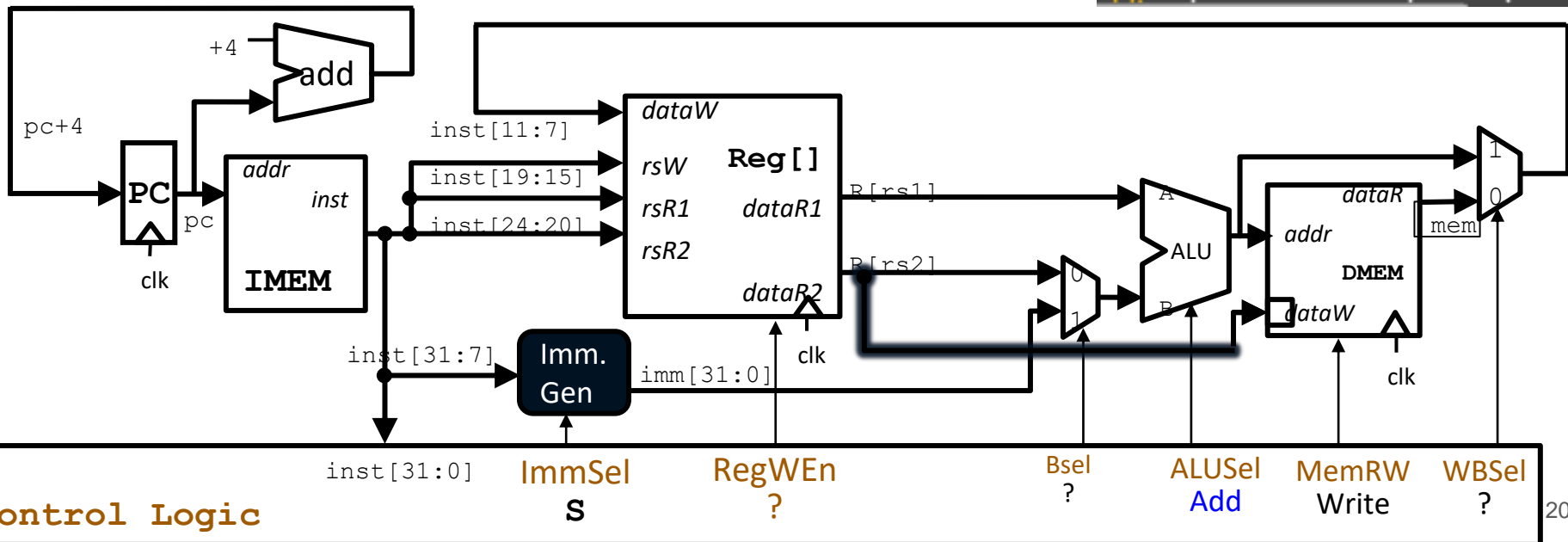



Store Instruction (4/4)

	RegWEn	Bsel	WBSel
C.	0	1	0
D.	0	1	1


Increment PC to next instruction.

Build **imm** from S-type instruction.

ALU computes address $alu = R[rs1] + imm$.

Write memory at address **alu**.

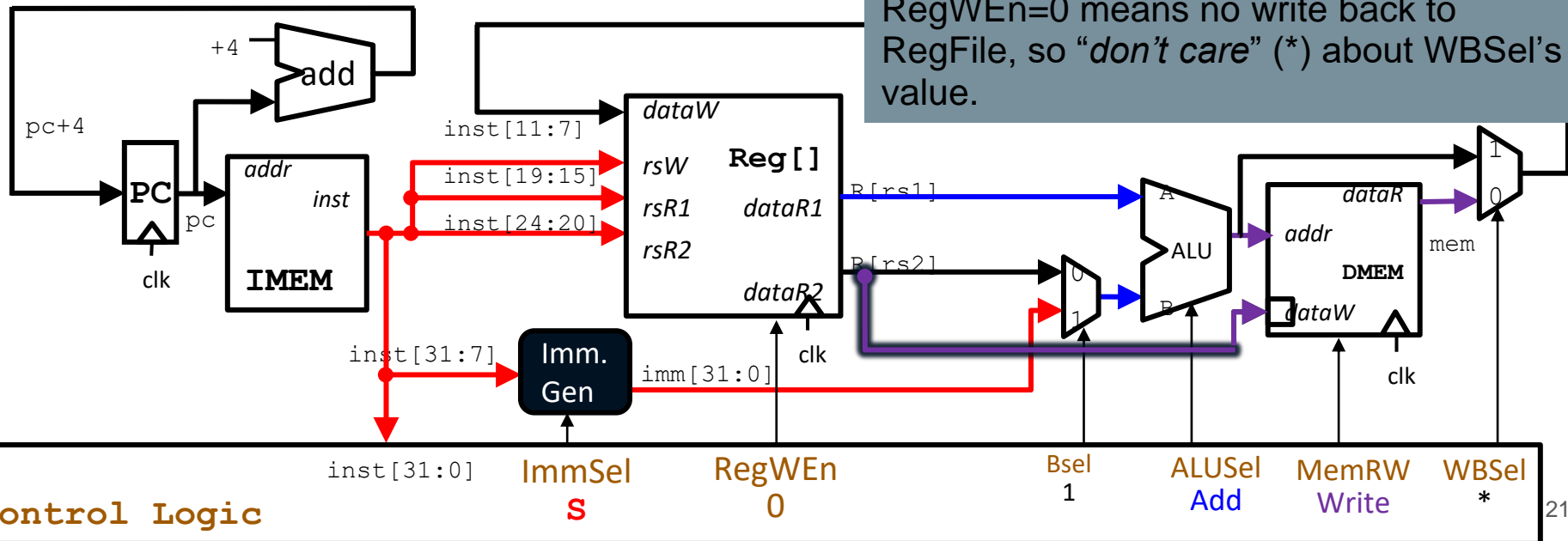RegWEn=0 means no write back to RegFile, so "don't care" (*) about WBSel's value.





Outline


- Processor Datapath
- Immediate Generator
- Load Instruction
- Store Instruction
- **Conditional Branch**
- Unconditional Jump
- U-Format Instruction



Conditional Branch (1/6)

- **SB-format: opcode rs1, rs2, Label(simm13)**

- BEQ/BNE/BLT/BLTU/BGE/BGEU

 

- **PC state element now conditionally changes**


- RegFile R[rs1] , R[rs2] (read only, for branch comparison)
- PC PC = PC + imm (if branch taken)
 - PC = PC + 4 (otherwise, not taken)



Conditional Branch (2/6)

Update PC based on
branch result.

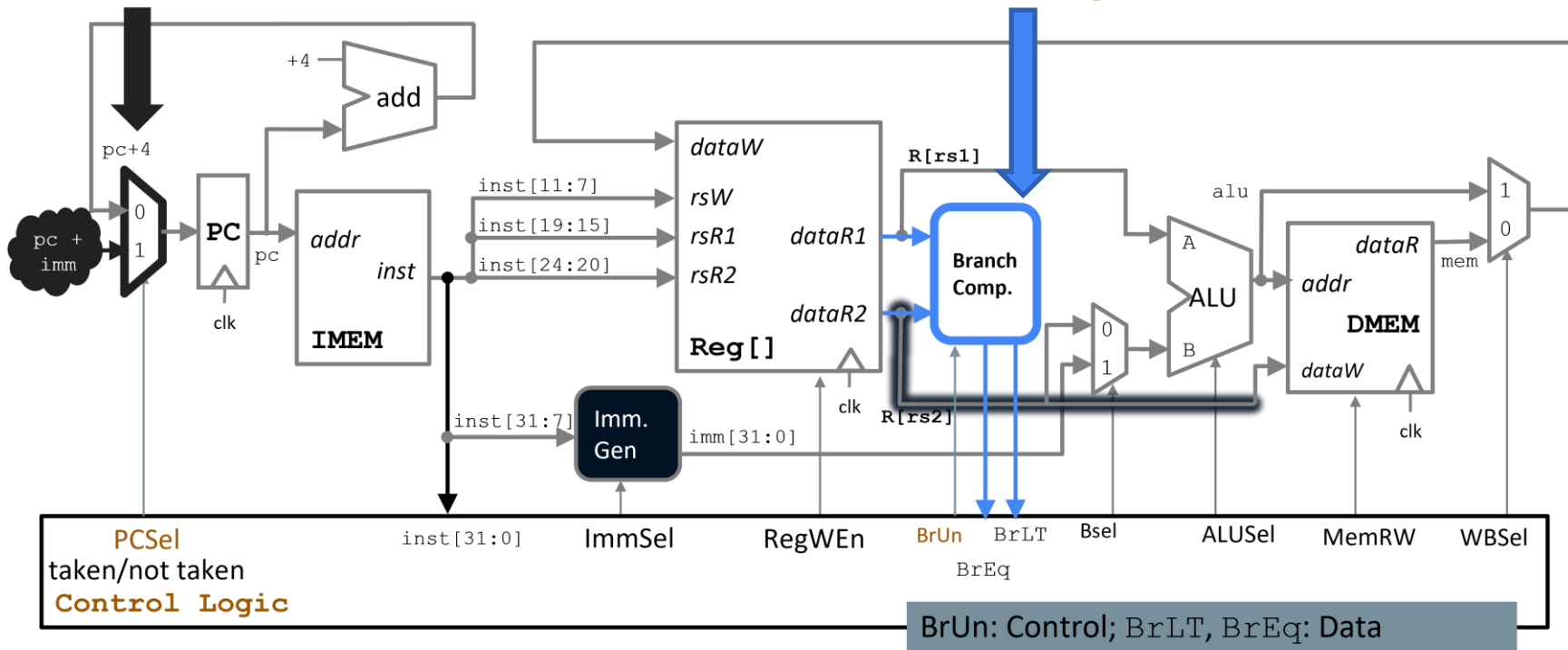Compare $R[rs1]$, $R[rs2]$,
feed result to **Control Logic**.





Conditional Branch (3/6)


- **The branch comparator is a combinational logic block**

Input:

1. Two data busses A and B (datapath $R[rs1]$ and $R[rs2]$)
2. **BrUn** (“Branch Unsigned”) control bit

Output:

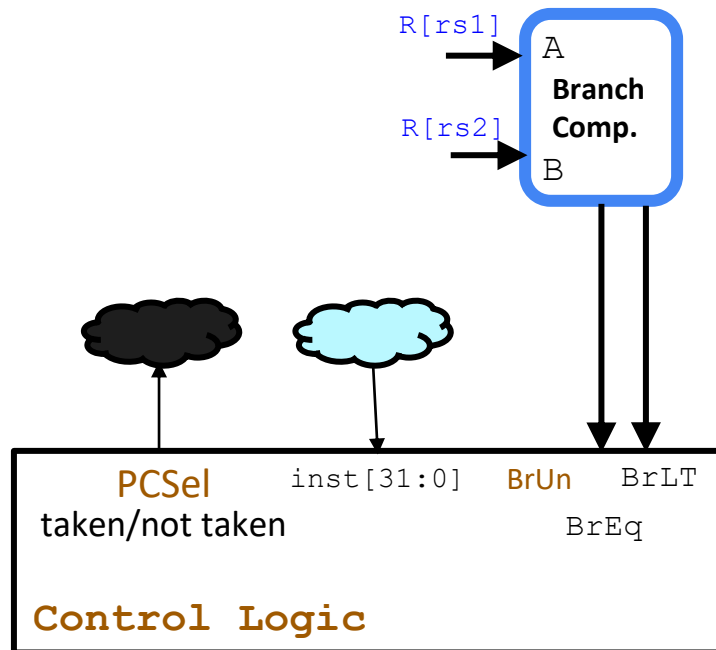1. BrEq flag: 1 if $A == B$
2. BrLT flag: 1 if $A < B$






Conditional Branch (4/6)

- **Control Logic**

- Set **BrUn** based on current instruction $inst[31:0]$
- Set **PCSel** based on branch flags **BrLT**, **BrEq**

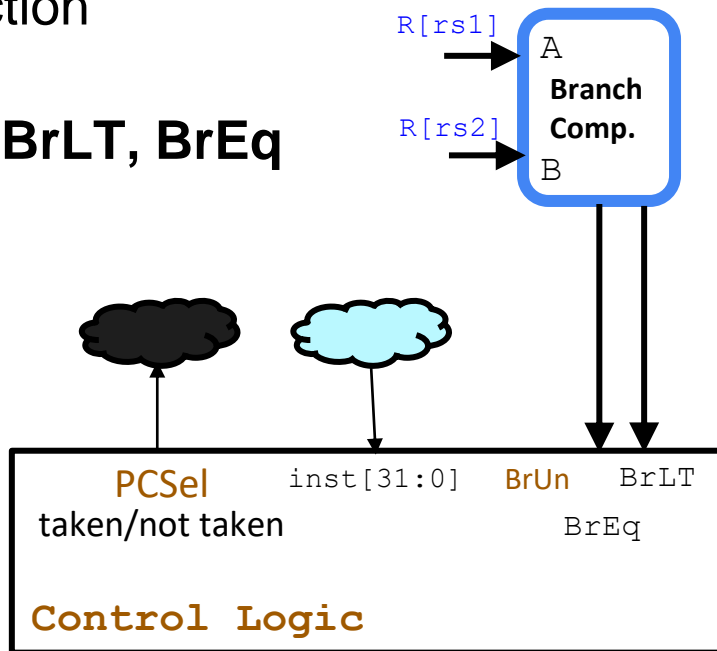- **Examples**


- **blt:**
 - If $BrLT=1$ and $BrEq=0$, then $PCSel=taken$
- **bge:** $(A \geq B) = \overline{A < B}$
 - If $BrLT=0$, then $PCSel=taken$





Conditional Branch (5/6)

$$\text{alu} = \text{PC} + \text{imm}$$

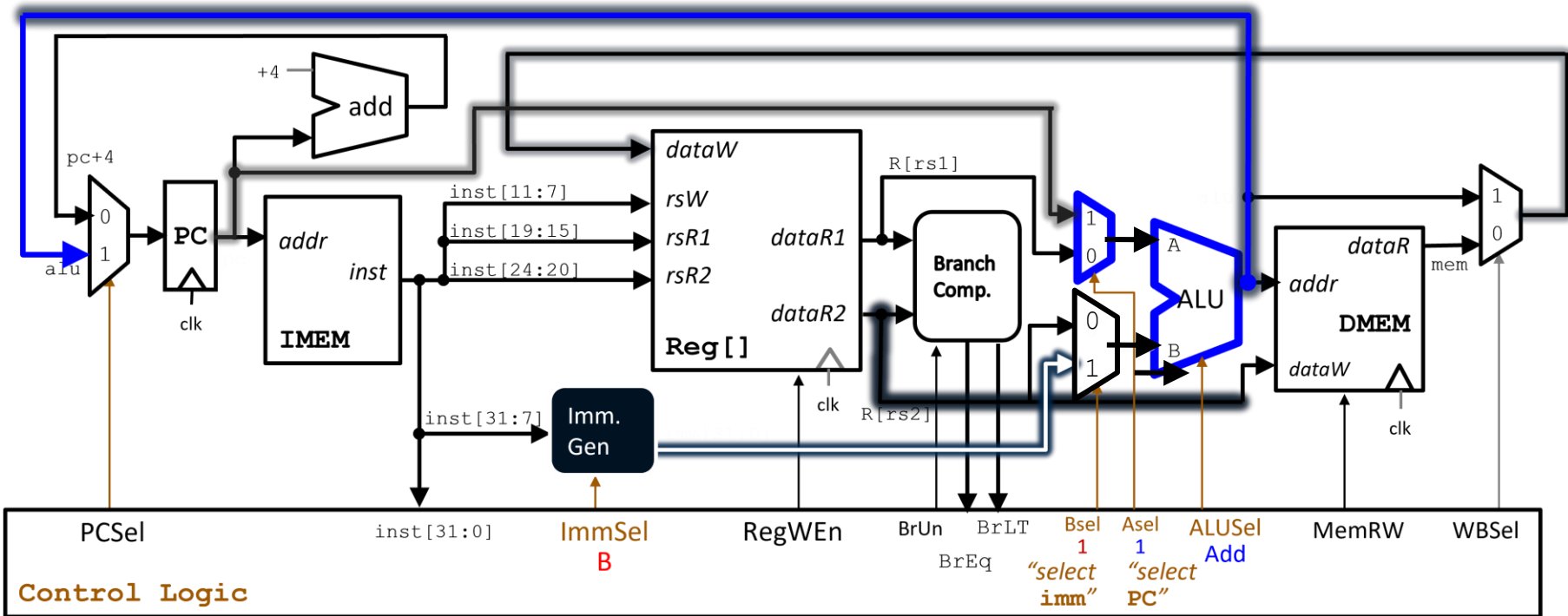



Conditional Branch (6/6)


If PCSel=taken, update PC to ALU output. Else, update to next instruction **PC + 4**.

Build **imm** from B-type instruction.

Compute branch; feed to **Control**.
Compute **PC + imm**.

Don't write to memory.

Don't write to registers.

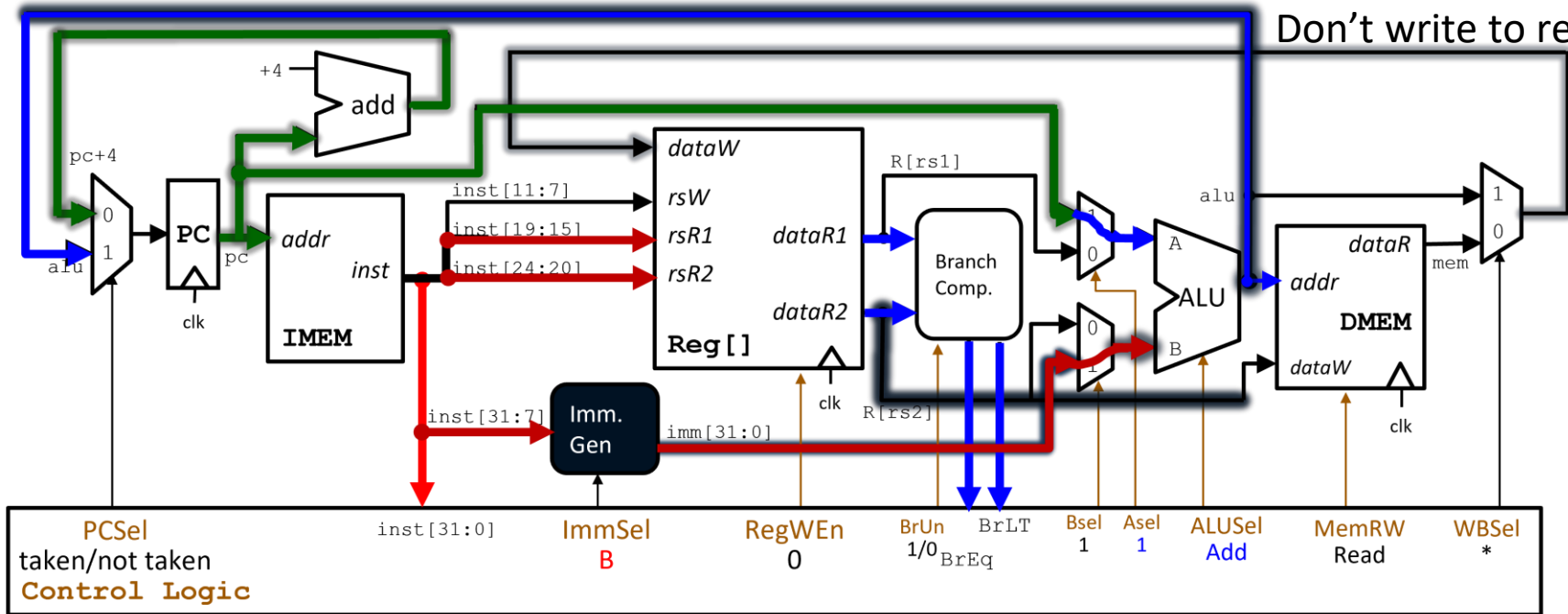




Outline

- Processor Datapath
- Immediate Generator
- Load Instruction
- Store Instruction
- Conditional Branch
- **Unconditional Jump**
- U-Format Instruction



Unconditional Jump (1/5)

- **UJ-Format: jal rd, Label (simm21)**

 

- **State Elements updated**


- PC $PC = PC + imm$ (unconditional PC-relative jump)
- RegFile $rd = PC + 4$ (save return address to RegFile destination register)



Unconditional Jump (2/5)

Immediate Generation Block
needs to support J-Types: 20-
bit \rightarrow byte offset.

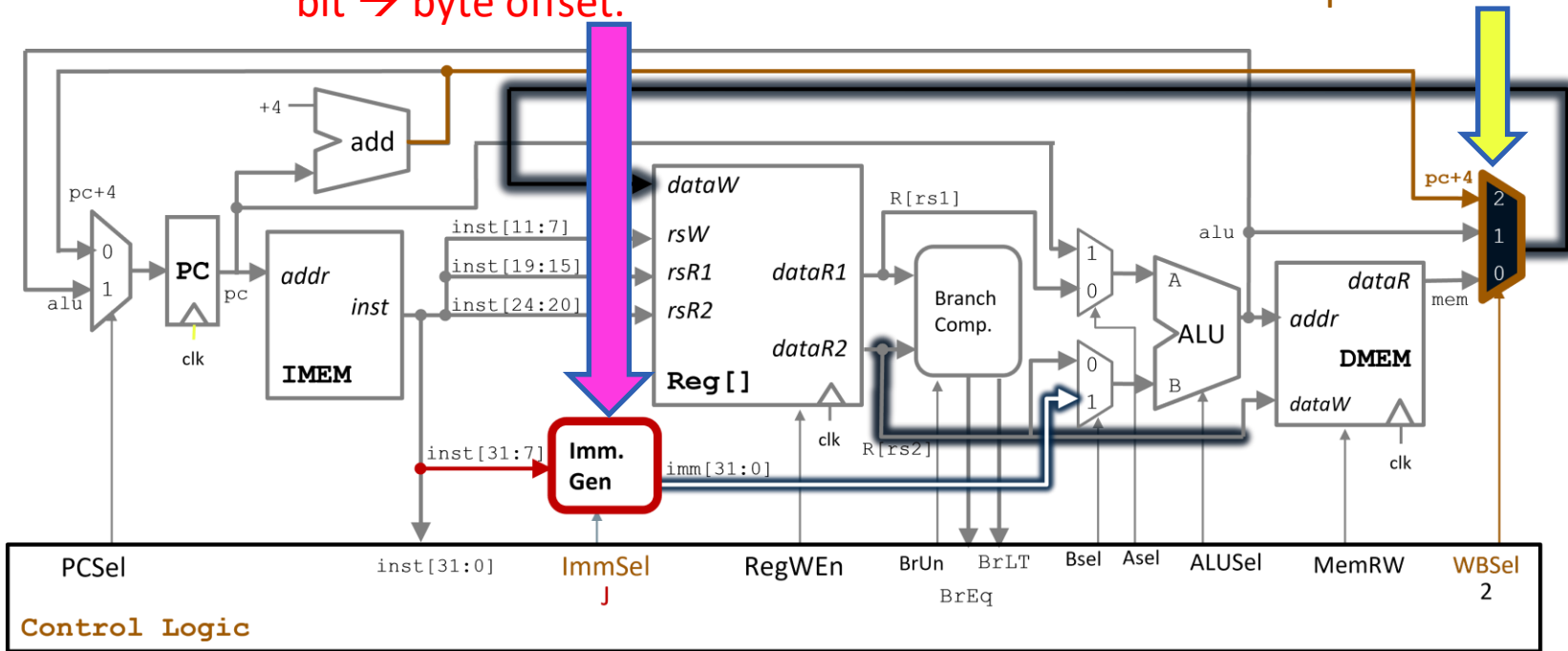To save $rd = PC + 4$,
WBSEL now controls
a 3-input MUX.





Unconditional Jump (3/5)

Feed PC into blocks.

Generate byte offset

imm for 20-bit PC-


Write ALU output to PC.

relative jump.

Compute $PC + imm$.

Write **PC + 4** to destination register.

Don't write to memory.

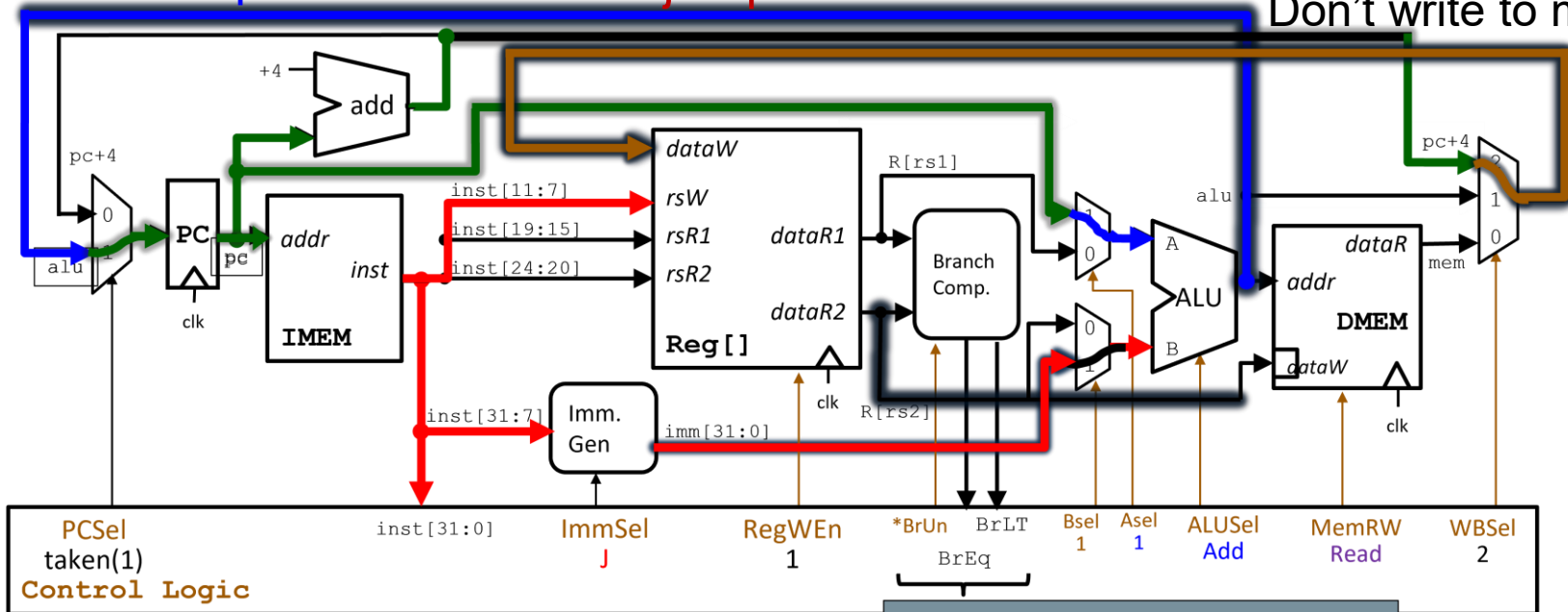


For JAL, "don't care" about branch.



Unconditional Jump (4/5)

 - **UJ-Format: jalr rd, rs1, imm (simm12)**



- **Two changes to state**

- PC $PC = R[rs1] + imm$ (absolute addressing)
- RegFile $R[rd] = PC + 4$
- jalr uses the same immediates as arithmetic/loads

Control ImmSel is based on instruction format, not instruction.
So far: **I, S, B, J**



Unconditional Jump (5/5)


Feed PC into blocks. Generate 12-bit **imm** (I-Format).

Write ALU output to PC.

Compute $PC + imm$.

Write $PC + 4$ to destination register.

Don't write to memory.

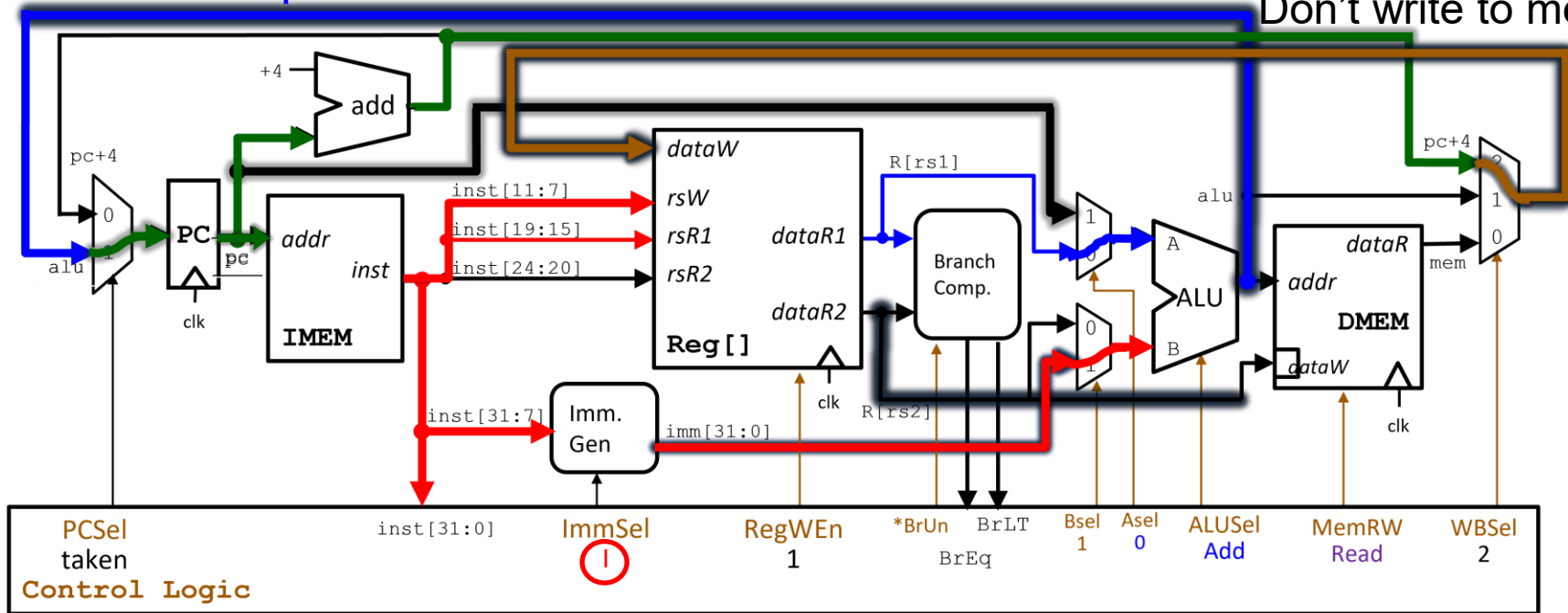



Outline


- Processor Datapath
- Immediate Generator
- Load Instruction
- Store Instruction
- Conditional Branch
- Unconditional Jump
- **U-Format Instruction**



U-Format Instruction(1/4)

- “Upper Immediate” instruction:

- opname rd, immed

 

Immediate represents *upper 20 bits* of a 32-bit immediate **imm**.


“Destination” Register

- **lui**: Load Upper Immediate (lui rd, uimm20)
- **auipc**: Add Upper Immediate to PC (auipc rd, uimm20)
- Both increment PC to next instruction and save to destination register



U-Format Instruction(2/4)

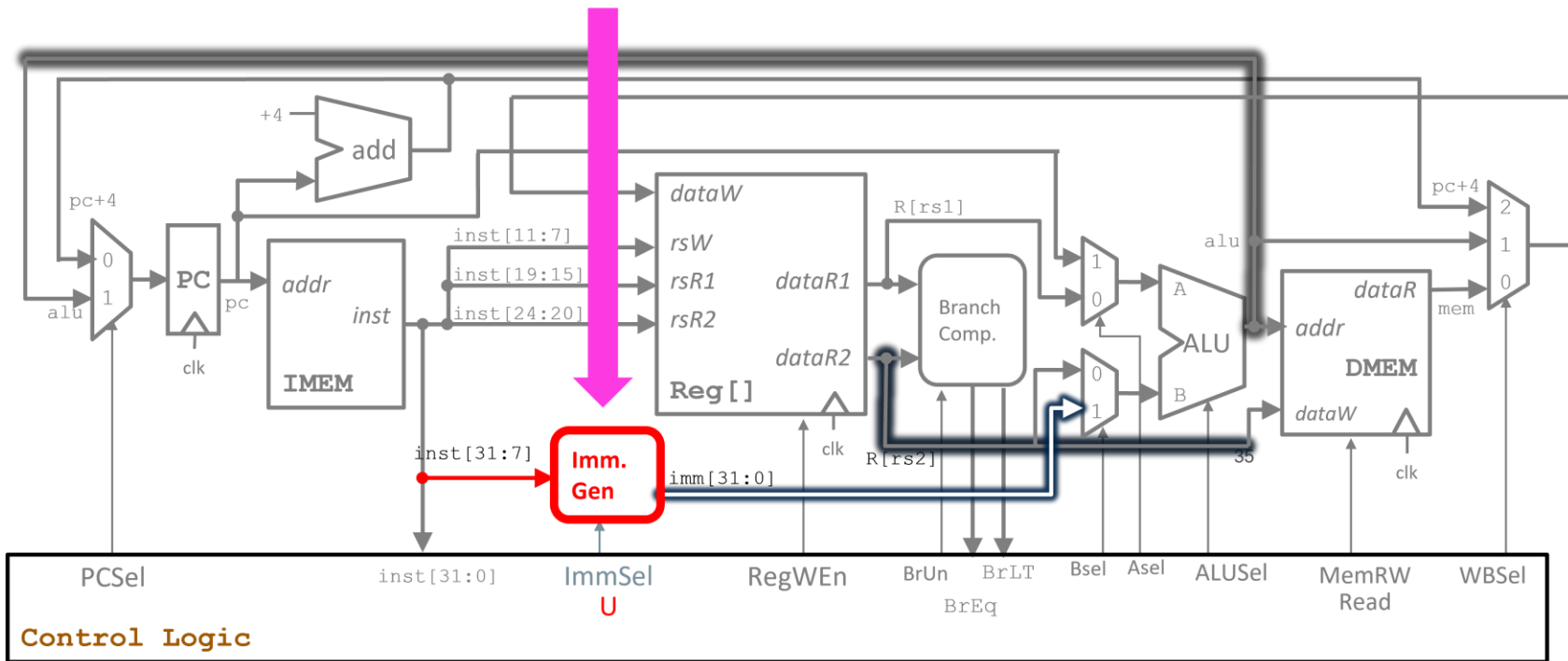Generate **imm** with
upper 20 bits. (U-format)





U-Format Instruction(3/4): LUI

Write result to destination register.


Increment PC to next instruction.

Generate **imm** with upper 20 bits. (U-format)

Grab only **imm**!

(ALUSel=B)

Don't write to memory.

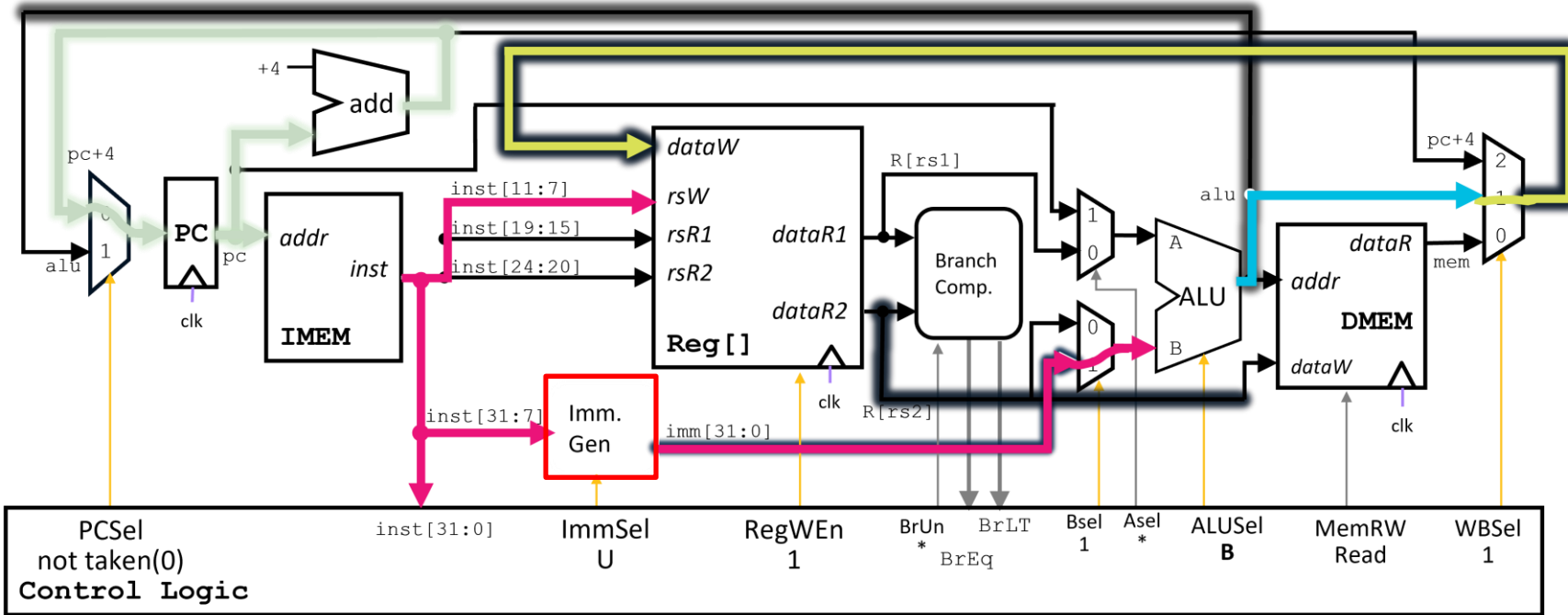



U-Format Instruction(4/4): AUIPC


Write result to destination register.

Increment PC to next instruction.

Generate **imm** with upper 20 bits. (U-format)


Add PC + **imm!**

Don't write to memory.

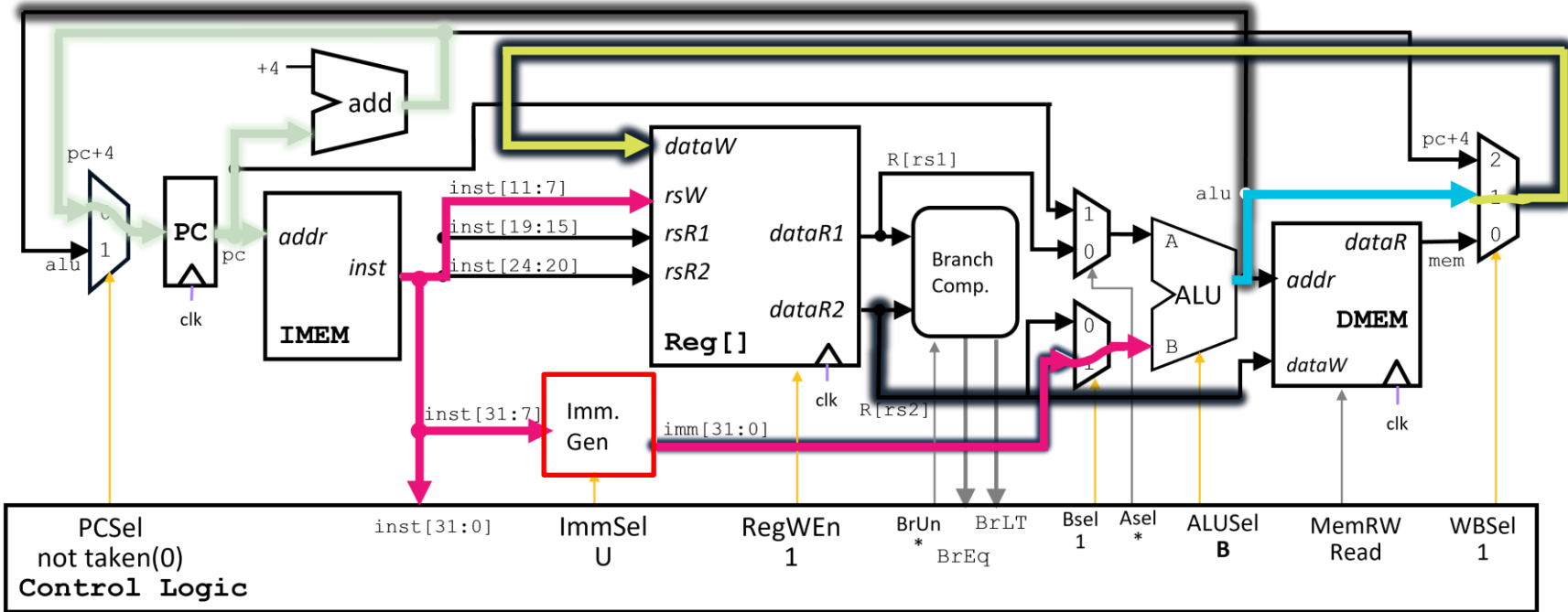



Datapath with Control Signal(1/6)

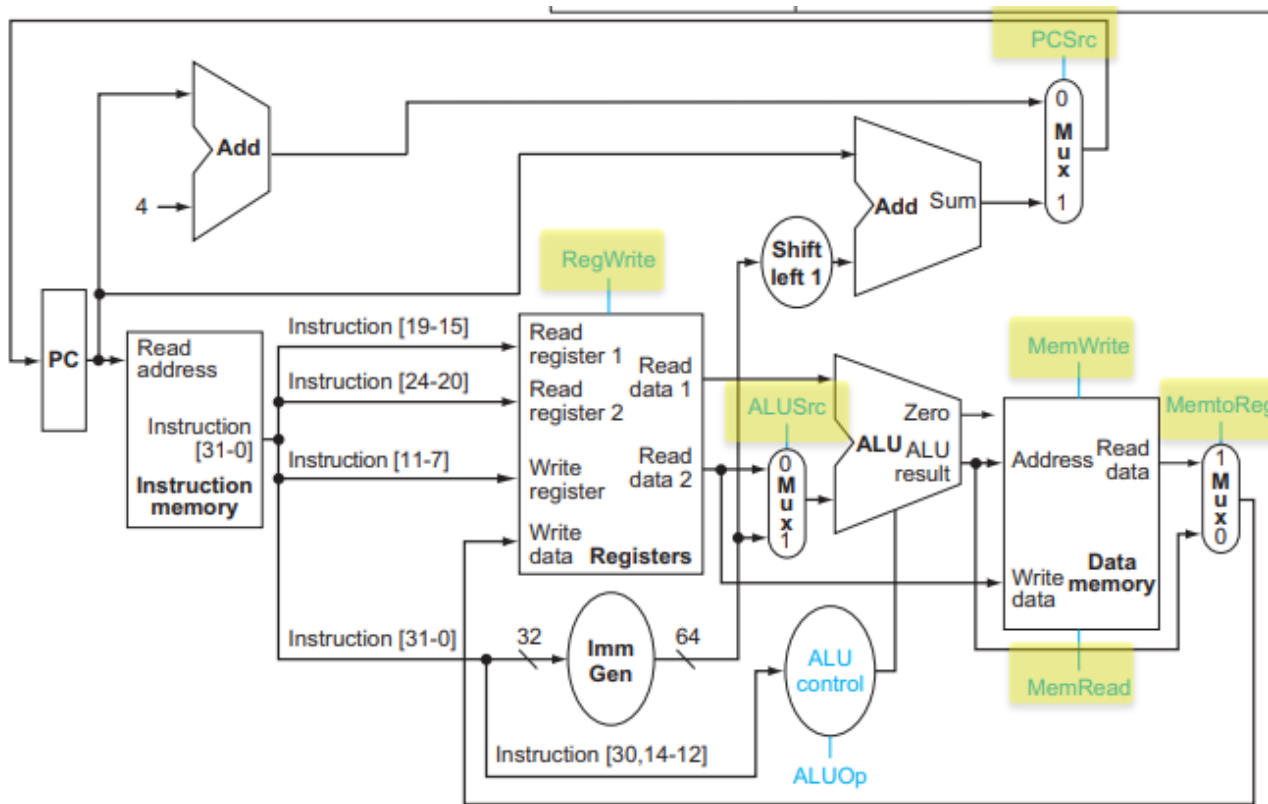



Datapath with Control Signal(2/6)

- Six Control Signals

Signal name	Effect when deasserted	Effect when asserted
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrc	The second ALU operand comes from the second register file output (Read data 2).	The second ALU operand is the sign-extended, 12 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of PC + 4.	The PC is replaced by the output of the adder that computes the branch target.
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input.
MemtoReg	The value fed to the register Write data input comes from the ALU.	The value fed to the register Write data input comes from the data memory.



Datapath with Control Signal(3/6)

- **Six 1-bit control**

- **PCSrc:**

- MUX input to select PC+4 or PC+offset
- For beq instruction to select next instruction

- **ALUSrc**

- MUX input to select input from rs2 or immediate
- For R/I-type ALU and load instruction

- **RegWrite**

- Enable signal to enable write to register
- For ALU, and load instruction (write to register)



Datapath with Control Signal(4/6)

- **Six 1-bit control**

- **MemRead:**

- Enable signal to enable read from memory
- For load instruction

- **MemWrite**

- Enable signal to enable write from memory
- For store instruction

- **MemtoReg**

- MUX input to select input to write to register from memory or ALU
- For ALU, and load instruction (write to register)



Datapath with Control Signal(5/6)

- **One 4-bit control: ALU operation**
 - **2-bit ALUOp (left)**
 - For enabling certain input (A invert or B invert)
 - **2-bit ALUOp (right)**
 - For enabling one MUX control signal
 - 00 is “and”, 01 is “or”, 10 is add, 11 is set on less than

ALUOp	Function
0000	and
0001	or
0010	add
0110	subtract
0111	set on less than
1100	nor



Datapath with Control Signal(6/6)

- **Setting six 1-bit controls**

Instruction	ALUSrc	Memto-Reg	Reg-Write	Mem-Read	Mem-Write	Branch	ALUOp1	ALUOp0
R-format	0	0	1	0	0	0	1	0
ld	1	1	1	1	0	0	0	0
sd	1	X	0	0	1	0	0	0
beq	0	X	0	0	0	1	0	1



RV32I Datapath

