



# Lecture 2: Hardware

## **CS10014 Computer Organization**

Tsung Tai Yeh

Department of Computer Science  
National Yang Ming Chiao University



# Acknowledgements and Disclaimer

- Slides were developed in the reference with
  - CS 61C at UC Berkeley
    - <https://inst.eecs.berkeley.edu/~cs61c/sp23/>
  - CS 252 at UC Berkeley
    - <https://people.eecs.berkeley.edu/~culler/courses/cs252-s05/>
  - EEC 170 at University of UC Davis
    - <https://www.ece.ucdavis.edu/~soheil/private/EEC170/>





# Outline

- Binary Arithmetic
- Adder
- Subtraction
- Multiplier
- Division


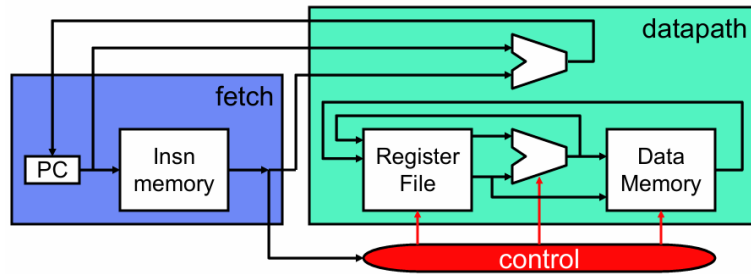 
# Central Processing Unit (CPU)


- Inside a CPU
  - **Datapath**: performs computation
    - Includes registers, ALUs ...
  - **Control**: determines which computation is performed
    - Routes data through datapath
  - **Fetch**: get insn, translate opcode into control
  - **Fetch**->**Decode**->**Execute** “cycle”




 
# Arithmetic Logic Unit (ALU)

- The ALU is used to compute the result of R-type instructions (ADD, SUB, ADDI, AND, OR)




When  $S = 00$ ,  $R = A + B$   
When  $S = 01$ ,  $R = A - B$   
When  $S = 10$ ,  $R = A \& B$   
When  $S = 11$ ,  $R = A | B$


 
# Arithmetic Logic Unit (ALU)

- The ALU is used to compute the result of R-type instructions (ADD, SUB, ADDI, AND, OR)
  - A 32-bit bitwise AND unit
  - A 32-bit bitwise OR unit
  - A 32-bit ADD/SUBTRACT unit with a control line
  - The logic to output carry
  - Overflow
  - Zero
  - Negative





# Binary Arithmetic

- Computers represent integers in binary (base2)
  - $3 = 11_2$ ,  $4 = 100_2$ ,  $5 = 101_2$ ,  $30 = 11110_2$
- Addition take place as usual (carry the 1, etc.)

$$\begin{array}{r} 17 = \quad 10001 \\ +5 = \quad \quad 101 \\ \hline 22 = \quad 10110 \end{array}$$

Carry out from the  
second column /  
Carry into the third  
column

$$\begin{array}{r} 1\boxed{1}\boxed{1} \\ + 101 \\ + 111 \\ \hline 100 \end{array}$$

Carry in to the  
second column



# Binary Arithmetic

- In hardware, integers have **fixed width**
  - N bits: 16, 32, or 64
  - LSB is  $2^0$ , MSB is  $2^{N-1}$
  - Range: 0 to  $2^N-1$





# Binary Arithmetic

- What about negative integers in binary numbers
  - Unsigned plus one bit for sign
    - $10 = 000001010$ ,  $-10 = 100001010$
    - Range:  $-(2^{N-1}-1)$  to  $2^{N-1}-1$
  - Option II: two's complement (2C)
    - Leading 0s mean positive number, leading 1s negative
    - $10 = 00001010$ ,  $-10 = 11110110$
    - + One representation for 0 (all zeros)
    - + Easy addition
    - Range:  $-(2^{N-1})$  to  $2^{N-1}-1$



# Binary Arithmetic

- Sign Magnitude Representation
  - The Most Significant bit of the number is a sign bit
  - The remaining bits represent the magnitude of the number in a binary form

**MSB**      **Magnitude**  
0 0 1 0 0 0 1 0

- Example: 8-bit sign-magnitude form

+34 = 0 0 1 0 0 0 1 0

-34 = 1 0 1 0 0 0 1 0



# Binary Arithmetic

- 1's Complement Representation
  - The representation of the negative number is different from the positive number representation
  - Example: The represent -34 in 1's complement form

$$\begin{array}{rcccccccc} +34 & = & 0 & 0 & 1 & 0 & 0 & 0 & 1 & 0 \\ & & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow \\ -34 & = & 1 & 1 & 0 & 1 & 1 & 1 & 0 & 1 \end{array}$$

Invert all 1s in  
that number by  
0s and 0s by 1s



# Binary Arithmetic

- 2's Complement Representation
  - The representation of the positive number as the 1's complement form
- Translate negative number from 1's complement to 2's complement form
  - Write the number corresponding to +34
  - Find 1's complement of +34
  - Add 1 to the 1's complement number



# Binary Arithmetic

- 2's Complement Representation
  - Translate negative number from 1's complement to 2's complement form
  - Write the number corresponding to +34
  - Find 1's complement of +34
  - Add 1 to the 1's complement number

$$\begin{array}{r} +34 = 00100010 \\ \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \\ 11011101 \quad (1's \text{ complement of } +34) \\ + \quad \quad \quad 1 \\ \hline -34 = 11011100 \quad (2's \text{ complement of } +34) \end{array}$$



# Takeaway Questions

- What is the 2C representation in the following numbers?
  - -1
  - 1
  - 0



# Takeaway Questions

- Still more on 2C
  - Trick to negating a number quickly:  $-B = B' + 1$ 
    - $-(1) = (0001)' + 1 = 1110 + 1 = 1111 = -1$
    - $-(-1) = (1111)' + 1 = 0000 + 1 = 0001 = 1$
    - $-(0) = (0000)' + 1 = 1111 + 1 = 0000 = 0$



# Understanding of overflow

- Carry indicates overflow

$$\begin{array}{rcccccl} & 1 & 0 & 1 & 1 & 7(\text{DEC}) \\ + & 0 & 1 & 1 & 1 & 11(\text{DEC}) \\ \hline \boxed{1} & 0 & 0 & 1 & 0 & 19(\text{DEC}) \end{array}$$


Overflow -> 19 is out of the range  
of the 4-bit value representation  
(0-15)

A	B	C	D	Unsigned
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15





# Overflow in Signed numbers (2C)

 


The range of 4-bits signed number  
 $-2^{n-1} <-> (2^{n-1} - 1) ==> -8 <-> 7$

	1	0	0	1	-7(DEC)	
+	1	1	0	1	-3(DEC)	
<hr/>						
	1	0	1	1	0	-10(DEC)

Overflow !



# Overflow in Signed numbers (2C)

 


The range of 4-bits signed number  
 $-2^{n-1} <-> (2^{n-1} - 1) ==> -8 <-> 7$

$$\begin{array}{rcccc} & 0 & 1 & 1 & 1 & & 7(\text{DEC}) \\ + & 0 & 0 & 0 & 1 & & 1(\text{DEC}) \\ \hline & 1 & 0 & 0 & 0 & & -8(\text{DEC}) \end{array}$$

Overflow !



# Overflow in Signed numbers (2C)

 


The range of 4-bits signed number  
 $-2^{n-1} \leftrightarrow (2^{n-1} - 1) \implies -8 \leftrightarrow 7$

	0	1	1	1	7(DEC)
+	0	0	0	1	1(DEC)
	<hr/>				
	1	0	0	0	-8(DEC)

Overflow ! How to fix this problem?



# Overflow in Signed numbers (2C)

 

The range of 5-bits signed number  
 $-2^{n-1} \leftrightarrow (2^{n-1} - 1) \implies -16 \leftrightarrow 15$

0	0	1	1	1	7(DEC)
+	0	0	0	0	1(DEC)
<hr/>					
0	1	0	0	0	8(DEC)

Extend 4-bit value to 5 bits to hold  
the correct result



# What is sign extension?

- Sign-extension
  - Copying the sign bit of the un-extended value to all bits on the left side of the larger-size value
  - **SEXT** instruction widens the data while maintaining its sign and value.
  - e.g. widen the data while maintaining its sign and value
  - **Unsigned number**, converts positive values, provided the sign bit is zero

01001000 <- 8-bit value of 72

00000000 01001000 <- extended to 16-bit value

00000000 00000000 00000000 01001000 <- extended 32-bit value



# What is sign extension?

- 8-bit encoding of decimal **signed number** -56 can be sign-extended as follows:

**Sign**

**0**0111000 <- 8-bit value of 56

11000111 <- 8-bit value of -56 (1's complement)

11001000 <- 8-bit value of -56 (2's complement)

11111111 11001000 <- extended to 16-bit value

11111111 11111111 11111111 11001000 <- extended 32-bit value



# Binary Addition

- Repeat N times
  - Add least significant bits and any overflow from previous add
  - Carry the overflow to next addition
  - Shift two addends and sum one bit to the right
- Sum of two N-bit numbers can yield an N+1 bit number
  - - More steps (smaller base)
  - + Each one is simple (adding just 1 and 0)
    - So simple, then we can do it in hardware


$$\begin{array}{rcl} & \textcolor{red}{1} & \textcolor{red}{111111} \\ 43 & = & 00101011 \\ +29 & = & \underline{00011101} \\ 72 & = & 01001000 \end{array}$$



# The Half Adder

- How to add two binary integers in hardware?
- Start with adding two bits
  - $S = A \oplus B$
  - $CO \text{ (Carry out)} = AB$
  - This is called a **half adder**

<u>A</u>	<u>B</u>	<u>=</u>	<u>CO</u>	<u>S</u>
0	0	=	0	0
0	1	=	0	1
1	0	=	0	1
1	1	=	1	0

 






# The Full Adder

- The full adder

- $S = C'A'B + C'AB' + CA'B' + CAB = C \oplus A \oplus B$
- $CO = C'AB + CA'B + CAB' + CAB = CA + CB + AB$


<u>C</u>	<u>A</u>	<u>B</u>	=	<u>CO</u>	<u>S</u>
0	0	0	=	0	0
0	0	1	=	0	1
0	1	0	=	0	1
0	1	1	=	1	0
1	0	0	=	0	1
1	0	1	=	1	0
1	1	0	=	1	0
1	1	1	=	1	1

 


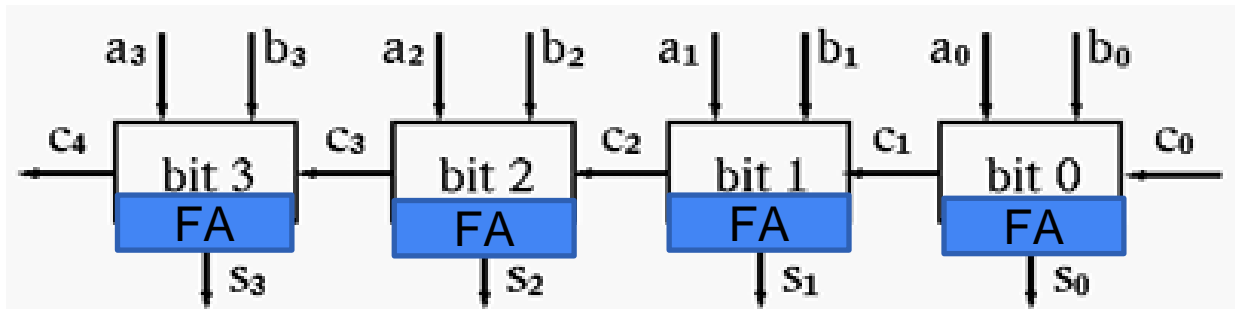
# Ripple-Carry Adder (RCA)



- N-bit ripple-carry adder (RCA)
  - N 1-bit full adders (FA) “chained” together
  - As the carry  $c_i$  needs to be passed on through all lower bits to compute the sums for the higher bits





# Ripple-Carry Adder (RCA)

- Gate delay of FA

 
 


- $C_{i+1} = x_i y_i + x_i c_i + y_i c_i$  (2 gate delays)
- $S_i = x'_i y'_i c_i + x'_i y_i c'_i + x_i y'_i c'_i + x_i y_i c_i$  (3 gate delays)



# Ripple-Carry Adder (RCA)

- Gate delay of RCA

  


- The total gate delays of n-bit sum of RCA is  $2(n-1)+3$ 
  - When  $n = 64$ , there will be **129** gate delays
  - When  $n = 16$ , there will be **33** gate delays


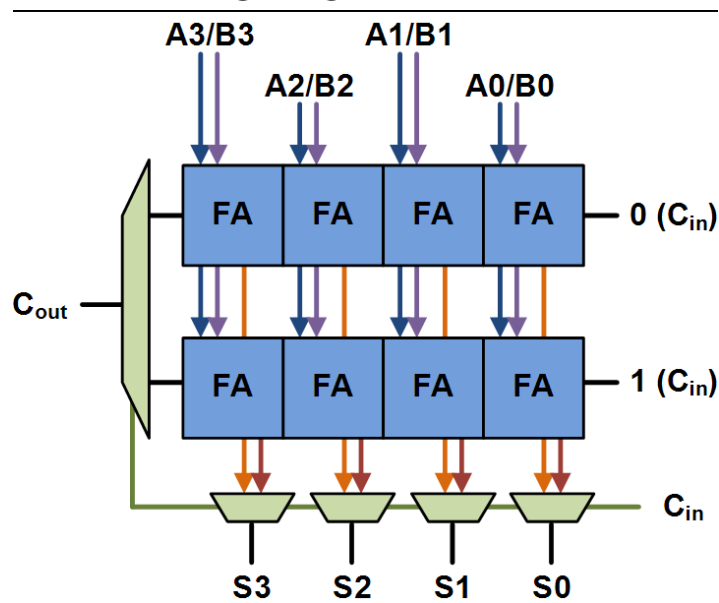
# Carry-Select Adder (CSA)


- Consists of RCAs and a multiplexer
  - Compute the  $(n + 1)$ -bit sum of two  $n$ -bit numbers
  - Simple but fast, having a gate level depth of  $O(\sqrt{n})$




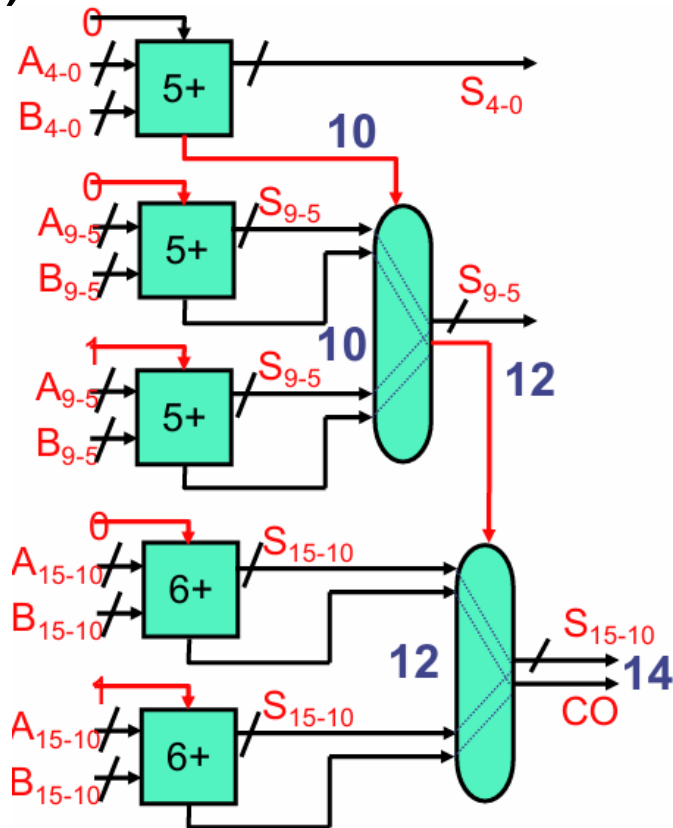
# Carry-Select Adder (CSA)

- Multi-Segment CSA
  - Example: 5, 5, 6 bit = 16 bit
  - Hardware cost
    - Compute each segment with 0 and 1 carry-in
    - Serial mux chain
- Delay
  - 5-bit adder (10) +  
Two muxes (4) = 14





# Carry-Select Adder (CSA)

- What is CSA delay (two segment)?
  - $d(\text{CO}_{15}) = \text{MAX}(d(\text{CO}_{15-8}), d(\text{CO}_{7-0})) + 2$
  - $d(\text{CO}_{15}) = \text{MAX}(2*8, 2*8) + 2 = 18$
  - In general:  $2*(N/2) + 2 = N + 2$  (vs about  $2N$  for RCA)
- What if we cut adder into 4 equal pieces?
  - $d(\text{CO}_{15}) = \text{MAX}(d(\text{CO}_{15-12}), d(\text{CO}_{11-0})) + 2$
  - $d(\text{CO}_{15}) = \text{MAX}(2*4, \text{MAX}(d(\text{CO}_{11-8}), d(\text{CO}_{7-0})) + 2) + 2$
  - $d(\text{CO}_{15}) = \text{MAX}(2*4, \text{MAX}(2*4, \text{MAX}(d(\text{CO}_{7-4}), d(\text{CO}_{3-0}))+2)+2)+2$
  - $d(\text{CO}_{15}) = \text{MAX}(2*4, \text{MAX}(2*4, \text{MAX}(2*4, 2*4)+2)+2)+2$
  - $d(\text{CO}_{15}) = 2*4 + 3*2 = 14$
- N-bit adder in M equal pieces:  $2*(N/M) + (M-1)*2$



# Takeaway Questions


- What is the delay of a 16-bit CSA adder with 8 parts?
  - (A) 16
  - (B) 18
  - (C) 20
  - (D) 32




 
# Carry Lookahead Adder (CLA)



- Let's look at the single-bit carry-out function
  - $CO = AB + AC + BC = (AB) + (A+B)C$
  - $(AB)$ : Generates carry-out regardless of incoming C -> rename to **G**
    - Generate function:  $g_i = x_i \bullet y_i$
    - If  $g_i = 1$ , the  $i^{th}$  bit generate a carry,  $c_i = 1$
  - $(A+B)$ : Propagates incoming C -> rename to **P**
    - Propagate function:  $p_i = x_i + y_i$
    - $p_i$  is true when  $A_i$  or  $B_i$  is 1  $\Rightarrow p_i = A_i \vee B_i$
  - $CO_{i+1} = G_i + P_i C_i$




 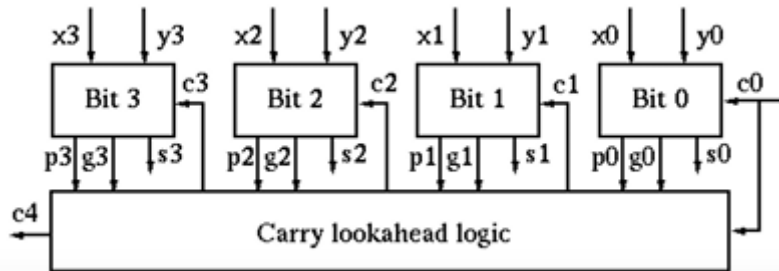
# Carry Lookahead Adder (CLA)

- The CLA requires
  - AND and OR gates with many inputs as  $n + 1$  (for  $C_n$ )
  - Both  $g_i$  and  $p_i$  can be generated for all  $n$ -bits in constant time (1 gate delay)



A	B	Ci	C i +1	Condition
0	0	0	0	No carry generate
0	0	1	0	
0	1	0	0	
0	1	1	1	No carry propagate
1	0	0	0	
1	0	1	1	
1	1	0	1	Carry generate
1	1	1	1	



# Carry Lookahead Adder (CLA)

- Infinite Hardware CLA

- Can expand  $C_1 \dots N$  in terms of  $G$ 's,  $P$ 's, and  $C_0$

- Example  $C_{16}$

- $C_{16} = G_{15} + P_{15}C_{15}$

- $C_{16} = G_{15} + P_{15}(G_{14} + P_{14}C_{14})$

- $C_{16} = G_{15} + P_{15}G_{14} + \dots + P_{15}P_{14} \dots P_2P_1G_0 + P_{15}P_{14} \dots P_2P_1P_0C_0$


- A CLA

- Generates  $c_i$  has logic in two gate delay after  $g_i$  and  $p_i$  are available
- Generates  $S_i$  has logic in three gate delay after  $g_i$  and  $p_i$  are available
- Example: the total gate delay of a 4-bit CLA is **6** ( $= 1 + 2 + 3$ )


 
# Carry Lookahead Adder (CLA)

- Is there a compromise?
  - Reasonable number of small gates?
  - Sublinear (doesn't have to be constant) latency?
  - **Multi-level CLA** exploits hierarchy to achieve this
  - Example, we pack  $n = 4$  bits as a block with carry lookahead
    - Still use ripple carry between the blocks ( $C_4, C_8, C_{12}, C_{16}$ )





# Carry Lookahead Adder (CLA)

- **Multi-level CLA**
  - There are  $n/4$  blocks in an  $n$ -bit adder, the total gate delays is

Operations	Number of Gate Delays
Generate $g_i$ and $p_i$	1
Generate $c_i$ ( $i=1,2,3,4$ ) in block 1	2
Generate $c_i$ ( $i=5,6,7,8$ ) in block 2	2
.....	.....
Generate $s_i$	3
Total	$1 + 2(n/4) + 3$

- Example: When  $n = 64$ , the number of gate delays is **36**



- Two-Level CLA

- $P_i = P_{4i+3} P_{4i+2} P_{4i+1} P_{4i}$





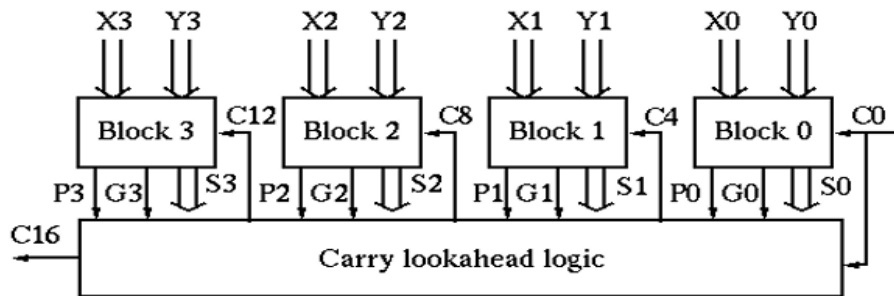
# Carry Lookahead Adder (CLA)

- Two-Level CLA

- The second-level generate and propagate functions
  - $C_4$  can be generated in constant time (independent of  $n$ )
    - $C_4 = (g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0) + (p_3p_2p_1p_0)C_0 = G_0 + P_0C_0$
    - $C_8 = G_1 + P_1C_4$ ,  $C_{12} = G_2 + P_2C_8$ ,  $C_{16} = P_3C_{12}$
  - Combine four blocks of 4-bit CLA as a super block
  - We get a 16-bit adder with two levels of carry-lookahead logic





# Carry Lookahead Adder (CLA)

- Two-Level CLA

- There are  $n/16$  super blocks in a  $n$ -bit adder
- The total gate delays can be found as

Operations	Number of Gate Delays
Generate all $g_i$ and $p_i$	1
Generate all $G_i$ and $P_i$ ( $i = 0, 1, 2, \dots$ )	2
Generate $c_i$ ( $i = 4, 8, 12, 16$ ) in Block 0	2
Generate $c_i$ ( $i = 20, 24, 28, 32$ ) in Block 1	2
.....	.....
Generate $s_i$	3
Total	$1 + 2 + 2(n/16) + 3$

- When  $n = 64$ , the number of gate delays is 14





# Carry Lookahead Adder (CLA)

- The third level of CLA

- With the carries  $C_{16}$ ,  $C_{32}$ ,  $C_{48}$ ,  $C_{64}$  generated simultaneously by the third-level carry-look ahead logic

Operations	Number of Gate Delays
Generate all $g_i$ and $p_i$	1
Generate all $G_i$ and $P_i$ ( $i = 0, 1, 2, \dots$ )	2
Generate all $\mathbf{G}_i$ and $\mathbf{P}_i$ ( $i = 0, 1, 2, \dots$ )	2
Generate $c_i$ ( $i = 16, 32, 48, 64$ ) in super block 0	2
.....	.....
Generate $s_i$	3
Total	$1 + 2 + 2 + 2(n/64) + 3$

- When  $n = 64$ , the number of gate delays is 10



# Subtraction

- Sign/magnitude subtraction is reverse addition
  - 2C subtraction is addition
- How to subtract using an adder?
  - $\text{sub } A \ B = \text{add } A \ -B$
  - Negate B before adding (fast negation trick:  $-B = B' + 1$ )



# Shift and Rotation

- Left/right shifts are useful
  - Fast multiplication/division by small constants
  - Bit manipulation: extracting and setting individual bits in words
- Right shifts
  - Can be **logical** (shift in 0s) or **arithmetic** (shift in copies of MSB)
    - srl 110011, 2 = 001100
    - sra 110011, 2 = 111100
    - Caveat: for negative numbers, sra is **not** equal to division by 2

-53 = 1111111111001011

sra 2

1111111111110010(11) = -14

^^

^^

sign

dropped

extension

53 sra 2 = floor( 53 / 2^2 ) = floor( 13.25 ) = 13  
-53 sra 2 = floor(-53 / 2^2 ) = floor(-13.25) = -14



# A Simple Shifter

- The simplest 16-bit shifter: can only shift left by 1
  - Implement using wires (no logics)
- Logical shift operators << >>
  - Performs zero-extension for >>
    - `wire [15:0] a = b << c[3:0];`
- Arithmetic shift operator >>>
  - Performs sign-extension
  - Require a signed wire input
    - `wire signed [15:0] b;`
    - `wire [15:0] a = b >>> c[3:0];`



# Multiplication

- How humans multiply
  - We first generate all partial product terms

1010      <- Multiplicand  
x 1101    <- Multiplier  
=====

1010      <- Partial Product



1010  
x 1101  
=====

1010  
0000      <- Partial Product



# Multiplication

- How humans multiply
  - We first generate all partial product terms

$$\begin{array}{r} 1010 \quad \leftarrow \text{Multiplicand} \\ \times 1101 \quad \leftarrow \text{Multiplier} \\ \hline 1010 \\ 0000 \\ 1010 \quad \leftarrow \text{Partial Product} \end{array}$$



$$\begin{array}{r} 1010 \\ \times 1101 \\ \hline 1010 \\ 0000 \\ 1010 \\ 1010 \quad \leftarrow \text{Partial Product} \end{array}$$



# Multiplication

- Then add column by column, right to left

$$\begin{array}{r} 1010 \\ \times 1101 \\ \hline \hline 1010 \\ 0000 \\ 1010 \\ 1010 \\ \hline \hline 0 \end{array} \leftarrow \text{Product}$$

$$\begin{array}{r} 1010 \\ \times 1101 \\ \hline \hline 1010 \\ 0000 \\ 1010 \\ 1010 \\ \hline \hline 10 \end{array} \leftarrow \text{Product}$$



# Multiplication

- Sometimes with one or more carry digits

$$\begin{array}{r} 1010 \\ \times 1101 \\ \hline \text{Carry} \rightarrow \begin{array}{r} 1 \\ 1010 \\ 0000 \\ 1010 \\ 1010 \end{array} \\ \hline 0010 \leftarrow \text{Product} \end{array}$$

$$\begin{array}{r} 1010 \\ \times 1101 \\ \hline \begin{array}{r} 1111 \\ 1010 \\ 0000 \\ 1010 \\ 1010 \end{array} \\ \hline 10000010 \leftarrow \text{Product} \end{array}$$







# Multiplication

- Human method not best for computers
  - Each partial product must be stored -> extra hardware
  - Columns vary in size -> complexity
  - Multiple-digit carries -> complexity
  - Need a simpler method for low-cost multipliers




# Multiplication

- Shift & Add Multiply

  

Left shift multiplicand

 




# Multiplication

- Shift & Add Multiply

Left shift multiplicand

1010	<- Multiplicand
x 1101	<- Multiplier
=====	
00001010	<- Old Product
00110010	<- New Product

 

Left shift multiplicand

1010	<- Multiplicand
x 1101	<- Multiplier
=====	
00110010	<- Old Product
10000010	<- New Product






# Multiplication

- Shift & Add Multiply
  - Computer multiply also shifts multiplier right so current multiplier bit is at a fixed position, the least significant bit (LSB)



# Multiplication




- Shift & Add Multiply

   



# Multiplication

- Shift & Add Multiply

   



# Multiplication


- Shift & Add Multiply
  - Shift & Add Multiply in C programming

```
int product = 0;
for (int i = 0; i < 32; i++)
    if ((multiplier >> i % 2) == 1)
        product = product + multiplicand << i;
```


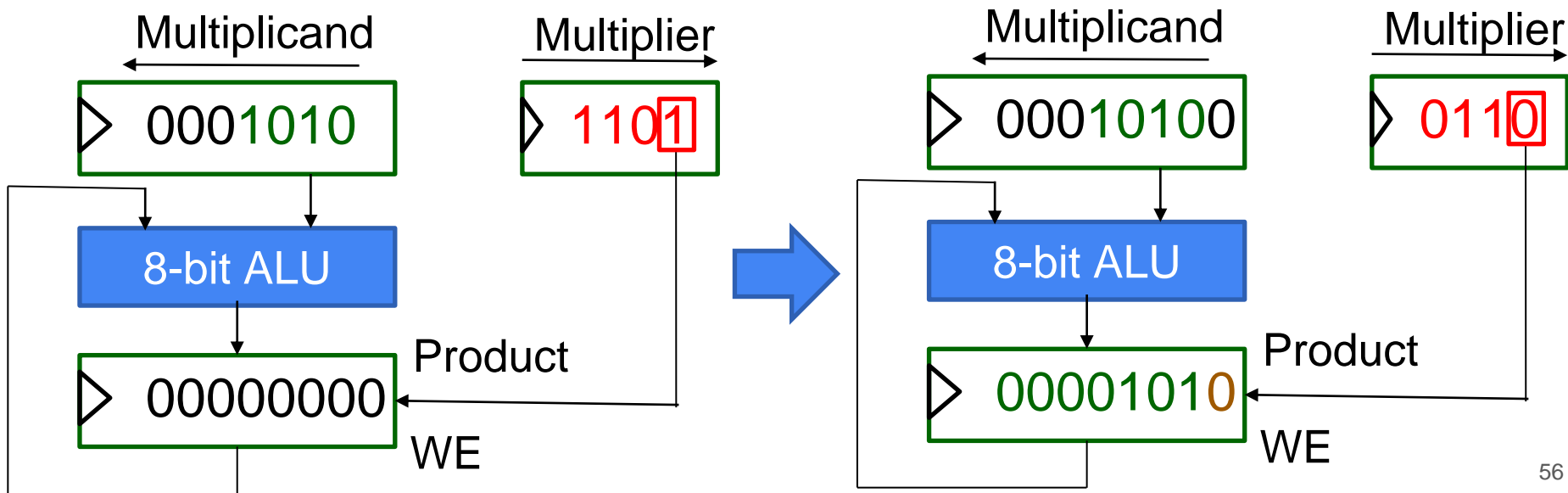
# Multiplication

- Simple Shift & Add Multiply Hardware
  - Multiplier LSB is write enable for product latch








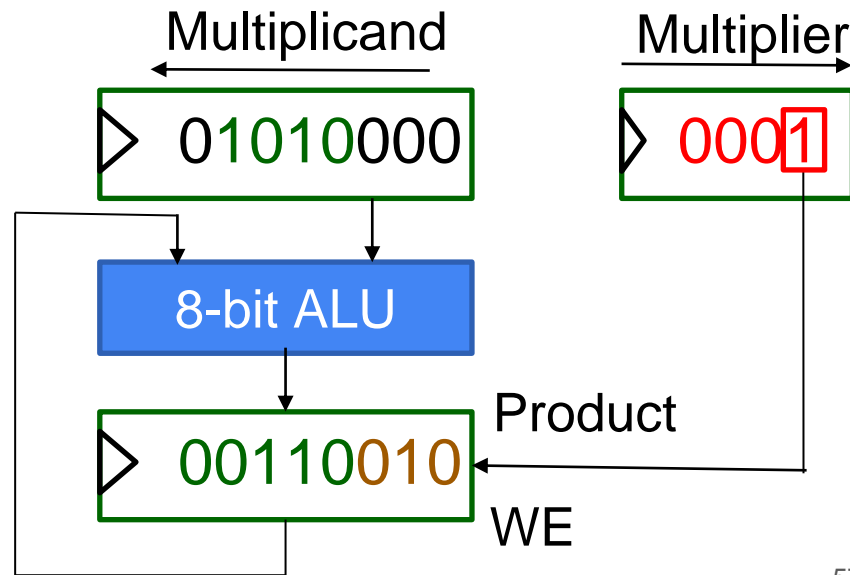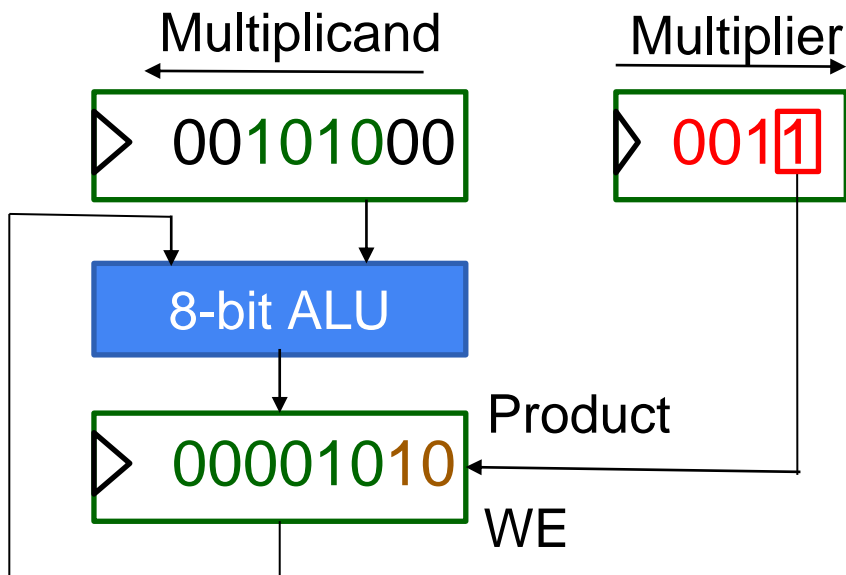
# Multiplication


- Simple Shift & Add Multiply Hardware
  - Multiplier LSB is write enable for product latch




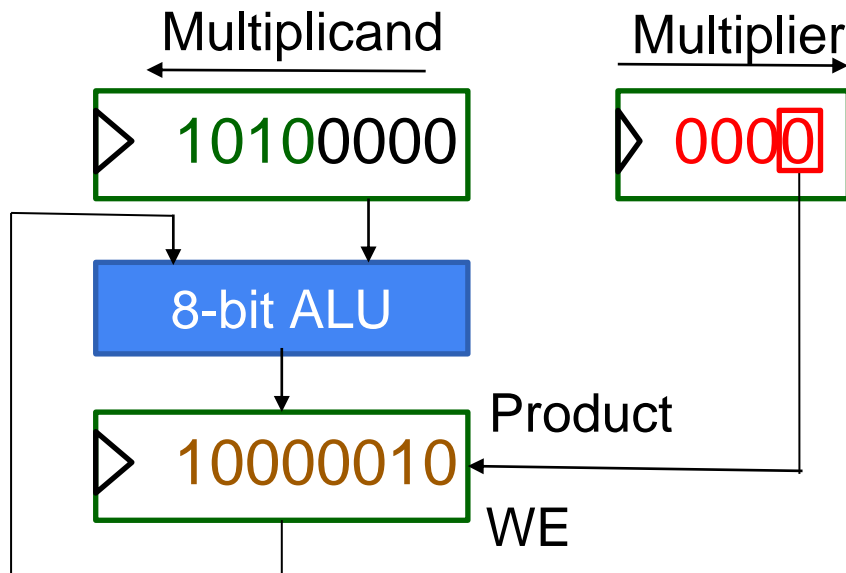
# Multiplication

- Simple Shift & Add Multiply Hardware
  - Multiplier LSB is write enable for product latch






# Multiplication

- This simple shift & add hardware
  - Only  $N$  significant bits are being summed each cycle, but we are using a  $2N$ -bit adder, a waste
  - Each cycle, one new bit of the product is resolved, while one old bit of the multiplier is discarded
  - Simple multiply shifts Multiplicand left and keep product stationary


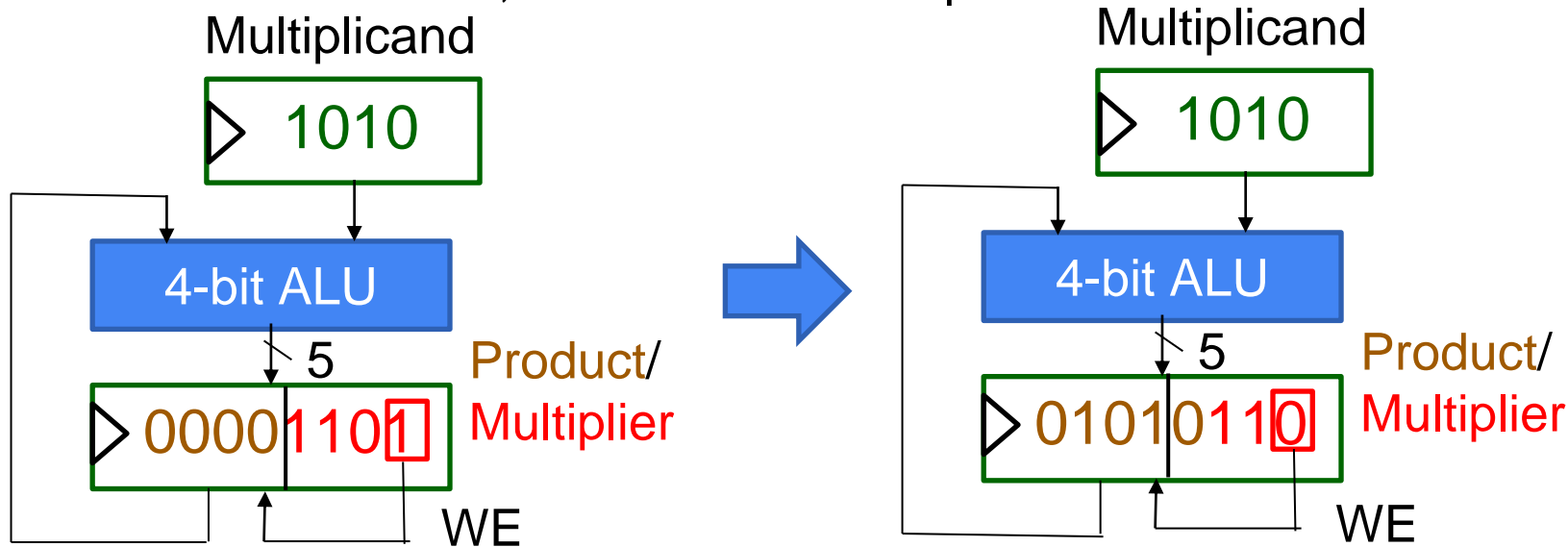
# Multiplication



- Refined shift & add hardware
  - ALU input is accept/not accept based on WE
  - When WE = 0, shift but no ALU input




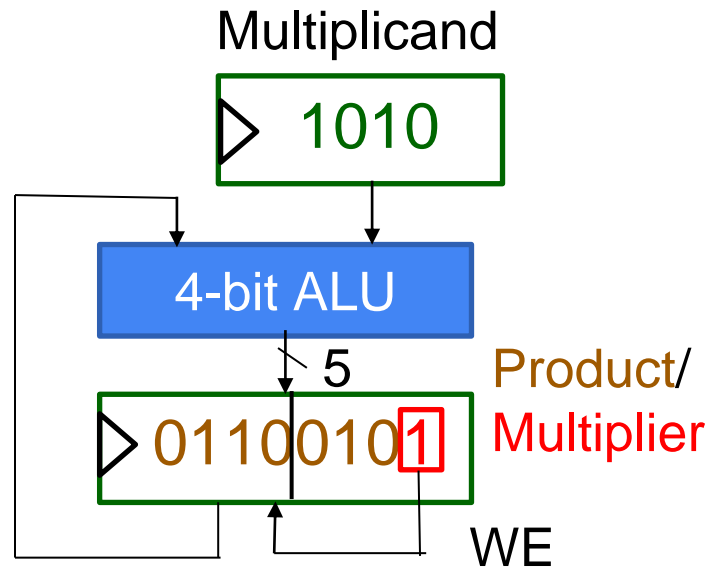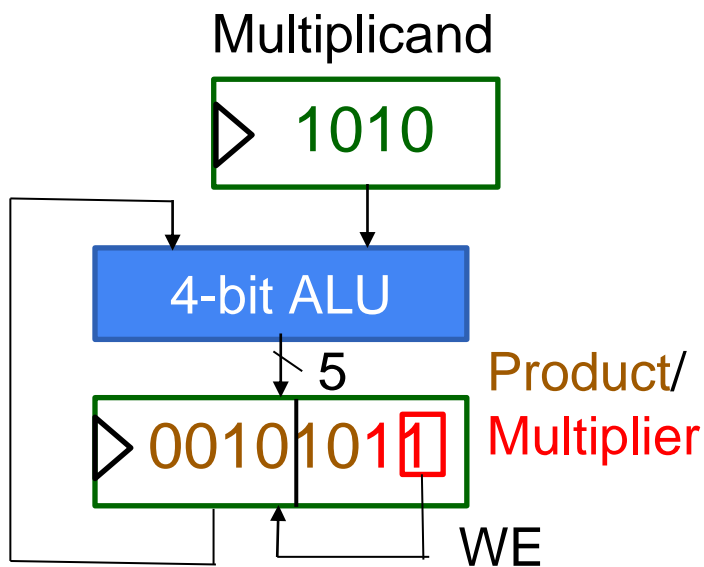
# Multiplication


- Refined shift & add hardware
  - ALU input is accept/not accept based on WE




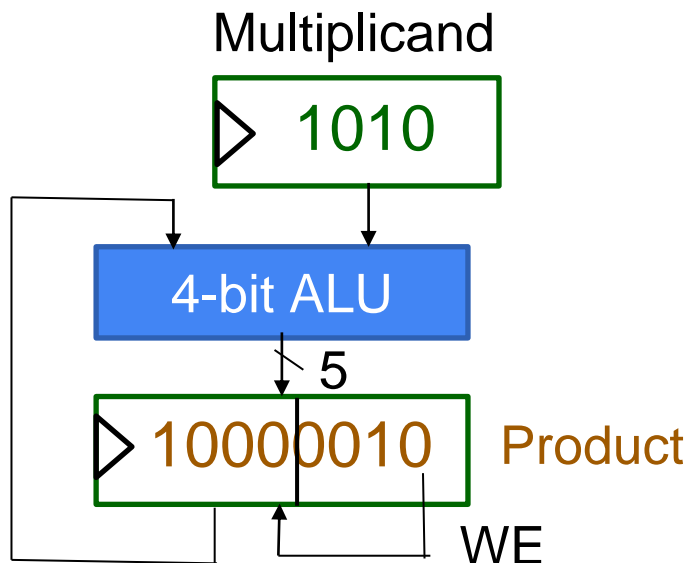
# Multiplication

- Refined shift & add hardware
  - Final Result:  $10 \times 13 = 130$





# Signed Multiplication

- Shift & Add Multiply only works for positive numbers
- To include negative numbers must:
  - Save XOR of sign bits to get product sign bit
  - Convert multiplier/multiplicand to positive
  - Do shift and add algorithm
  - Negate result if product sign bit is 1



# Signed Multiplication

- Booth's algorithm
  - Handle positive/negative number uniformly
  - E.g.  $01110_2 (14_{10}) = 10000_2 (16_{10}) - 00010_2 (2_{10})$   
 $= \textcolor{blue}{1}0000_2 - 000\textcolor{red}{1}0_2$
  - Convert string of 1s into leading  $\textcolor{blue}{+1}$  and a trailing  $\textcolor{red}{-1}$





# Signed Multiplication

- Booth's algorithm

- Identify leading **+1s** and trailing **-1s** in multiplier bit position  $i$  by looking at multiplier bit  $i$  and bit  $i-1$

- Example

- $1_{10} = 000\boxed{10} \Rightarrow 1$
- $1_{10} = 00\boxed{010} \Rightarrow 11$
- $1_{10} = 00\boxed{010} \Rightarrow 011$
- $1_{10} = \boxed{00010} \Rightarrow 0011$
- $1_{10} = 2 - 1 = 1$

		$i$	$i-1$
<b>-1</b>	for	1	0
<b>+1</b>	for	0	1
0	for	0	0
0	for	1	1



# Signed Multiplication

- Booth's algorithm

- Identify leading **+1s** and trailing **-1s** in multiplier bit position  $i$  by looking at multiplier bit  $i$  and bit  $i-1$

- Example

- $-1_{10} = 11110 \Rightarrow 1$
- $-1_{10} = 11110 \Rightarrow 01$
- $-1_{10} = 11110 \Rightarrow 001$
- $-1_{10} = 11110 \Rightarrow 0001$
- $-1_{10} = -1$

		$i$	$i-1$
<b>-1</b>	for	1	0
<b>+1</b>	for	0	1
0	for	0	0
0	for	1	1



# Signed Multiplication

- Booth's algorithm

- Identify leading **+1s** and trailing **-1s** in multiplier bit position  $i$  by looking at multiplier bit  $i$  and bit  $i-1$

- Example



- $-6_{10} = 10100 \Rightarrow 0$
- $-6_{10} = 10100 \Rightarrow 10$
- $-6_{10} = 10100 \Rightarrow 110$
- $-6_{10} = 10100 \Rightarrow 1110$
- $-6_{10} = -8 + 4 - 2 = -6$

		$i$	$i-1$
<b>-1</b>	for	1	0
<b>+1</b>	for	0	1
0	for	0	0
0	for	1	1


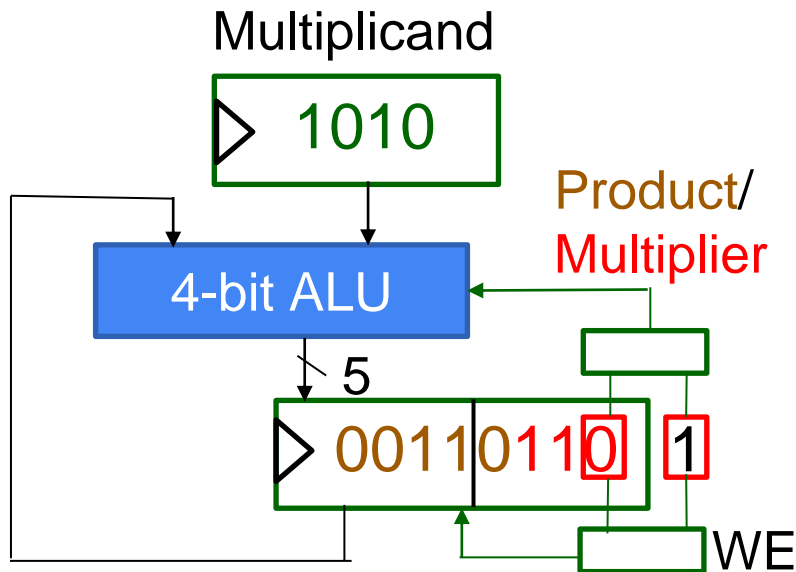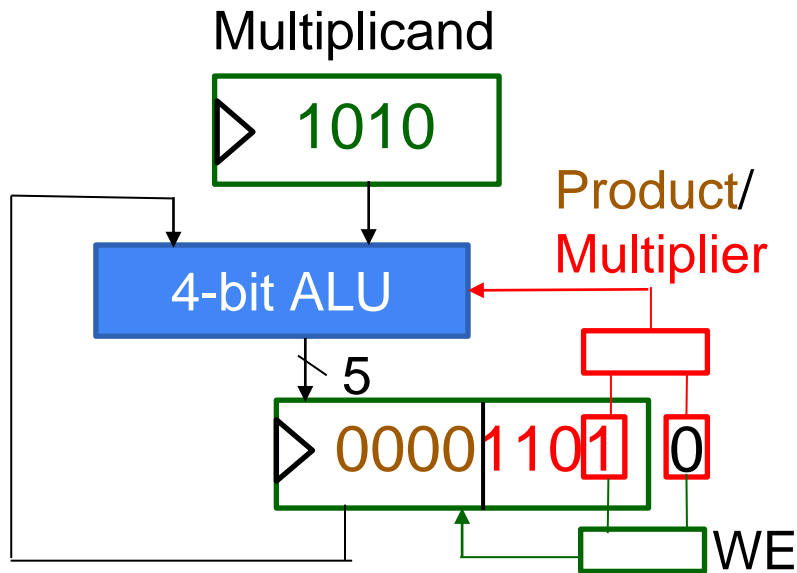
# Booth's Algorithm Hardware



- Use ALU to **ADD** or **SUB** based on the trailing -1s, leading 1s from the Multiplier




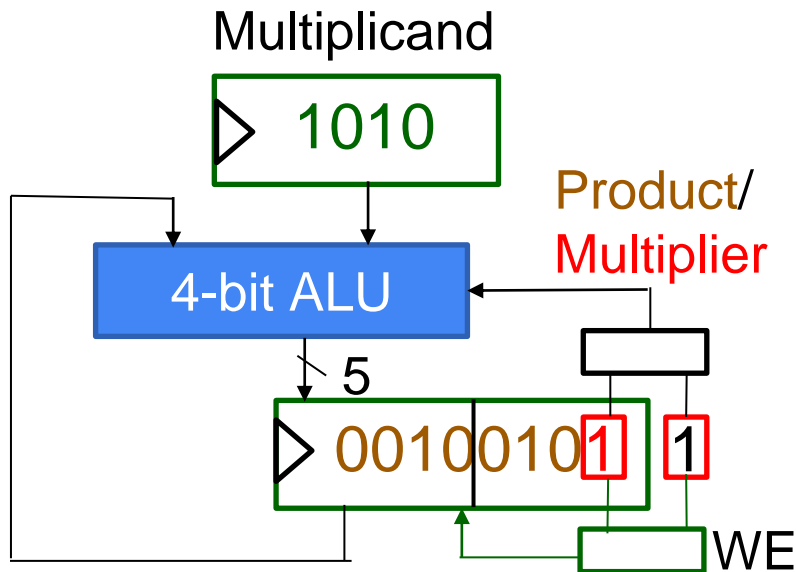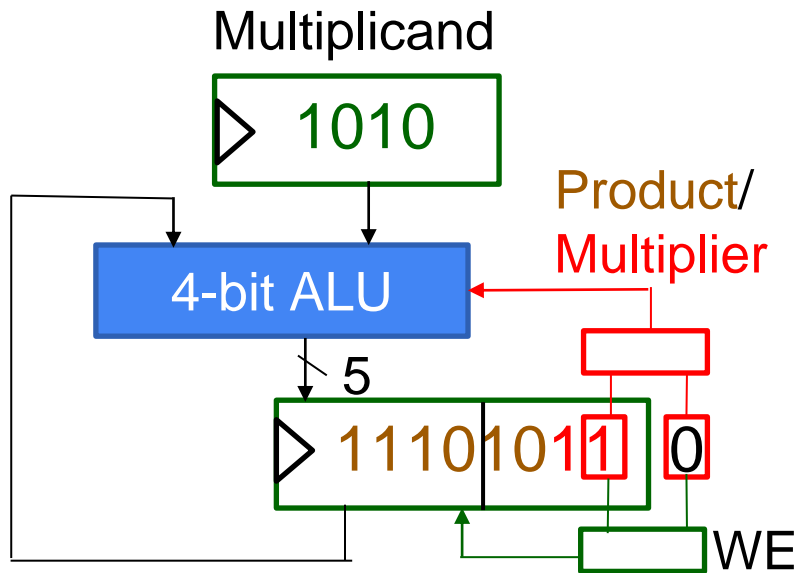
# Booth's Algorithm Hardware


- Use ALU to **ADD** or **SUB** based on the trailing -1s, leading 1s from the Multiplier





# Booth's Algorithm Hardware

- Final Result:  $-6 \times -3 = 18$

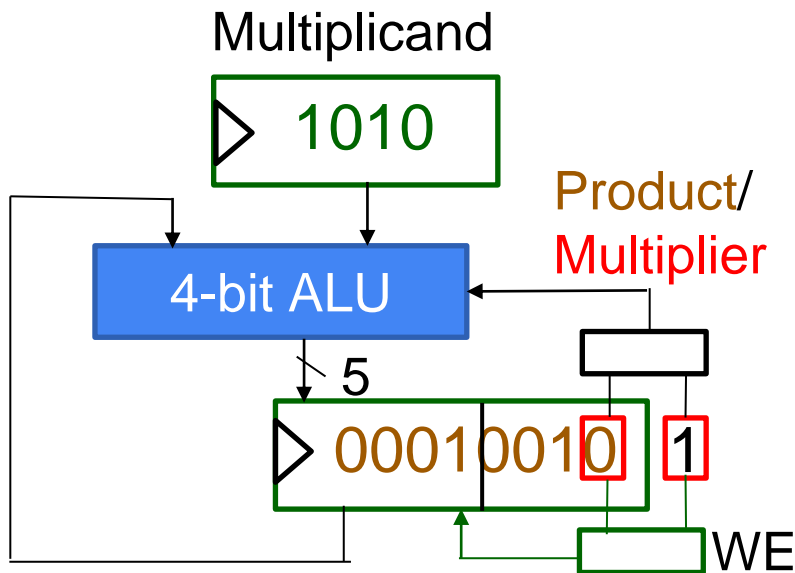




# Wallace Tree Multiplier

- Partial products produced sequentially (slow)

1010 Multiplicand  
x 1101 Multiplier  
=====

1010  
0000  
1010  
1010 Partial Products

 - Partial products produced using array of AND gates (fast)






# Wallace Tree Multiplier


- Wallace Tree Reducers

- Full adder cells used to reduce column segment of height 3 to row of width 2
  - Sum and carry out
- Half adders used selectively for height-3 column that does not need full reduction

Full Adder

 

Half Adder

 






# Wallace Tree Multiplier

- Wallace Tree: 4 x 4 example


Stage 1

 



# Wallace Tree Multiplier




- Wallace Tree: 4 x 4 example

 




# Wallace Tree Multiplier

- Wallace Tree: 4 x 4 example

   



# Wallace Tree Multiplier

 



# Wallace Tree Multiplier

- Wallace tree fast multiply
  - column height is reduced by about 2/3 during each level
- For NxN multiply, an estimate for number of levels

$$\begin{aligned} N \times (2/3)^x &= 2, (2/3)^x = 2/N, x \log_2(2/3) = \log_2(2/N), \\ x &= \log_2(2/N) / \log_2(2/3), x = (\log(2) - \log(N)) / -0.6, \\ x &= -1.7 \times (1 - \log_2(N)) \end{aligned}$$

- 2 levels for  $N = 4$
- 4 levels for  $N = 8$
- 7 levels for  $N = 32$



# Division

- Consider a long division example

$$\begin{array}{r} \text{Divisor } 1234_{10} \overline{) 7006789_{10}} \\ \underline{7006} \phantom{00} \\ 8367 \phantom{00} \\ \underline{-7404} \phantom{00} \\ \dots \\ \underline{\phantom{00}137} \phantom{00} \end{array}$$

Quotient:  $0005678_{10}$   
Dividend:  $7006789_{10}$   
Partial Remainder:  $8367$   
Remainder:  $137_{10}$



# Division


- Human Division

- 1. Bring down next digit to partial remainder
- 2. Compare divisor and partial remainder
  - If partial remainder  $<$  divisor: put 0 digit in quotient, goto 1
- 3. Estimate Quotient digit
- 4. Multiply divisor by estimated digit
- 5. Subtract from partial remainder
  - IF result is negative, erase work, decrement estimated digit, goto 4
  - IF result  $>$  divisor, erase work, increment estimated digit, goto 4
  - ELSE put estimated digit in quotient, goto 1


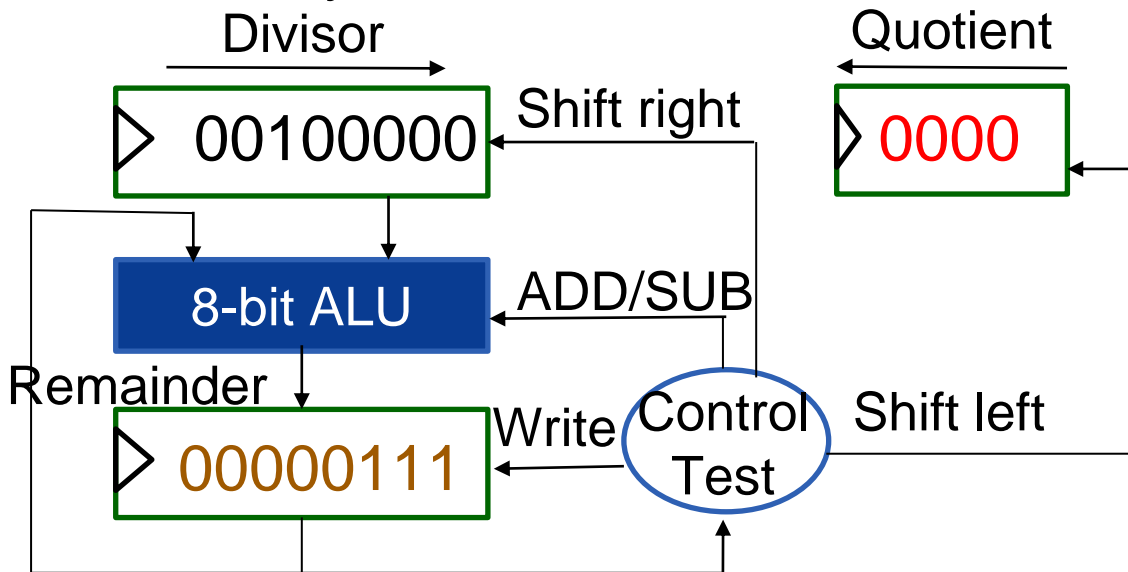
# Division

- Simple hardware divider
  - Use ALU to subtract/add shift divisor from remainder
    - Conditionally add to 'erase' work after subtract








# Division

- Simple division algorithm

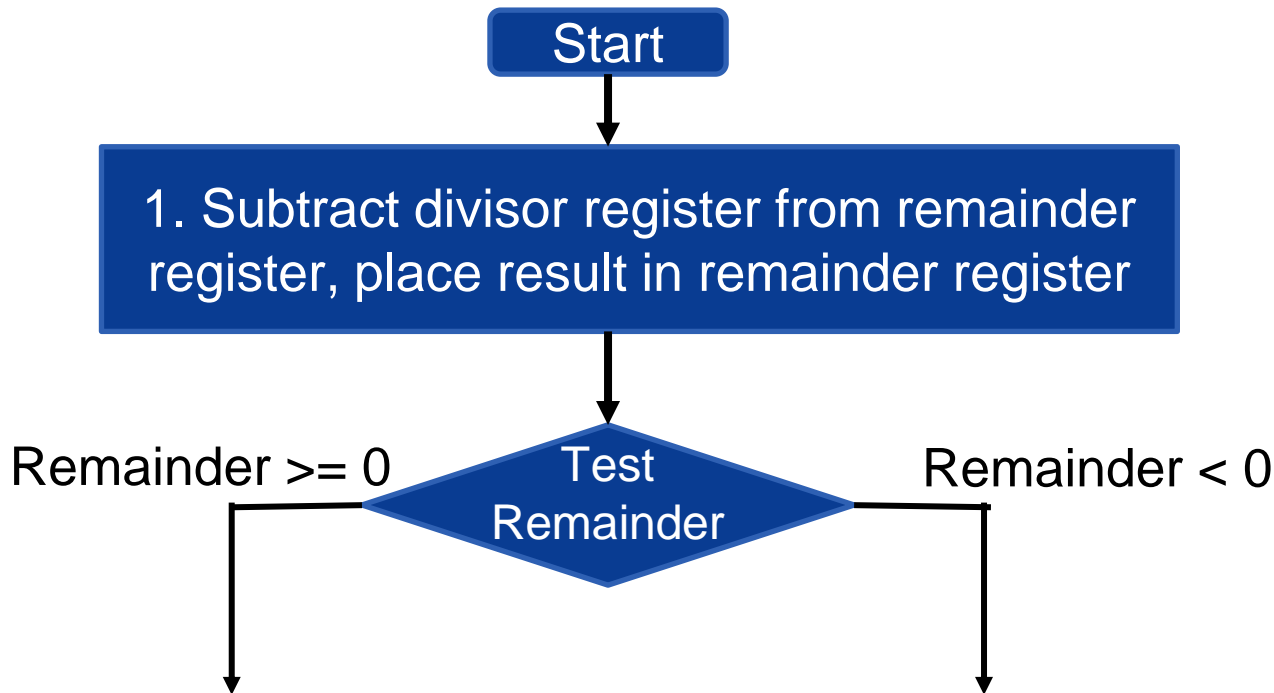



# Division

- Simple division algorithm

2a. Shift quotient register to left, set new rightmost bit to 1


2a. Restore original value by adding divisor register to remainder register, place sum in remainder register. Shift quotient register to left, set new rightmost bit to 0

3. Shift divisor register right 1 bit



# Division


- Simple division algorithm

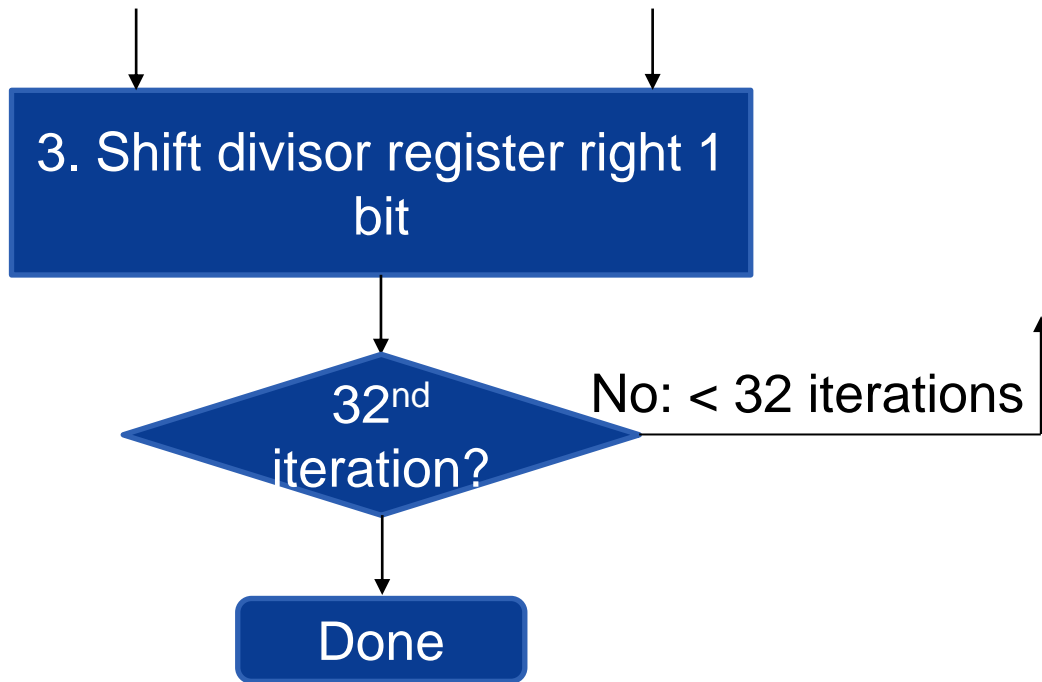


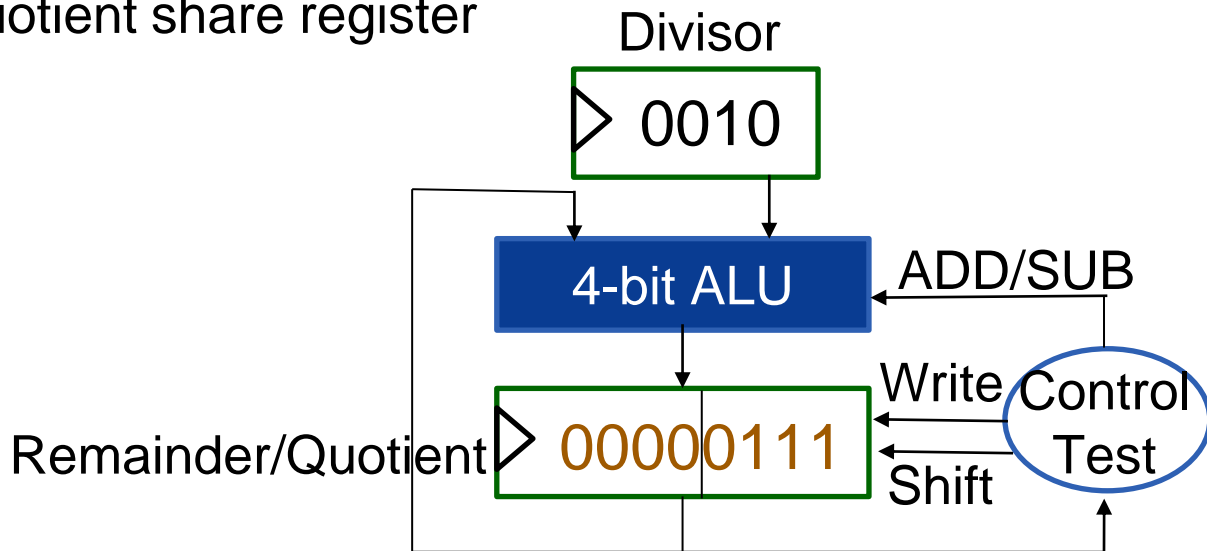
# Division

- Improved hardware divider
  - Divider, ALU are reduced in half
  - Remainder shifts left, divider fixed
  - Remainder/Quotient share register





# Division

- Signed division
  - Sign of quotient is XOR of signs of dividend and divisor
  - Sign of remainder matches sign of dividend
    - $122 / 3 = 40$  remainder 2
    - $-122 / -3 = 40$  remainder -2
    - $-122 / 3 = -40$  remainder -2
    - $122 / -3 = -40$  remainder 2



# Division

- Fast division
  - So far all ALU operations can be done in  $\log_2 N$  time units
    - Carry Look-Ahead Adder: 1 clock cycle
    - Wallace Tree Multiplier: 2 clock cycles
    - Barrel Shifter: 1 clock cycle
  - Best division algorithms take  $N$  time units (slow)
    - Resolve 4 bits per iteration rather than 1, and iterations are complex